
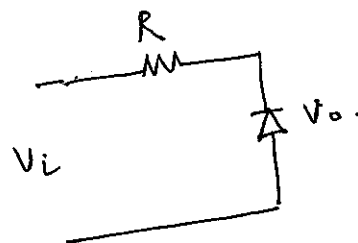
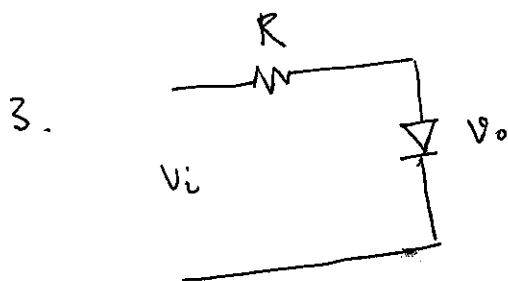
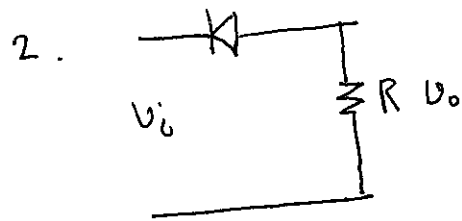


Tutorial Problem. 11.02.19.

- For the circuits shown below determine the following.
 - transition state voltage.
 - Range of V_i for which the diode is ON and the range of V_i the diode is OFF.
 - i/o relationship for diode is ON and for the diode is OFF
 - sketch V_o in correspondence to V_i

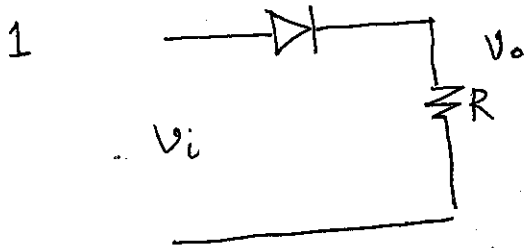Here V_i is sinusoidal wave with amplitude 10V.
[Consider the diode is Si diode]



Steps Step 1: Determine transition state voltage.


@ transition $V_D = 0.7V$, $I_D = 0$.

- Redraw the CKT assuming the diode is going through transition.
 - Apply KVL to determine V_i at which transition occurs.
- [Since, V_i is unknown, consider it +ve]


Step 2: - Draw the transition state voltage line on the V_i (input) wave shape

Step 3: Determine the range of V_i for which diode is on and range of V_i for which the diode is OFF

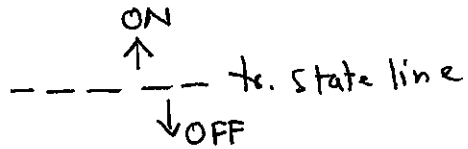If Diode orientation is clockwise direction $\left(\begin{array}{c} \rightarrow \\ \downarrow \end{array} \right)$ then



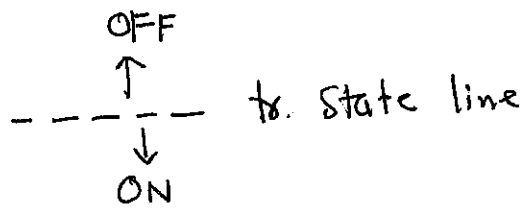If diode orientation is anticlockwise " $\begin{array}{c} \leftarrow \\ \downarrow \end{array}$ " then



Step 4. Determine i/o relation.
 when diode is "ON": Replace diode with 0.7. Redraw CKT and apply KVL.
 when diode is "OFF": Replace diode " open CKT. Redraw CKT and apply KVL

Step 5. sketch V_o ~~at~~ base on the i/o relationship.