

$$V_p = \frac{V_p}{f C R_L}, \quad V_p = \frac{V_p}{2 f C R_L}$$


$$V_p = V_m - 2V_D \text{ [F.W.B.R]}$$

$$V_p = V_m - V_D \text{ [F.W.C.T]}$$

$$\text{Ripple factor: } \frac{V_r \text{ (P-P)}}{V_{DC}}$$

$$V_{DC} = V_p - V_r/2$$

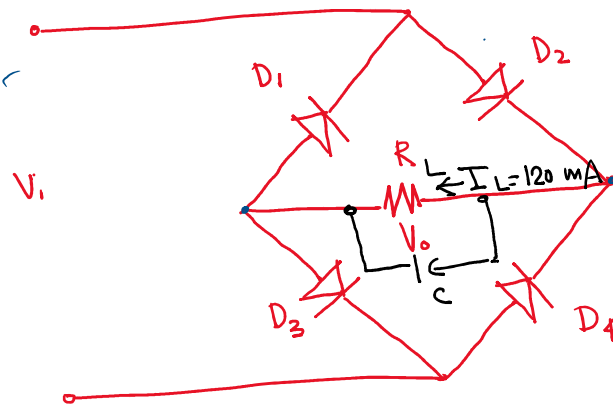Design a FW Rectifier, that delivers peak current $I_L(p) = 120 \text{ mA}$ to a Load R_L , peak output voltage $V_p = 12 \text{ V}$, $V_r \leq 5\%$ of Input max (V_m) $f = 50 \text{ Hz}$. R_L & C ?



$$R_L = \frac{V_p}{I_L(p)} = \frac{12 \text{ V}}{120 \text{ mA}} = 100 \Omega$$

$$V_r \leq 5\% \text{ of } V_m$$

$$V_p = 0.04 V_m$$

$$V_m = V_p + 2V_D$$


$$\Rightarrow V_m = V_p + 2V_D = 12 + 2 \times 0.7 = 13.4 \text{ V}$$



$$V_p = \frac{V_p}{2 f C R_L} \Rightarrow 0.04 \times 13.4 = \frac{12}{2 \times 50 \times 100 \times C}$$

$$C = \dots \dots$$

$$V_{DC} = V_p - V_r/2$$

$$R.F. = \frac{V_r}{V_{DC}}$$

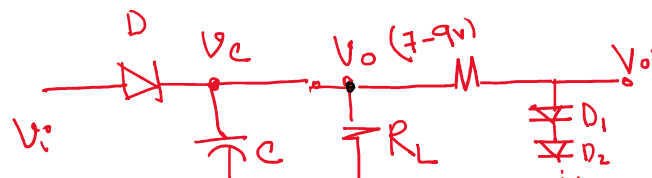

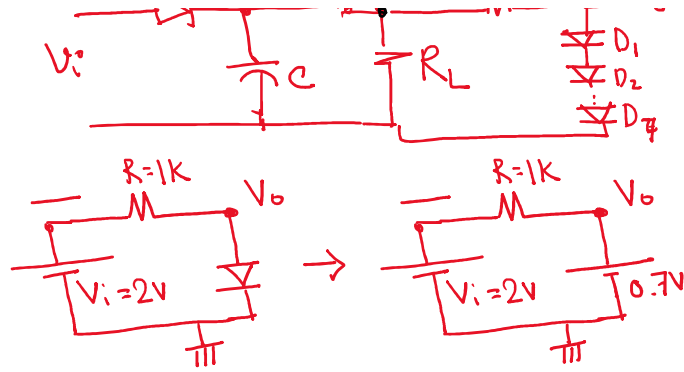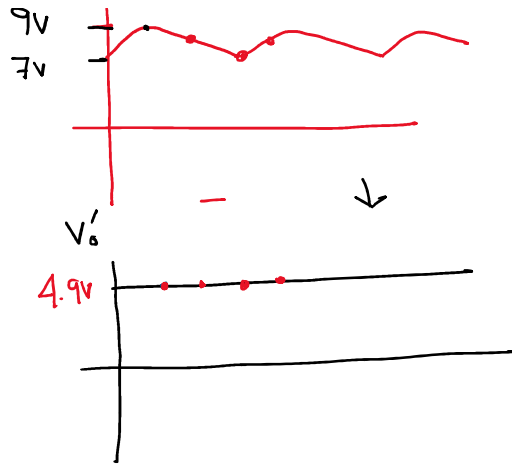

Zener diode

$V_Z = 5V$ (Breakdown Voltage)
R.B. $V_i > V_Z$

