

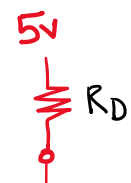
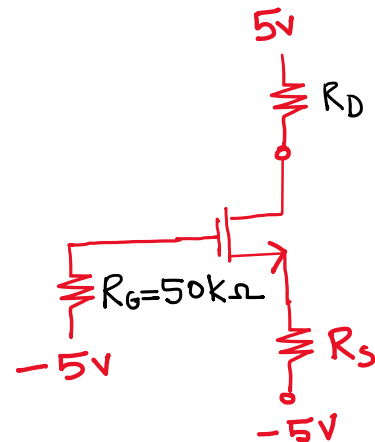
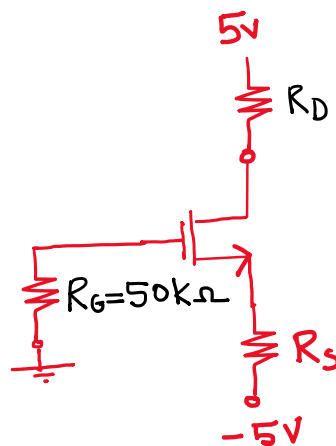
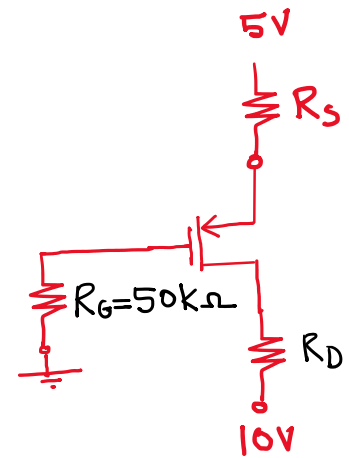
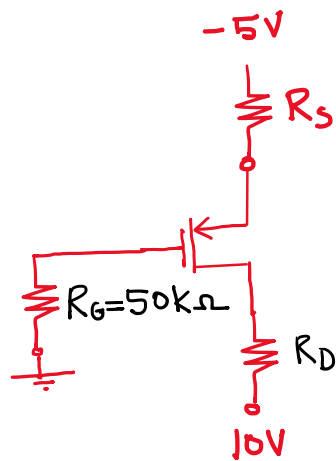
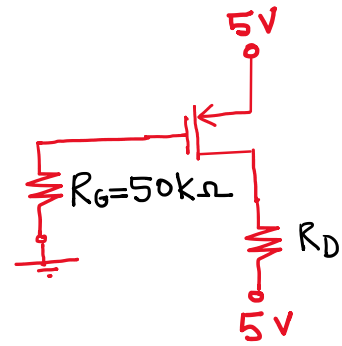
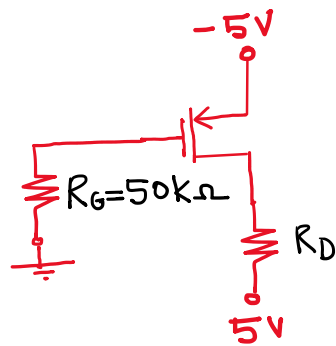
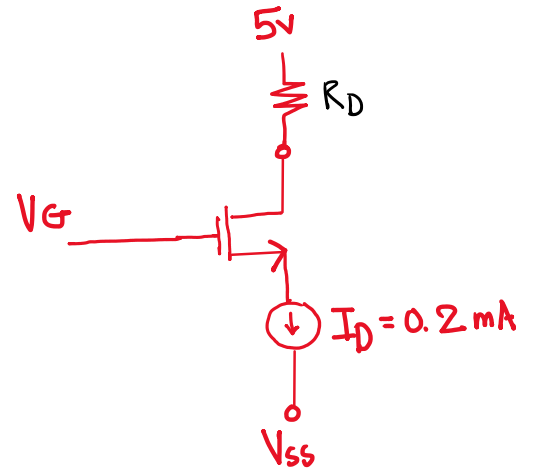
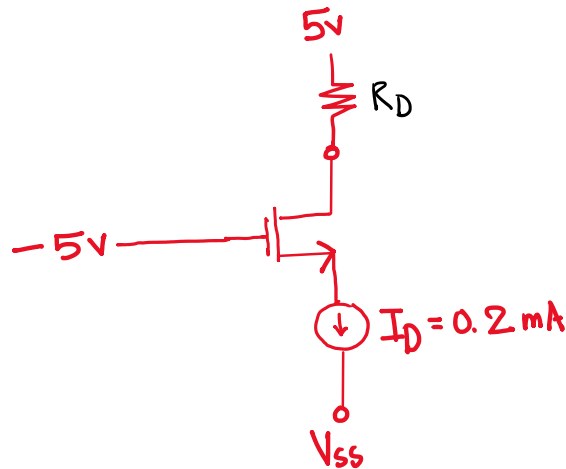


MOSFET Short Q

Wednesday, March 12, 2025 10:15 PM

For the MOSFETs in the circuits below determine if channels are induced or not. $|V_T| = 0.8V$

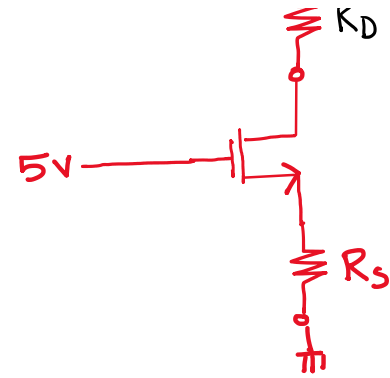

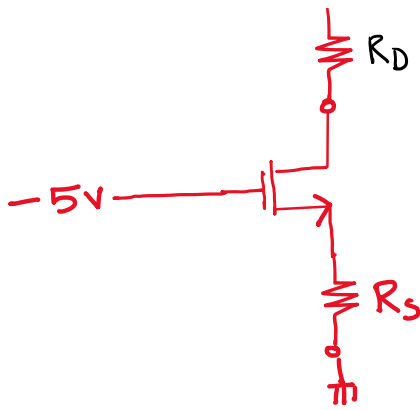

□ For each of the circuits above, state the terminal voltages that are known and identify the terminals whose voltages are not known.

□ For the MOSFETs given below determine the region of operations. $|V_T| = 0.6V$

