

Steps to follow while solving:

1. Check if channel is induced:

- If a current is shown to be flowing ($I_D \neq 0$) then channel is **definitely induced**.
- If $V_{GS} < V_{TN}$, **no channel is induced (NMOS)** → *Cut – off*
- If $V_{GS} > V_{TP}$, **no channel is induced (PMOS)** → *Cut – off*
- If gate terminal voltage is greater than source terminal voltage (even if there is a resistance connected between source terminal and the DC voltage source) by more than the threshold voltage, then channel is induced. (NMOS)
- If gate terminal voltage is smaller than source terminal voltage (even if there is a resistance connected between source terminal and the DC voltage source) by more than the threshold voltage, then channel is induced. (PMOS)

Steps to follow while solving:

2. check V_{GD} , If channel is induced, [to determine the region of operation]

- if V_{GD} can be measured directly, then find the region of operation.
 - For **NMOS**, $V_{GD} < V_{TN}$: *saturation*, $V_{GD} \geq V_{TN}$: *Triode*.
 - For **PMOS**, $V_{GD} > V_{TP}$: *saturation*, $V_{GD} \leq V_{TP}$: *Triode*.
- If V_{GD} cannot be determined directly (as there is resistor between drain terminal and the V_{DD} , for example), then go for **assumption**.
- Assume **saturation region/Triode**.
- Solve the circuit based on the assumption you have made, find I_D, V_D, V_S etc.
- **Justify** your assumption. For justification check V_{GD} ,
- if V_{GD} can be measured directly, then find the region of operation.
 - For **NMOS**, $V_{GD} < V_{TN}$: *saturation*, $V_{GD} \geq V_{TN}$: *Triode*.
 - For **PMOS**, $V_{GD} > V_{TP}$: *saturation*, $V_{GD} \leq V_{TP}$: *Triode*.
- Follow the problems solved in the class.

$k_n = 0.5 \text{ mA/V}^2$, $V_t = 0.8 \text{ V}$, Determine I_D , V_D , V_S . Determine the region of operation.


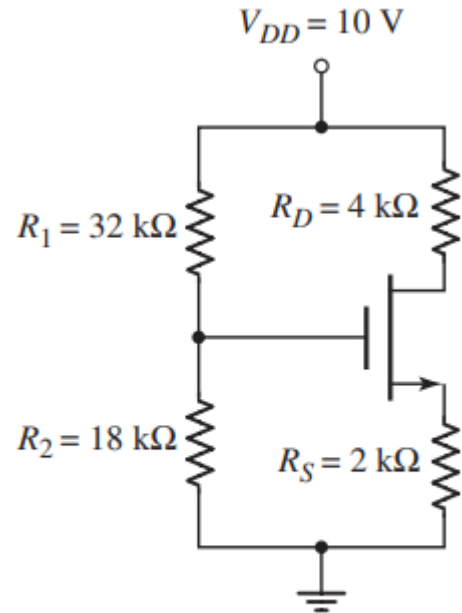


Figure P3.26

 

$V_{DD} = 5 \text{ V}$, $R_D = 5 \text{ k}\Omega$, $2 \text{ k}\Omega$, $10 \text{ k}\Omega$


 



Figure P3.34

$V_{GS} = 5 \text{ V}$

 

$k_n = 0.4 \text{ mA/V}^2$, $V_t = 1\text{V}$, Determine I_D , and the labeled voltages


Determine the region of operation

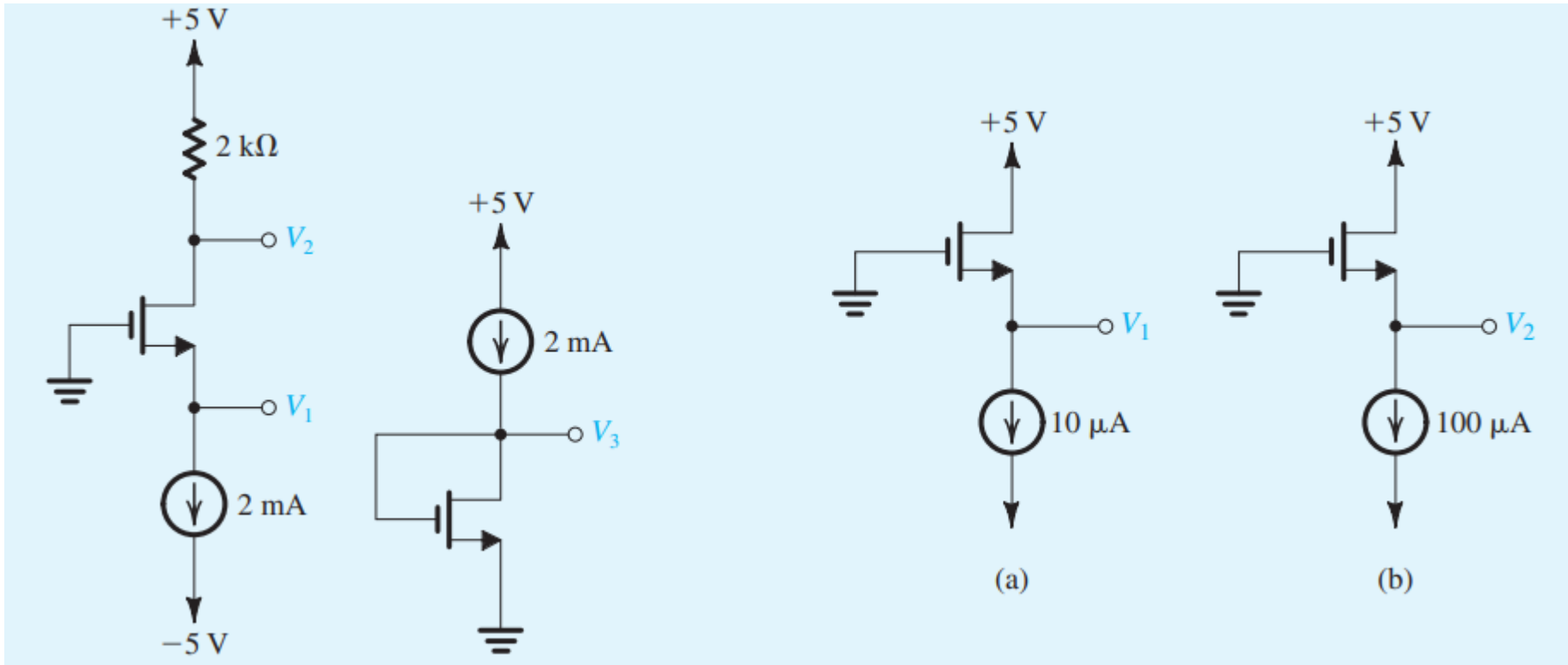


For the circuit (a) and (b), determine the labeled voltages.

$$k_p = 0.4 \text{ mA/V}^2, V_{tp} = -0.8 \text{ V}.$$


Determine the region of operation

 

(a)

 

(b)


 


If the transistor is specified to have $|V_{tp}| = 1 \text{ V}$ and $k_p = 0.2 \text{ mA/V}^2$, and for $I = 0.1 \text{ mA}$, find the voltages V_{SD} and V_{SG} for $R = 0, 10 \text{ k}\Omega, 30 \text{ k}\Omega$, and $100 \text{ k}\Omega$.

(c)

$k_n = 0.5 \text{ mA/V}^2$, $V_t = 0.8 \text{ V}$, Determine I_D , and the labeled voltages

Determine the region of operation

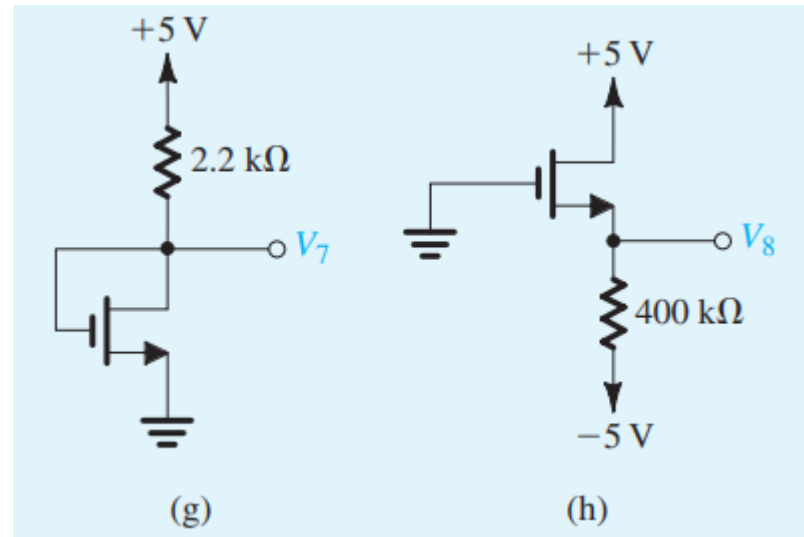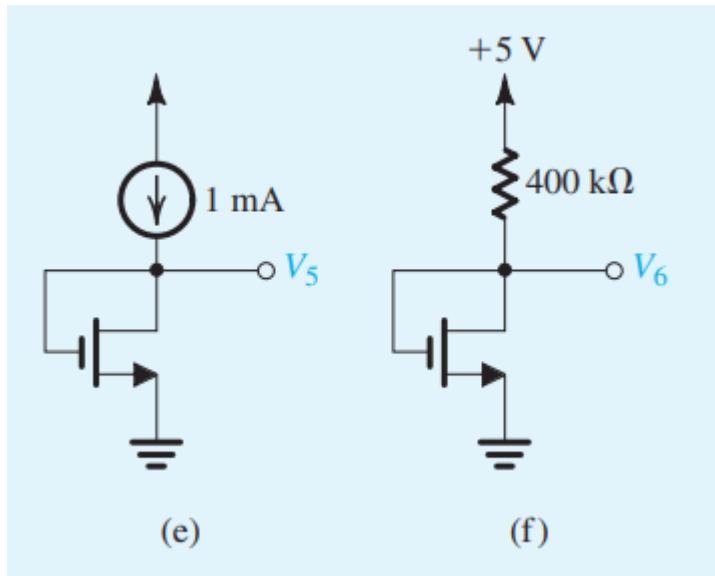

- 3.29 The transistor in the circuit in Figure P3.29 has parameters $V_{TP} = -0.8 \text{ V}$ and $K_p = 0.20 \text{ mA/V}^2$. Sketch the load line and plot the Q -point for (a) $V_{DD} = 3.5 \text{ V}$, $R_D = 1.2 \text{ k}\Omega$ and (b) $V_{DD} = 5 \text{ V}$, $R_D = 4 \text{ k}\Omega$. What is the operating bias region for each condition?
- 3.30 Consider the circuit in Figure P3.30. The transistor parameters are $V_{TP} = -0.8 \text{ V}$ and $K_p = 0.5 \text{ mA/V}^2$. Determine I_D , V_{SG} , and V_{SD} .

