

$$I_D = I_s \left[e^{\frac{V_D}{nV_T}} - 1 \right]$$

$$I_D = I_s \left[e^{\frac{V_D}{nV_T}} - 1 \right] : \text{diode equation}$$

I_D : Current through the diode

V_D : Voltage across the diode


I_s : Reverse saturation current (minority carrier current)

$V_T = \frac{kT}{e}$, k : Boltzmann's const
 e : charge of electron

$T = 300K$, $V_T \approx 25mV$ [thermal voltage]

n : Ideality factor; $1 \sim 2$ (Si)

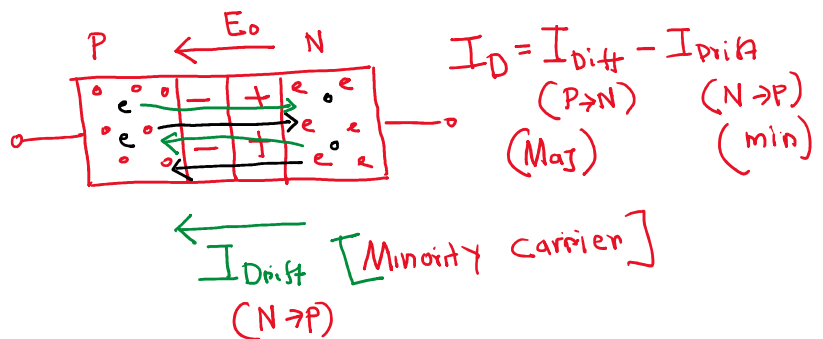$I_{D, \text{diff}} (P \rightarrow N)$ [Majority carrier]



$$I_s = I_{D, \text{drift}}$$

$$I_D = I_s \left[e^{\frac{V_D}{nV_T}} - 1 \right] = I_s e^{\frac{V_D}{nV_T}} - I_s$$

$I_D = I_{D, \text{diff}} (P \rightarrow N) - I_{D, \text{drift}} (N \rightarrow P)$

$\sim 10^{-3} A$ $\sim 10^{-10} A$ (nA - pA)

$$I_{D, \text{drift}} = I_s e^{\frac{V_D}{nV_T}}$$


$$I_{D, \text{diff}} = I_{Se}^{V_D/nV_T}$$

$$\sim 10^{-3} \text{ A}$$

$$\sim 10^{-10} \text{ (nA - pA)}$$

$$I_{D, \text{diff}} \gg I_{D, \text{diff}} (10^{6+1})$$

$$I_D \approx I_{Se}^{V_D/nV_T}$$

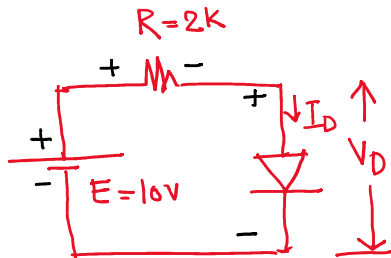

Unknowns/Variables: \$I_D\$ & \$V_D\$

Assume all the other parameters are known except \$I_D\$ & \$V_D\$

$$+E - I_D R - V_D = 0$$

$$I_D = \frac{E - V_D}{R} \quad \text{--- (I)}$$

$$I_D \approx I_{Se}^{V_D/nV_T} \quad \text{--- (II)}$$

Non-linear

$$I_{Se}^{\frac{V_D}{nV_T}} = \frac{E - V_D}{R} \quad \text{--- (III)}$$

linear - Trial & Error method

- IEEE 282 (Numerical technique)

$$V_D = 0.51\text{V}, 0.53\text{V}, 0.55\text{V}$$

Solution \$\rightarrow\$ [exact/Accuracy]

$$18.83$$

$$19.08$$

$$19.11$$

$$19.35$$

$$19.15$$

$$19.11$$

$$V_D = 0.25\text{V}$$

$$V_D = V_D + 0.001\text{V}$$

Simpler Way even we have to compromise on the accuracy.


find

- 1.13 PM \$\rightarrow\$ Slow/corrupt


- 1.15 PM \$\rightarrow\$ Fast/not accurate


$$1.52/$$

$$1.50$$

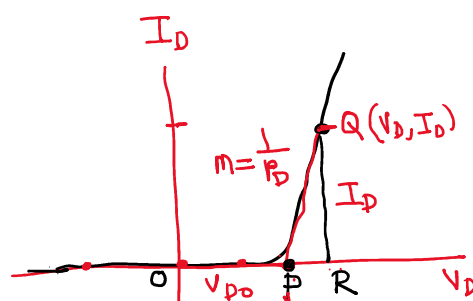

$$I_D = I_{Se}^{V_D/nV_T}$$

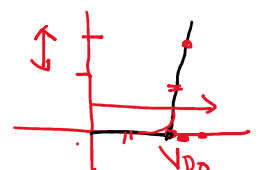

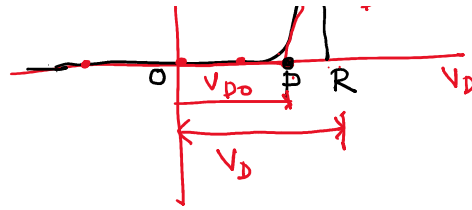


$$OR = OP + PR \quad \triangle PQR$$

$$V_D = V_{D0} + PR \quad m = \frac{1}{r_D} = \frac{QR}{PR}$$


$$V_D = V_{D0} + PR = V_{D0} + I_D r_D$$

$$\Rightarrow PR = QR \cdot r_D = I_D r_D$$
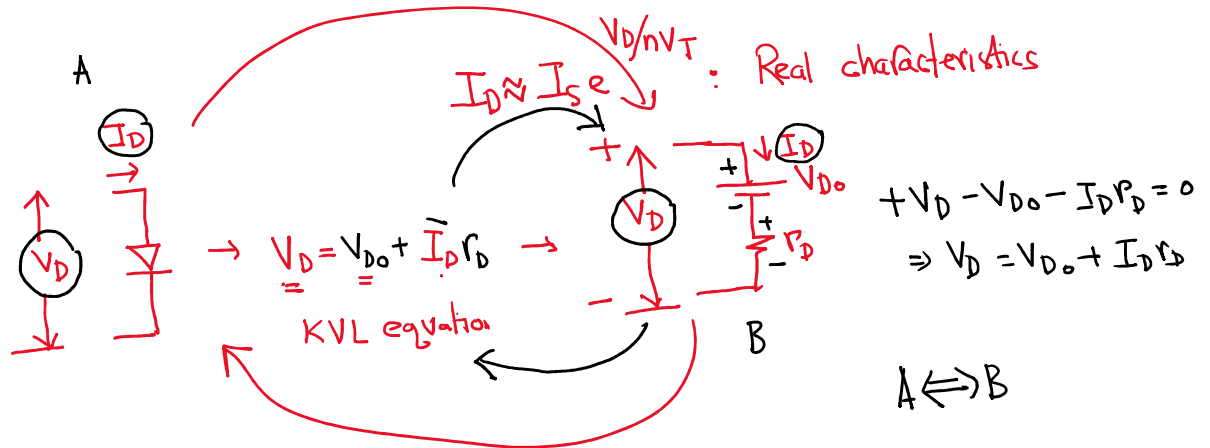
$$V_D = V_{D0} + I_D r_D \quad : \text{Approximation}$$




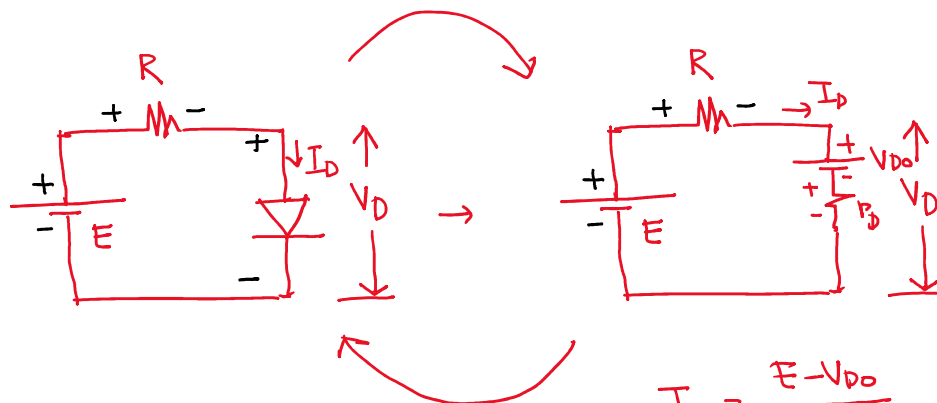
If two isolated systems have identical outwards behaviour, then they are said to be equivalent to each other.




$$I_D = \frac{E - V_{D0}}{R + r_D}$$


$$V_D = V_{D0} + I_D r_D$$

$$r_D : 10 - 20 \Omega \ll R = 2k$$

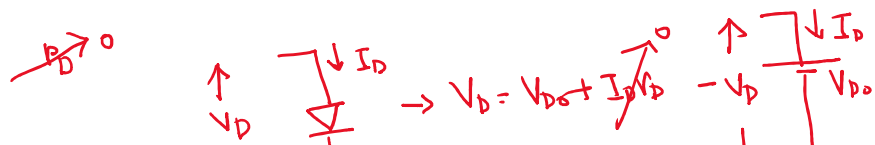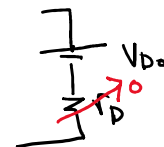


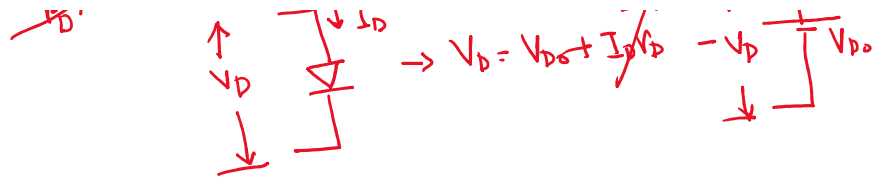

Constant voltage drop model/Approx.

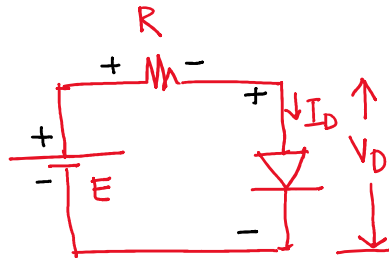


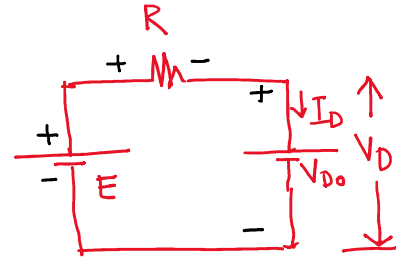
$$V_D = V_{D0} = 0.7V \text{ (Si)} \\ = 0.3V \text{ (Ge)}$$



$$I_D = \frac{E - V_{D0}}{R}$$

③ Ideal diode model.

$$V_D = V_{D0} + I_D r_D$$
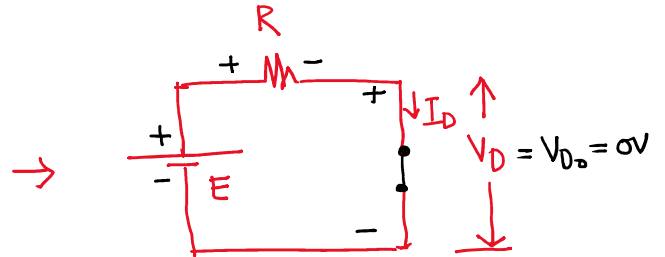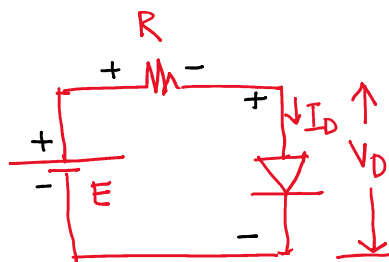
$$V_D = V_{D0} = 0V$$


F.B

$$I_D = \frac{E - V_{D0}}{R + r_D}$$


$$I_D = \frac{E - V_{D0}}{R}$$

$$I_D = \frac{E}{R}$$


I_D

$$I_D = \frac{E}{R}$$

$$I_D = \frac{E}{R}$$

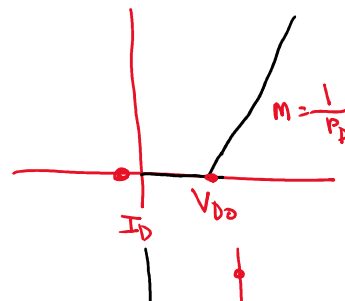

$$r_D = 0, m = \frac{1}{r_D} = \infty$$

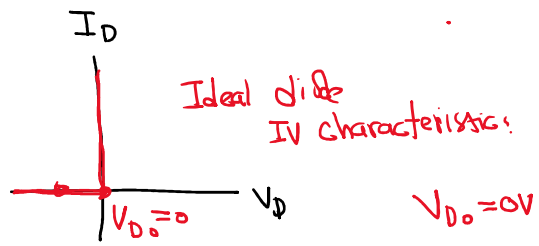

$$V_{D0} = 0V$$

R.B \rightarrow diode OFF

