

Department of Electrical & Electrical Engineering
BRAC University
Semester- Fall 2025



EEE205L

ELECTRONIC CIRCUITS I LABORATORY

Section: 01

Experiment:6 - BJT BIASING

Group Number: 1

Group Members:

SL	Student ID	Name
01.	24121204	Abir Chowdhury Ratul
02.	24121076	Tashin Ahmed Sakib
03.	24121308	Alif Tamjid
04.	24121205	Souvik Barman Ratul
05.	24121058	Muhammad Mushfiqur Rahman

Submitted by :

Submitted To : Aldrin Nippon Bobby

Name : Abir Chowdhury Ratul

Aldrin Nippon Bobby

ID : 24121204

Objective:

To study the common emitter amplifier and measure its gain,
input impedance and output impedance.

Equipments:

1. Breadboard
2. Jumper wires
3. Multimeter
4. n-p-n Transistor (C828, BD135)
5. 100k Potentiometer
6. Resistors (470Ω , 560Ω , $10k\Omega$, $220k\Omega$)
7. DC Voltage Source

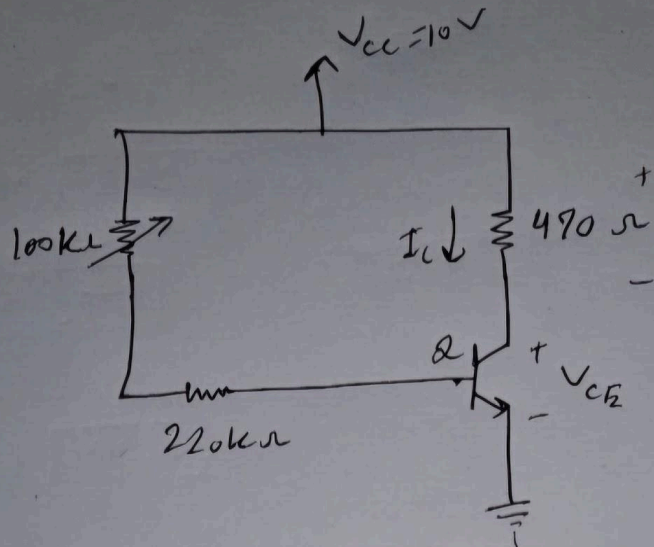


Fig: Fixed - bias .

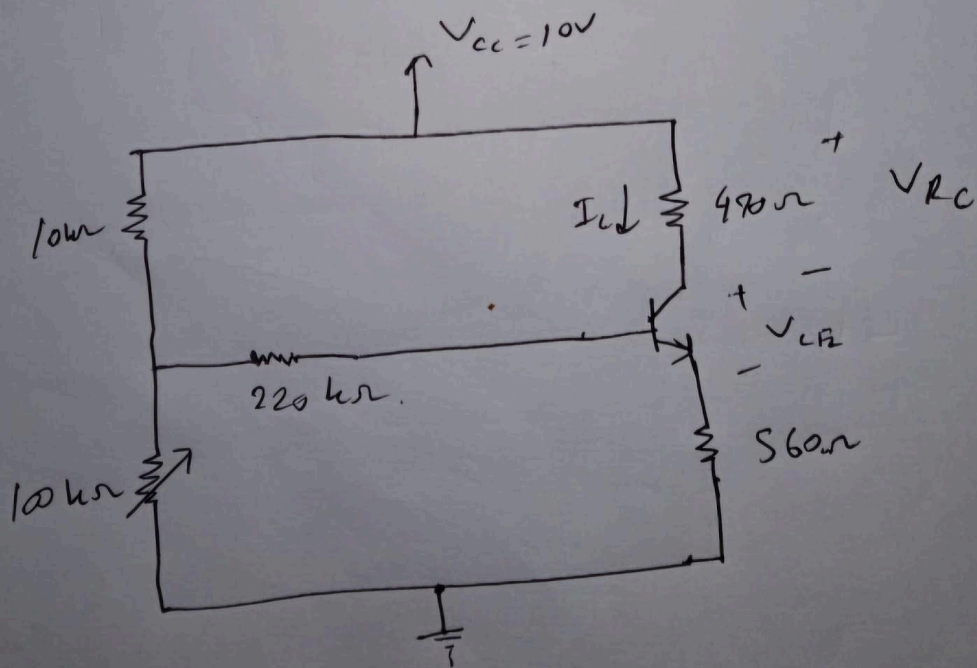


Fig: self - bias

→ Fixed - Bias data

$R_3(\Omega)$	BJT	$V_{CE}(V)$	$V_{R_3}(V)$	$I_C = \frac{V_{R_3}}{R_3}$ (mA)	ΔV_{CE} (V)	ΔI (mA)
470	BD135	6.37	3.76	8	1.90	4.00
	C828	4.56	5.66	12.04		


→ Self - Bias data

$R_4(\Omega)$	BJT	$V_{CE}(V)$	$V_{R_4}(V)$	$I_C = \frac{V_{R_4}}{R_4}$ (mA)	ΔV_{CE} (V)	ΔI_C (mA)
470	BD135	7.45	1.44	3.064	1.44	0.979
	C828	6.01	1.90	4.040		

Experiment 6 BJT Biasing.

Group: 01


Fixed Bias.

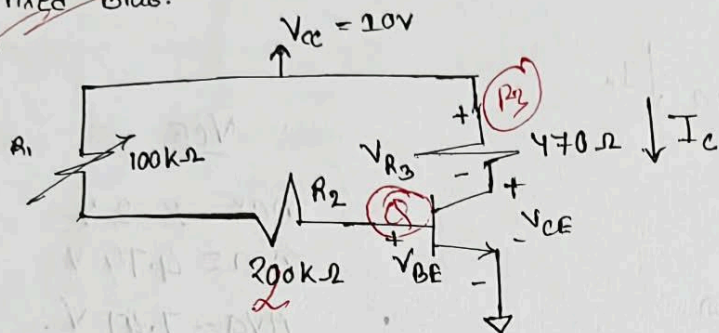

V_{CE}
 $\max = 7.11V$
 $\min = 5.63V$
 $Avg = 6.37V$

$R_1 (\Omega)$	BJT.	$V_{CE} (V)$	$V_{R_3} (V)$	$I_C = \frac{V_{R_3}}{R_3}$ (mA)	ΔV_{CE} (V)	ΔI_C (mA)
470	BD135 C828	6.37 4.56	8 3.76 5.66	8 12.04	1.9	4.0

Self Bias

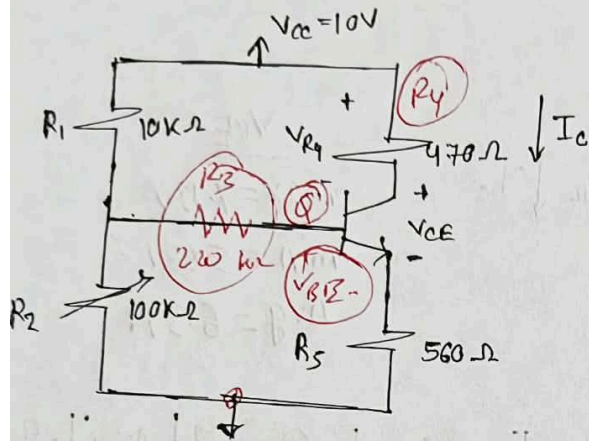

V_{CE}

$$\text{max} = 10.2 \text{ V}$$

$$\text{min} = 4.74 \text{ V}$$

$$\text{Avg} = 7.47 \text{ V}$$

R_4 (Ω)	BJT	V_{CE} (V)	V_{R4} (V)	$I_C = \frac{V_{R4}}{R_4}$ (mA)	ΔV_{CE} (V)	ΔI_C (mA)
470 Ω	BD135	7.45	1.44	3.064		
	C828	6.01	1.9	4.04	1.44	0.979


ack.

$$V_{CE} \rightarrow 0.5V - 0.7V$$

2) Gradual change in V_{CE} .

④ Terminal Configuration.

~~PNP~~ \rightarrow BD135.

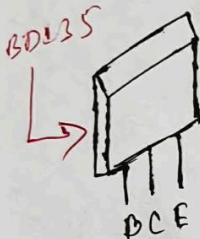

$\frac{9}{10}$

Alto

2015 - December - 11

