

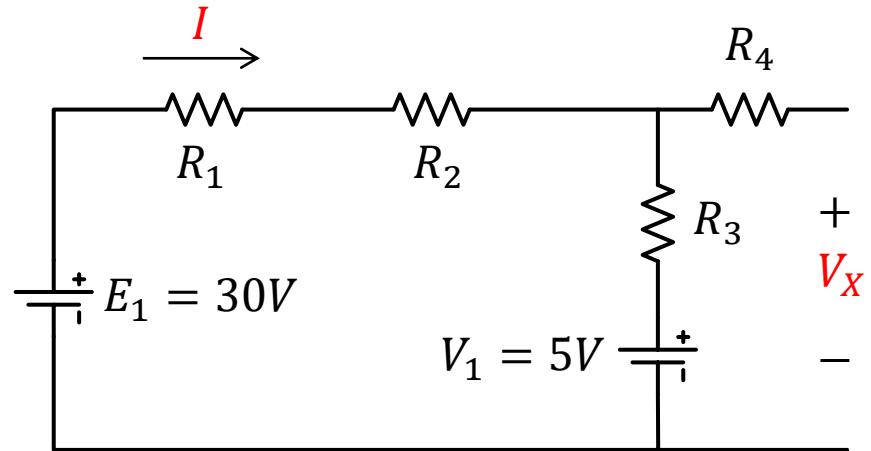


Review: Concepts of DC Circuit Analysis.



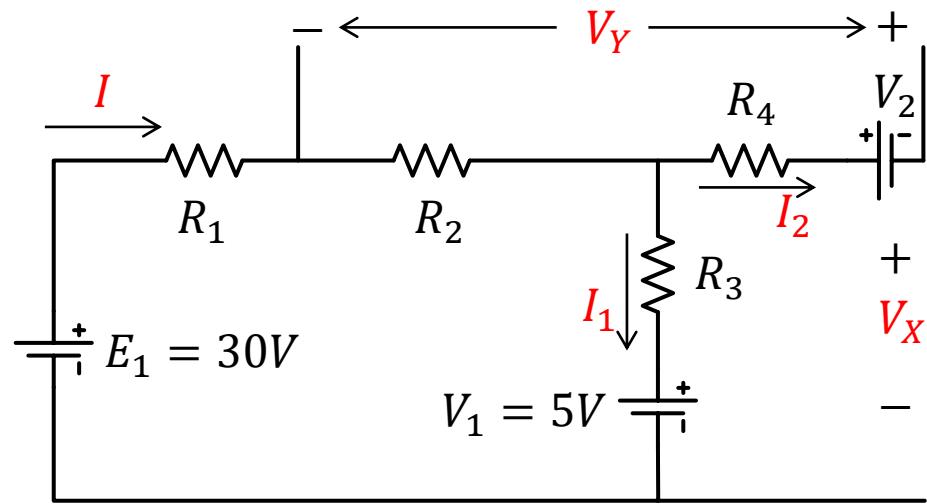


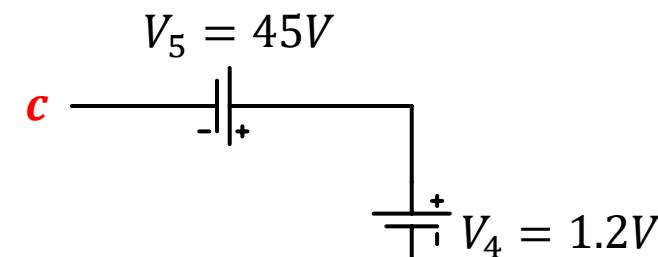Using KVL, KCL, ohm's law, determine the labelled currents and the voltages in the following circuits. $R_1 = 10\Omega$, $R_2 = 20\Omega$, $R_3 = R_4 = 15\Omega$, $V_2 = 10V$.





Find V_{ab} and V_{cb}

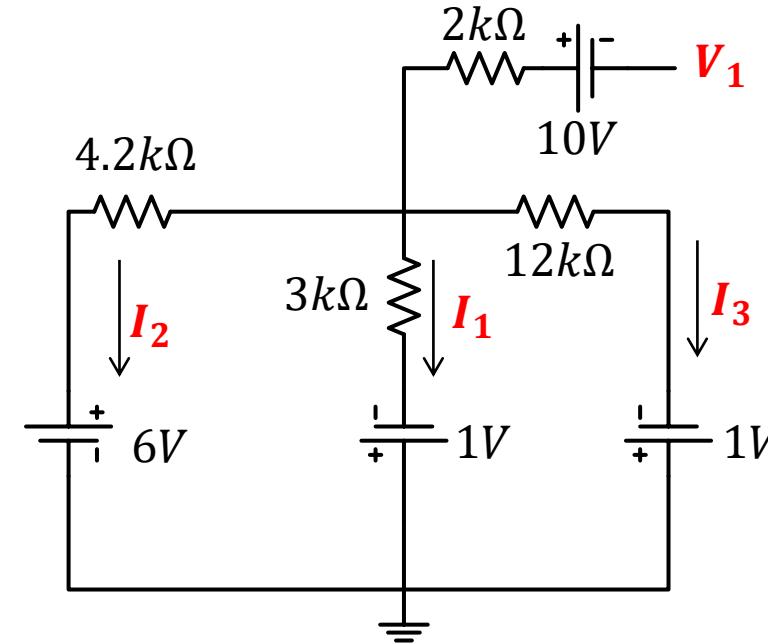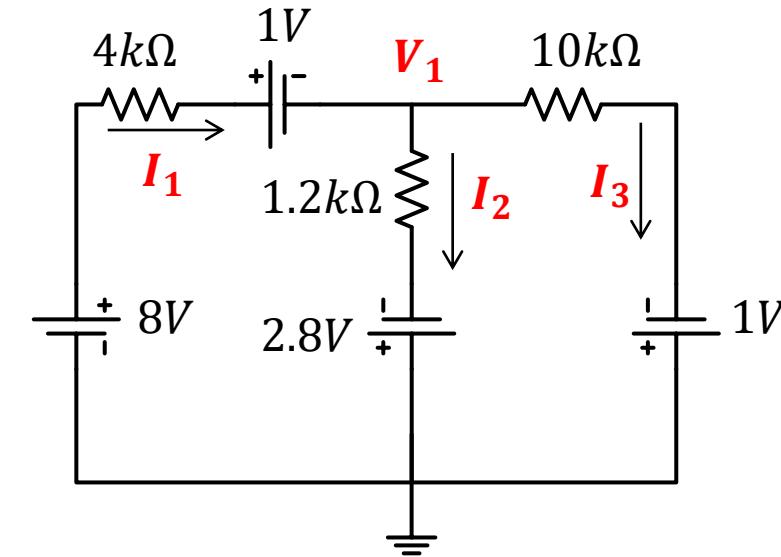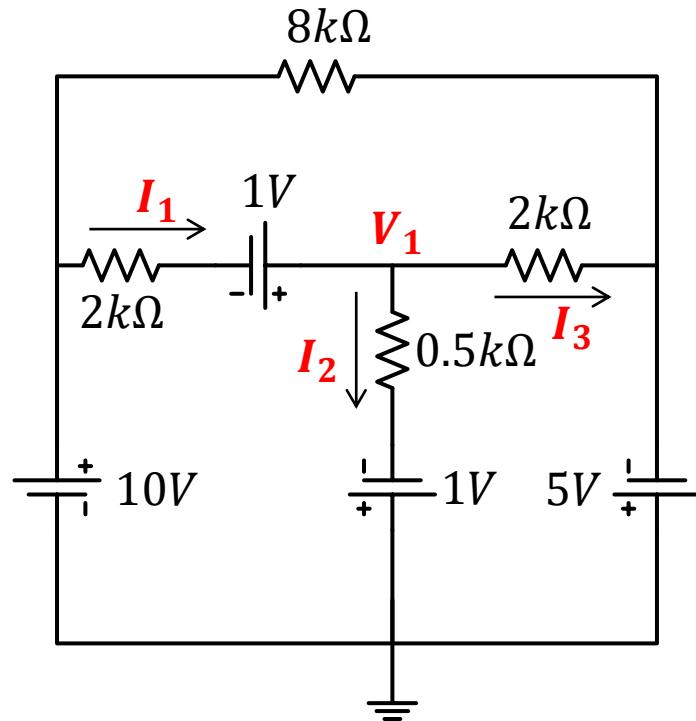
Employing **Mesh Analysis & Node Analysis**, determine the labelled currents and the node voltage of the circuits shown in figure below.



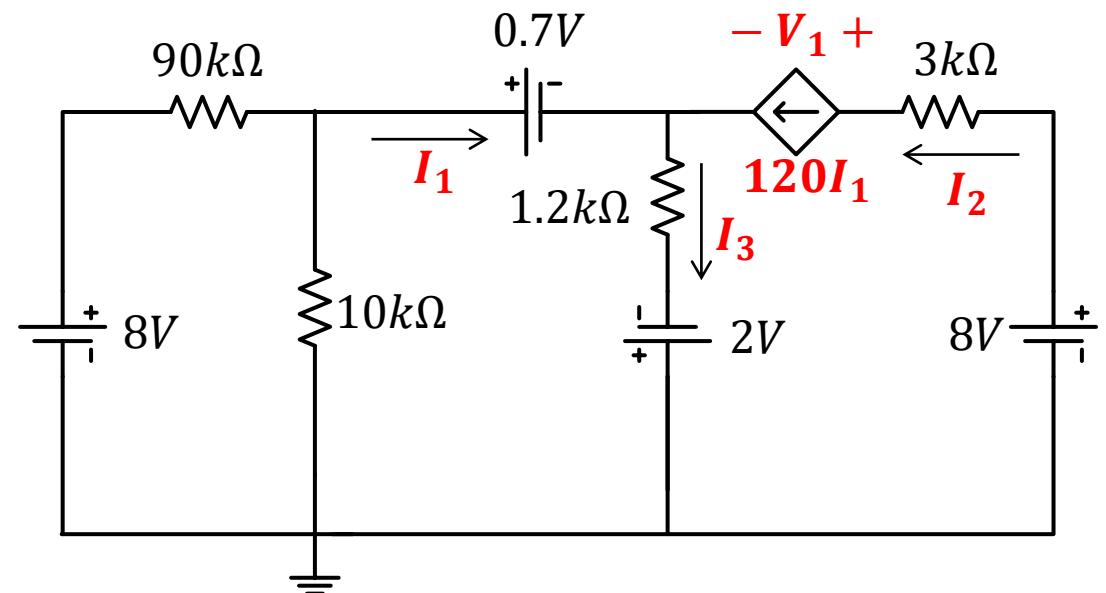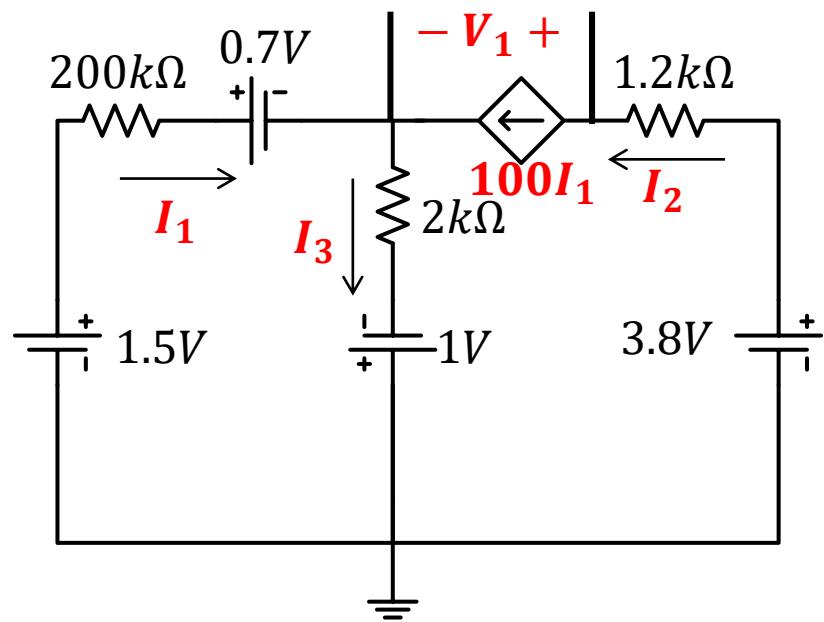Determine the labelled currents and the node voltage of the circuits shown in figure below.



Determine V_{Th} & R_{TH} between $A - A'$

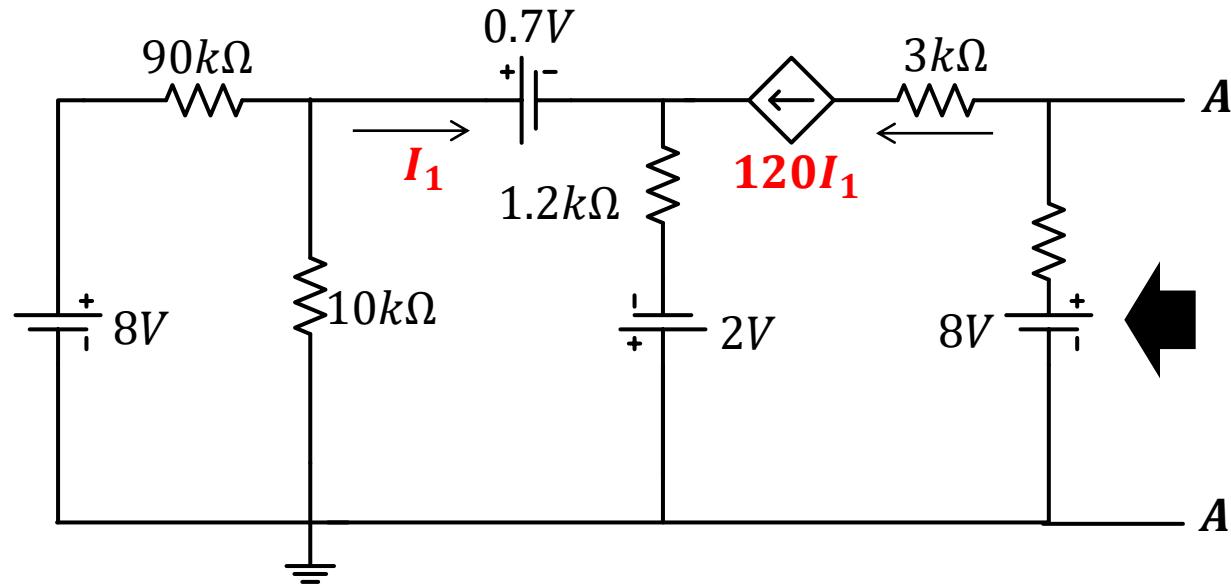

EEE205


HW - 1

Name: Souvik Barman Ratna.

ID: 24121205

Section: 04

Q1(a)

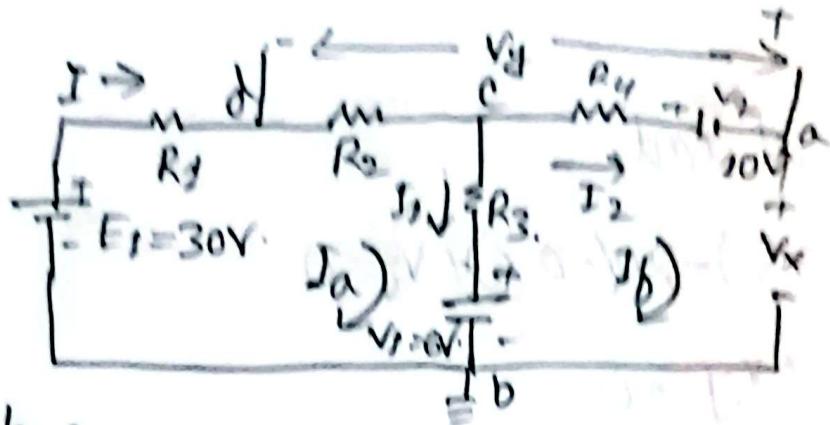

For mesh-a,

$$30 - 10J_a - 20J_a - 15J_a + 15J_b - 5 = 0$$

$$\Rightarrow -45J_a + 15J_b + 25 = 0$$

$$\Rightarrow 45J_a - 15J_b - 25 = 0 \dots \textcircled{i}$$

For mesh-b,

$$\Rightarrow 5 - R_3(J_b - J_a) - R_4 J_b - 10 = 0$$

$$\Rightarrow 5 - 15J_b + 15J_a - 15J_b + 10 = 0$$

$$\Rightarrow 30J_b - 15J_a + 5 = 0 \dots \textcircled{ii}$$

From \textcircled{i} , \textcircled{ii} ,

$$J_a = -2A, \quad J_b = -4.33A.$$

$$\left. \begin{aligned} J_1 &= J_a - J_b = 2.33A. \\ J_2 &= J_b = -4.33A. \end{aligned} \right\} \text{Ans}$$

again,

Applying KVL at abc,

$$\Rightarrow 5 - 15(-0.467) - 15(0.133) - 10 = V_x.$$

$$\therefore V_x = 0.01V. \text{ Ans}$$

again,

Applying KVL at acd ,

$$10 - 15(-0.133) - 20(-0.6) + V_y = 0$$


$$\Rightarrow 23.995 + V_y = 0$$

$$\therefore V_y = -23.995 \text{ V} \quad \underline{\text{Ans}}$$

$$P = ZS + dI_Z$$

$$\textcircled{1} \cdot 0 = ZS - P$$

11 b)

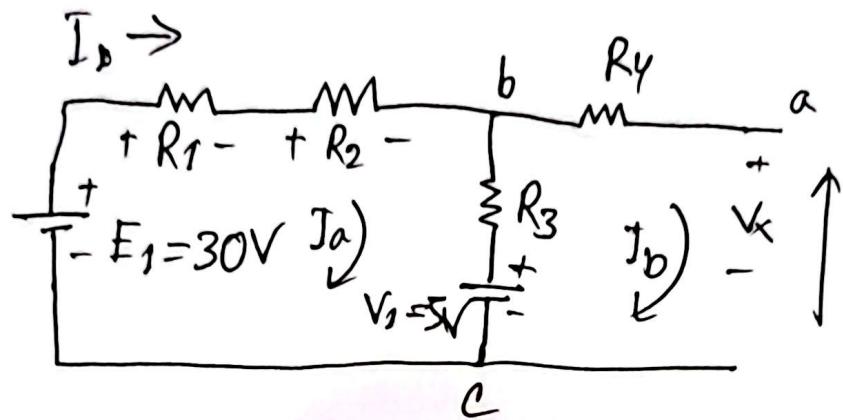

Applying KVL at loop-a,

$$E_1 - V_{R_1} - V_{R_2} - R_3(I_a - I_b) - V_x = 0$$

$$\Rightarrow E_1 - I_a R_1 - I_a R_2 - I_a R_3 + I_b R_3 - V_x = 0$$

$$\Rightarrow 30 - 10I_a - 20I_a - 15I_a + 15I_b - 5 = 0$$

$$\Rightarrow -45I_a + 15I_b + 25 = 0$$

$$\Rightarrow 45I_a - 15I_b = 25 \dots \textcircled{i}$$

Applying KVL at loop-b,

$$+V_x - V_{R_3} - V_{R_4} = 0$$

$$\Rightarrow 5 - I_b R_3 + I_a R_3 - I_b R_4 = 0$$

$$\Rightarrow 5 - 15I_b + 15I_a - 15I_b = 0$$

$$\Rightarrow 15I_a - 30I_b = -5 \dots \textcircled{ii}$$

from \textcircled{i}, \textcircled{ii},

$$I_a = 0.733 A$$

$$I_b = 0.533 A.$$

$$I_a - I_b = 0.2 A$$

Applying KVL in abc


$$V_x + V_{R_4} + V_{R_3} - V_x = 0$$

$$\Rightarrow V_x + 15(-0.533) + 15(0.2) - 5 = 0$$

$$\Rightarrow V_x - 9.995 = 0$$

$$V_x = 9.995 V$$

Ans

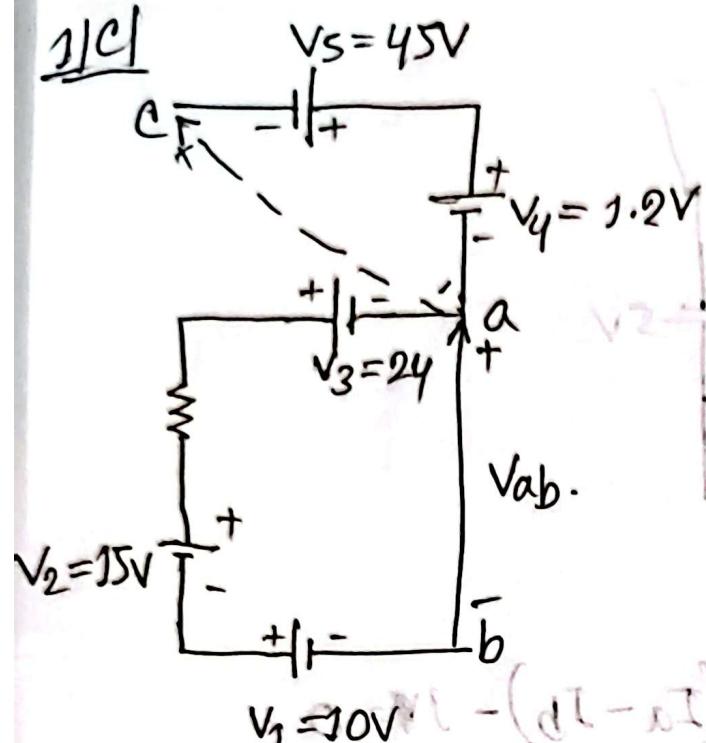

$$\begin{aligned}R_1 &= 10\Omega \\R_2 &= 20\Omega \\R_3 &= R_{CF} 15\Omega \\V_2 &= 10V.\end{aligned}$$

~~KVL~~. Applying KVL

$$V_1 + V_2 - V_3 - V_{ab} = 0$$

$$\sqrt{ab} = \sqrt{1} + \sqrt{2} - \sqrt{3}$$

$$0 = 2 = 10 + 15 - 2$$

$$0 = z - \overline{z} \text{cis } -\alpha$$

$$0 = 2 - 0.8 - \cancel{A_m} + 0.820 = 1.2 + 0.8$$

Applying KVL

$$V_{AC} + V_5 - V_4 = 0$$

$$\Rightarrow v_{ac} = v_4 - v_5.$$


$$\Rightarrow \text{vac} = 1.2 - 4.5$$

$$\Rightarrow V_{AC} = 1.2 - 45\sin(\omega t) + 1 + (41 - 9t)\cos(\omega t) + 9\sqrt{12}$$

$$\Rightarrow V_{\text{ac}} = -43.8 \text{ mV}$$

Verbal

2) a)

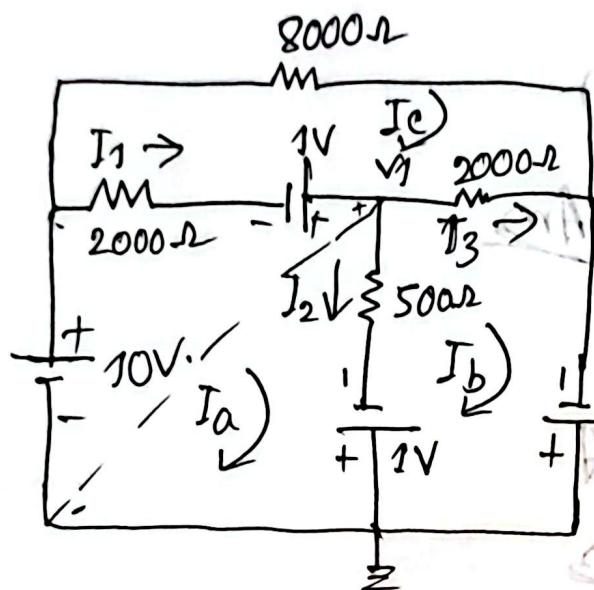

For mesh A,

$$-10 + 2000I_a - 2000I_c - 1 + 500I_a - 500I_b - 1 = 0$$

$$\Rightarrow 2500I_a - 500I_b - 2000I_c = 12 \dots \textcircled{i}$$

For mesh B,

$$1 + 500I_b - 500I_a + 2000I_b - 2000I_c - 5 = 0$$

$$\Rightarrow -500I_a + 2500I_b - 2000I_c = 4$$

$$\Rightarrow 500I_a - 2500I_b + 2000I_c = -4 \dots \textcircled{ii}$$

For mesh C,

$$8000I_c + 2000I_c - 2000I_b + 1 + 2000I_c - 2000I_a = 0$$

$$\Rightarrow -2000I_a - 2000I_b + 12000I_c = -1 \dots$$

$$\Rightarrow 2000I_a + 2000I_b - 12000I_c = 1 \dots \textcircled{iii}$$

from $\textcircled{i}, \textcircled{ii}, \textcircled{iii}, \Rightarrow$

$$I_a = 7.21A \quad I_b = 4.54A \quad I_c = 1.88A$$

Here

$$\begin{aligned} I_1 &= I_c - I_a \\ &= (1.88 - 7.21) \\ &= -5.33 A \quad \underline{\text{Ans}} \end{aligned}$$

$$\begin{aligned} I_2 &= I_a - I_b \\ &= (7.21 - 4.54) A \\ &= 2.67 A \quad \underline{\text{Ans}} \end{aligned}$$

$$\begin{aligned} I_3 &= I_b - I_c \\ &= (4.54 - 1.88) \\ &= 2.66 A \quad \underline{\text{Ans}} \end{aligned}$$

for V_1 ,


$$\begin{aligned} 0 &= 1 - 500V_2 - V_1 = 0 \\ -1 - 500V_2 - V_1 &= 0 \\ -1 - 500I_2 - V_1 &= 0 \\ -1 - 500(2.67) - V_1 &= 0 \quad \underline{\text{Ans}} \end{aligned}$$

$$0 = 1 - 500V_1 - 5(0008) + 5(0002) - 5(0008) + 5(0008) +$$
$$V_1 = -1336 V \quad \underline{\text{Ans}}$$

(III) $\rightarrow I = 5(0008) - 5(0008) +$

$$0.22 A = 0.1 A \quad 1.62 A = 1.7 W \text{ Ans}$$

Q2(b)

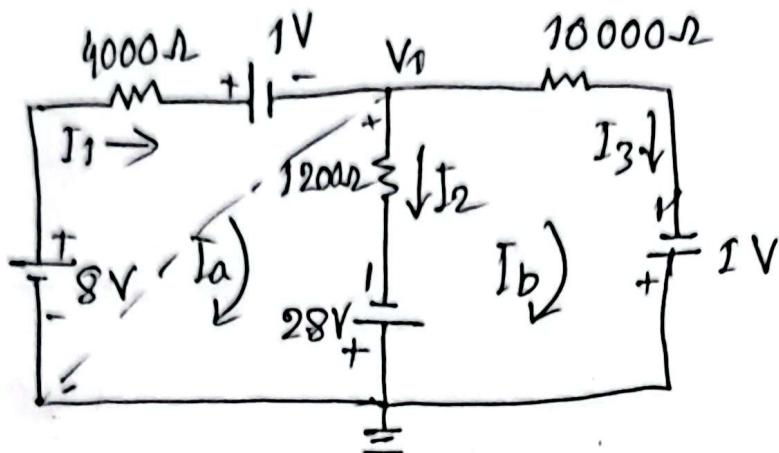

For mesh-a,

$$-8 + 4000I_a + 1 + 1200I_a - 1200I_b - 28 = 0$$

$$\Rightarrow 5200I_a - 1200I_b = 35 \dots \textcircled{i}$$

For mesh-b,

~~$$28 + 1200I_b - 1200I_a + 10000I_b - 1 = 0$$~~

$$\Rightarrow -1200I_a + 11200I_b = -27$$

$$\Rightarrow 1200I_a - 11200I_b = 27 \dots \textcircled{ii}$$

from \textcircled{i}, \textcircled{ii},

$$I_a = 6.33A, \quad I_b = -1.73A$$

$$I_1 = I_a = 6.33A$$

$$I_2 = I_b - I_a = -1.73 - 6.33 = -8.06A$$

$$I_3 = I_b = -1.73A$$


For V_1 ,

$$-28 - 1200V - V_1 = 0$$

$$\Rightarrow -28 - 1200I_2 = V_1$$

$$\begin{aligned} V_1 &= -28 - 1200(-8.06) \\ &= -28 + 9672 \\ &= 9644V \text{ Ans} \end{aligned}$$

20C

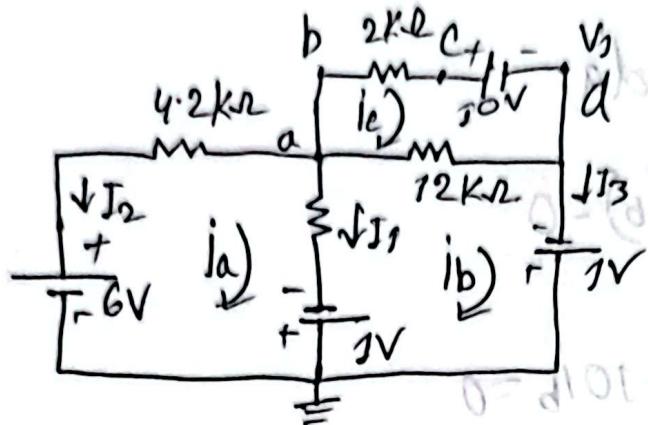

For mesh-a,

$$-6 + 4.2i_a + 3i_a - 3i_b - 1 = 0 \quad \text{Eqn. 1}$$

$$\Rightarrow 7.2i_a - 3i_b = 7 \quad \text{Eqn. 1(i)}$$

For mesh-b,

$$1 + 3i_b - 3i_a + 12i_b - 12i_c - 1 = 0 \quad \text{Eqn. 2}$$

$$\Rightarrow i_a - 15i_b + 12i_c = 0 \quad \text{Eqn. 2(ii)}$$

For mesh c,

$$12(i_c - i_b) + 2i_c + 10 = 0$$

$$\Rightarrow 12i_c - 12i_b + 2i_c + 10 = 0$$

$$\Rightarrow -12i_b + 14i_c = -10$$

$$\Rightarrow 12i_b - 14i_c = 10 \quad \text{Eqn. 3(iii)}$$

from, (i), (ii), (iii),

$$i_a = 0.24 \text{ mA}, \quad i_b = -0.77 \text{ mA}, \quad i_c = -2.23 \text{ mA}.$$

$$\therefore I_2 = -i_a = 0.24 \text{ mA.}$$

$$I_1 = (i_b - i_a) = (-0.77 - 0.24) = -1.01 \text{ mA}$$

$$I_3 = i_b = -0.77 \text{ mA.}$$

Ans

Applying KVL at abceda;

$$2i_c + 10 - V_1 + 10(i_c - i_b) = 0$$

$$\Rightarrow V_1 = 10 + 10i_c - 10i_b$$

$$\Rightarrow 2i_c + 10 - V_1 + 10i_c - 10i_b = 0$$

$$\Rightarrow -10i_b + 12i_c - V_1 = -10$$

$$\Rightarrow -V_1 = -10 + 10i_b - 12i_c \quad (i)$$

$$\Rightarrow V_1 = 10 - 10(-1.77) - 12(-2.23)$$

$$= 10 + 17.7 + 26.73$$

$$= 54.43 \text{ V} \quad \underline{\text{Ans}}$$

$$0 = 0 + j180 + (j)$$


$$0 = 0 + j180 + j180$$

$$0 = 0 + j180 + j180$$

$$(iii) \quad 0 = j180$$

$$.180 \times 8.8 = j180 \times 8.8 = j180$$

3(a)

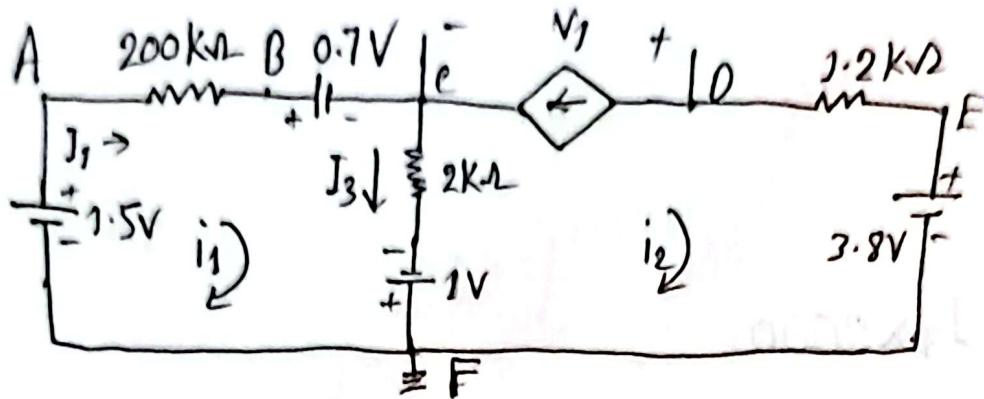

For mesh-1,

$$-1.5 + 200000i_1 + 0.7 + 2000(i_1 - i_2) - 2 = 0 \\ \Rightarrow 202000i_1 - 2000i_2 = 1.8 \quad \text{--- (i)}$$

again,

$$i_2 = -100i_1 = -100i_1 \quad [i_2 = i_1]$$

(i) -->

$$202000i_1 - 2000 \times (-100)i_1 = 1.8$$

$$\Rightarrow 402000i_1 = 1.8$$

$$i_1 = 4.478 \times 10^{-6} \text{ A}$$

$$\therefore i_2 = -100 \times i_1 = -4.478 \times 10^{-4} \text{ A.}$$

$$\therefore I_1 = i_1 = 4.478 \times 10^{-6} \text{ A}, \quad I_2 = -i_2 = 4.478 \times 10^{-4} \text{ A.}$$

$$\therefore I_3 = i_1 - i_2 = (4.478 \times 10^{-6} + 4.478 \times 10^{-4}) = 4.5258 \times 10^{-3}$$

$$\text{For } 1.2 \text{ k}\Omega, \quad V_E - V_D = I_2 \times 1.2 \times 1000$$

$$\Rightarrow V_E - V_D = I_2 \times 1.2 \times 1000$$

$$\Rightarrow V_D = -0.53736 \times 3.8 = 3.26 \text{ V}$$

ECE208

For $2k\Omega$,

$$V_C - V_G = I_3 \times 2000$$

$$\Rightarrow V_C - V_G = (4.5258 \times 10^{-3}) \times 2000$$

$$V_C = 1.90456V.$$

$$\therefore V_I = V_D - V_C$$

$$= (3.26 - 1.90456) V$$

$$= 1.356 V$$

$$I_1 = 4.78 \times 10^{-6} A$$

$$I_2 = 4.478 \times 10^{-4} A$$

$$I_3 = 4.5258 \times 10^{-3} A$$

Ans


Ans

Ans

$A^P - 0.1 \times 85 P.P.$

$A^P - 0.1 \times 85 H.P. = 81.5 - 81.5$

3(b)

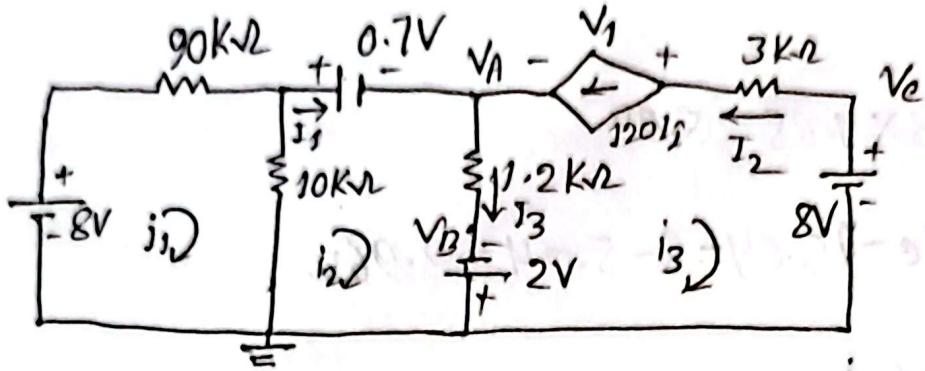

For mesh 1,

$$-8 + 90i_1 + 10(i_1 - i_2) = 0 \\ \Rightarrow 100i_1 - 10i_2 = 8 \dots \textcircled{i}$$

For mesh-2,

$$10(i_2 - i_3) + 0.7 + 1.2(i_2 - i_3) - 2 = 0$$

$$\Rightarrow -10i_1 + 11.2i_2 - 1.2i_3 = 1.3$$

$$\Rightarrow -10i_1 + 11.2i_2 - 1.2(-120i_2) = 1.3$$

$$\Rightarrow -10i_1 + 155.2i_2 = 1.3 \dots \textcircled{ii}$$

From, \textcircled{i} and \textcircled{ii} ,

$$i_2 = 0.08 \text{ mA}, \quad i_2 = 0.014 \text{ mA}.$$

$$I_1 = i_2 = 0.014 \text{ mA}, \quad I_2 = -i_3 = 120i_2 = 1.68 \text{ mA}$$

$$I_3 = I_1 + I_2 = 1.694 \text{ mA}$$

$$\text{For } 1.2 \text{ k}\Omega, \quad v_A - v_B = 1.2 \times 1.694 = 2.0328 \text{ V.}$$

$$\Rightarrow v_A = 2.0328 + v_B$$

$$= 2.0328 + 2$$

$$= 4.0328 \text{ V}$$

$$i_3 = -120i_2$$

$$= -120i_2$$

$$8820.4 - 8820.4 = 0$$

$$v_{AB} = ?$$

$$100 \times 0.0 = 0 \text{ V}$$

$$100 \times 0.1 = 10 \text{ V}$$

$$100 \times 0.2 = 20 \text{ V}$$

FET, 3KΩ

$$V_C - V_D = 3 \times 1.68 = 5.04$$

$$\Rightarrow V_D = V_C - 5.04 = 8 - 5.04 = 2.96 \text{ V.}$$

$$\therefore V_I = V_D - V_A$$

$$= 2.96 - 4.0328$$

$$= -1.07 \text{ V}$$

$$I_1 = 0.014 \text{ mA.}$$

$$I_2 = 1.68 \text{ mA}$$


$$I_3 = 1.694 \text{ mA}$$

$$f_{m3} = (s_1 - s_1) R$$

$$\varepsilon \cdot t = \varepsilon_1 s$$

$$\varepsilon \cdot t = (s_1 \delta s t -)$$

41

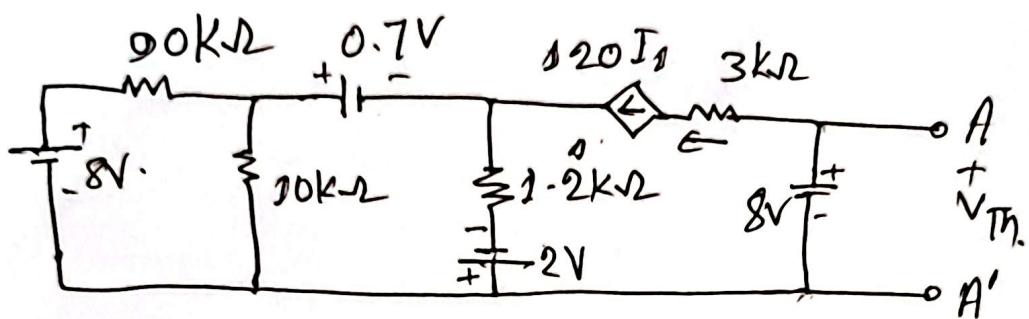


~~V_{Th}~~


Hence 8V DC source parallelly connected in reference node to ground. for this reason,

$$V_{Th} = V_{OC} = 8V$$

R_{Th}

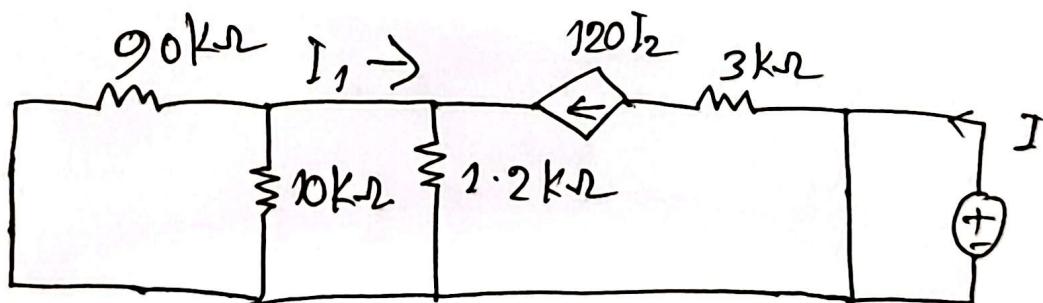

$$R_{Th} = 0\Omega$$

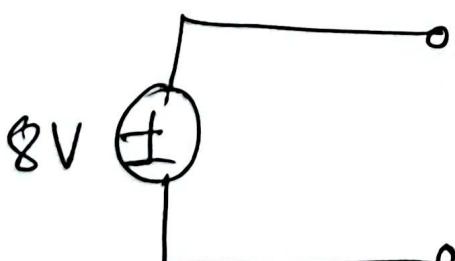

Thevenin
equivalent
circuit.