
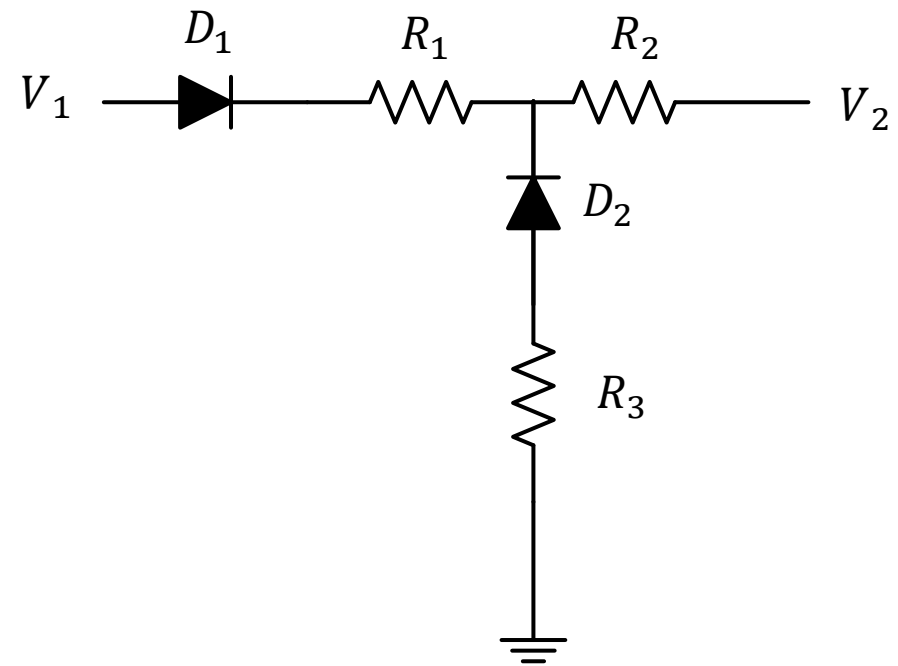



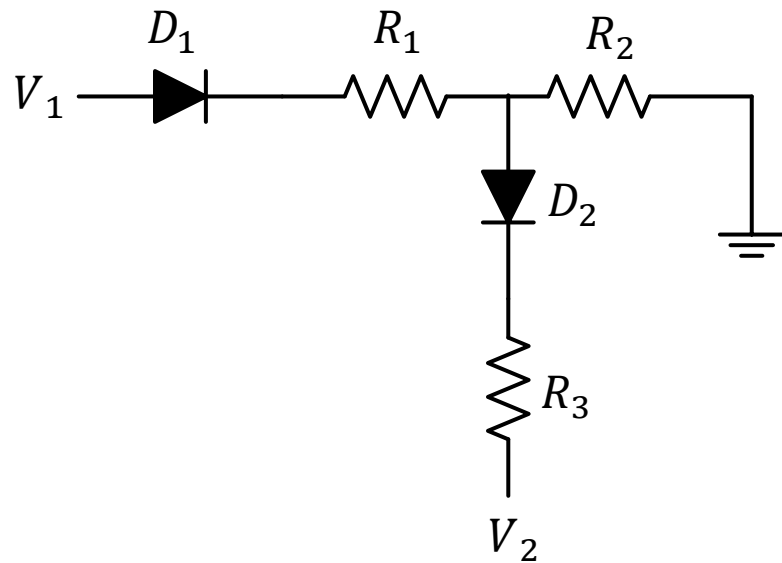
1. Determine the conduction state of the diodes assuming that all the diodes are ON.
2. Determine the diode currents. consider Si diode.  $R_1 = 2k$ ,  $R_2 = 0.5k$ ,  $R_3 = 5k$ ,  $V_1 = 4V$  and  $V_2 = 2V$





1. Solve the circuit making the following assumptions and justify the assumptions made.

D1	D2
ON	OFF
OFF	ON

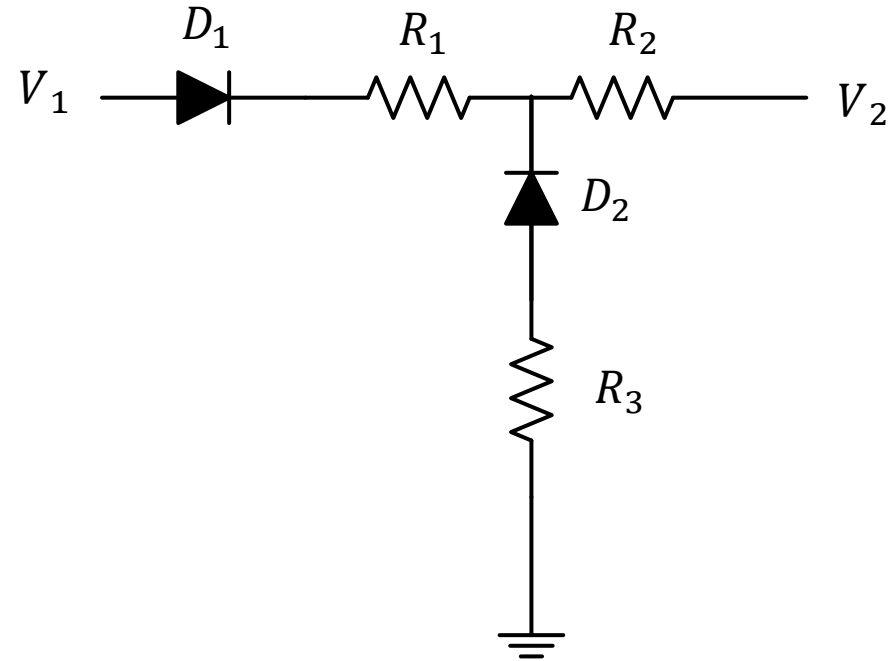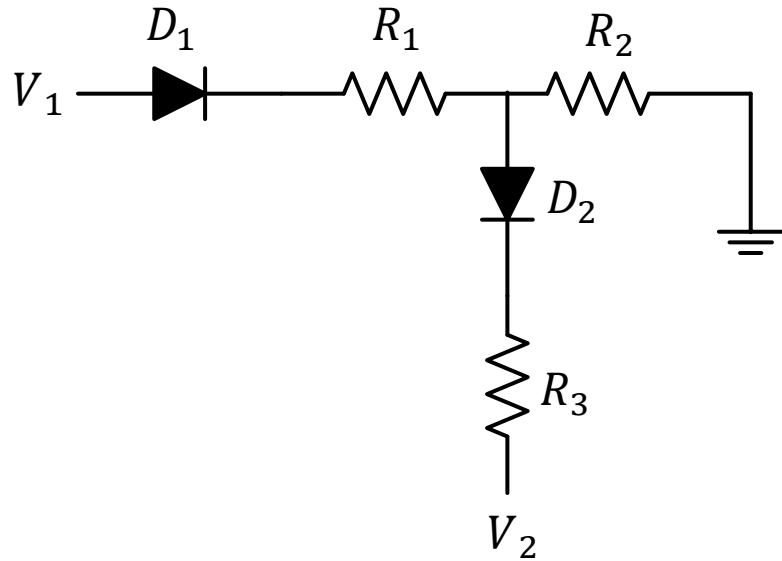Consider Si diode.  $R_1 = 2k$ ,  $R_2 = 0.5k$ ,  $R_3 = 5k$ ,  $V_1 = 4V$  and  $V_2 = 2V$



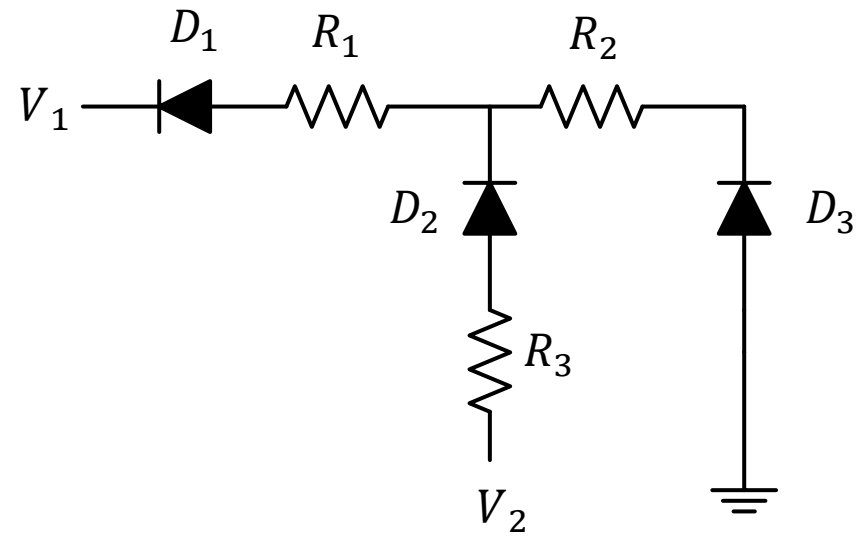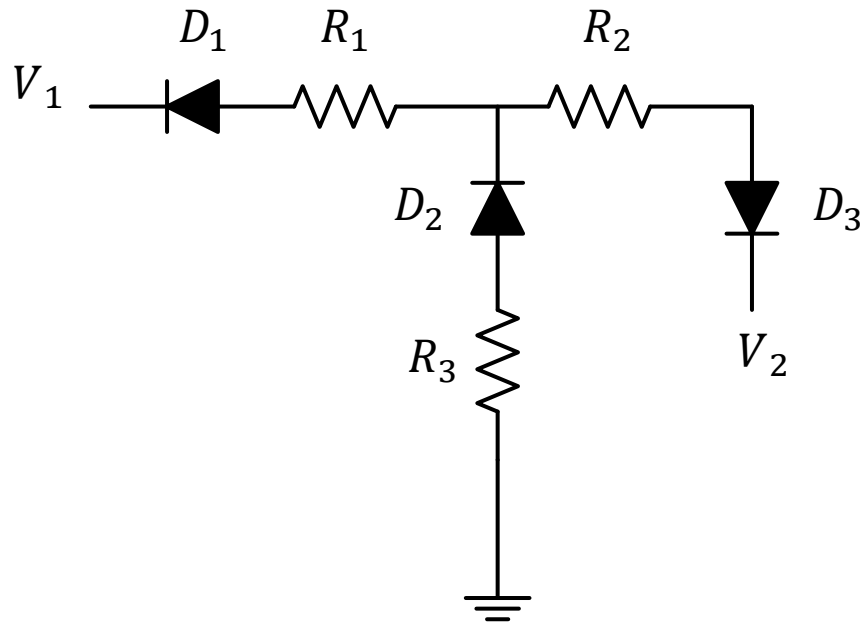1. Determine the conduction state of the diodes assuming that all the diodes are ON.
2. Determine the diode currents. consider Si diode.  $R_1 = 2k$ ,  $R_2 = 0.5k$ ,  $R_3 = 5k$ ,  $V_1 = 4V$  and  $V_2 = 2V$



1. Determine the conduction state of the diodes assuming that all the diodes are ON.
2. Determine the diode currents. consider Si diode.  $R_1 = 2k$ ,  $R_2 = 0.5k$ ,  $R_3 = 5k$ ,  $V_1 = 4V$  and  $2V$ .

