

Brac University

Department of Electrical & Electronic Engineering

Semester - Fall25



Course Number

Course Title: ELECTRONIC CIRCUITS I LABORATORY

Section:01

Lab Report

Experiment no.

Name of the experiment: Rectification

Prepared by:

Name: Tashin Ahmed Sakib ID: 24121076

Group Number: 01

Other Group members:

| <i>Sl.</i> | <i>ID</i> | <i>Name</i> |
|------------|-----------------|----------------------------------|
| <i>01</i> | <i>24121308</i> | <i>Alif Tamjid</i> |
| <i>02</i> | <i>24121205</i> | <i>Souvik Barman Ratul</i> |
| <i>03</i> | <i>24121058</i> | <i>Muhammad Mushfiqur Rahman</i> |
| <i>04</i> | <i>24121204</i> | <i>Abir Chowdhury Ratul</i> |

Experiment 02


Rectification

Objective: To find the operation and performance of half-wave and full-wave bridge rectifier circuits by analyzing their input and output voltage waveforms and evaluating their ability to convert alternating current (AC) into pulsating direct current (DC).

Equipments:

1. Breadboard
2. Jumper Wires
3. AC voltage Source
4. $1\text{K}\Omega$ Resistors
5. Diode (1N4007)
6. Oscilloscope

Half wave Rectifier Circuit:

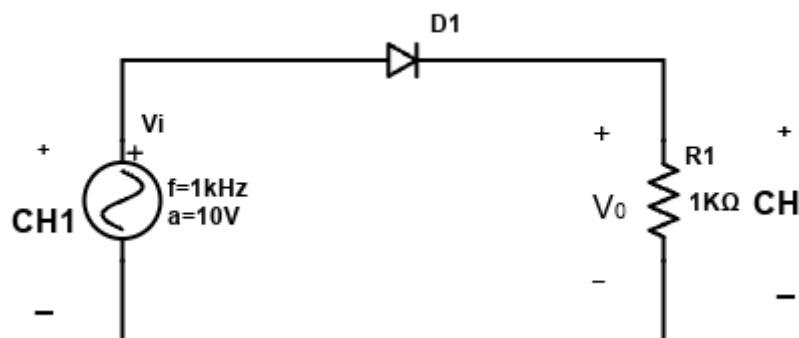

Data:

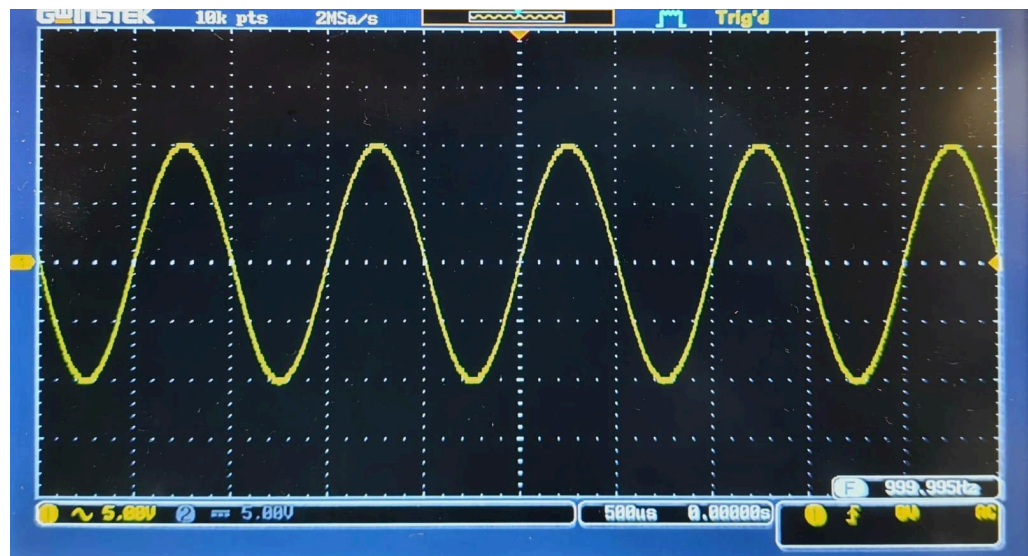


Fig: Input AC Voltage (V_i)


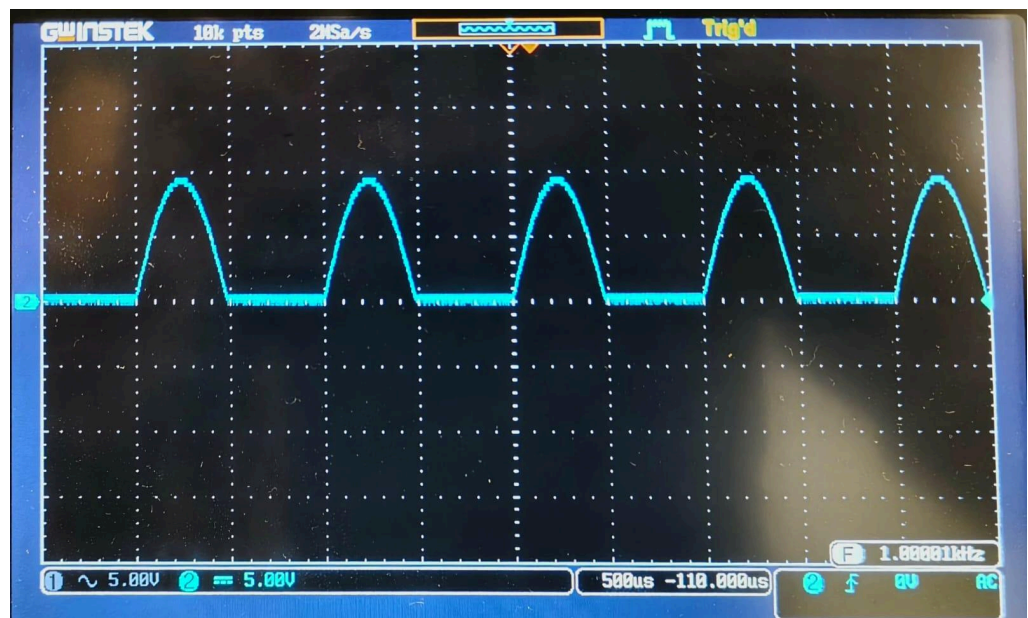


Fig: Half-Wave Rectified Output Voltage (V_o)

Full Wave rectifier circuit:

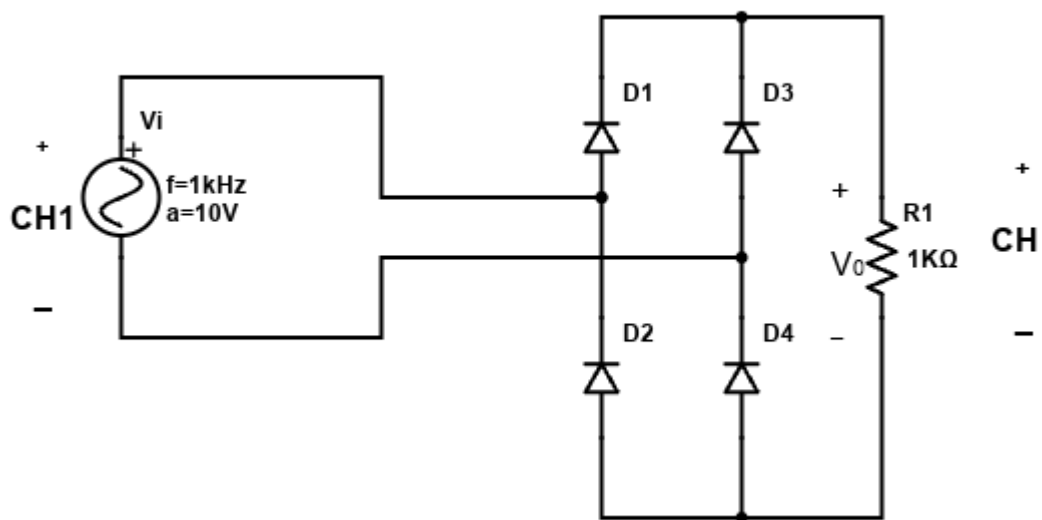

Data:

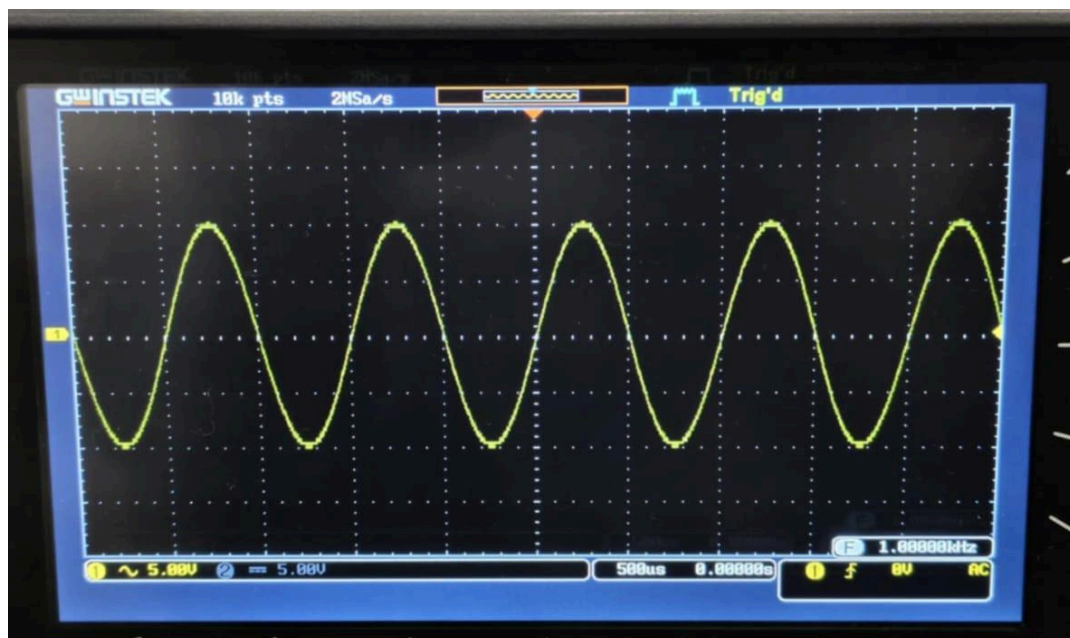


Fig: Input AC Voltage (V_i)

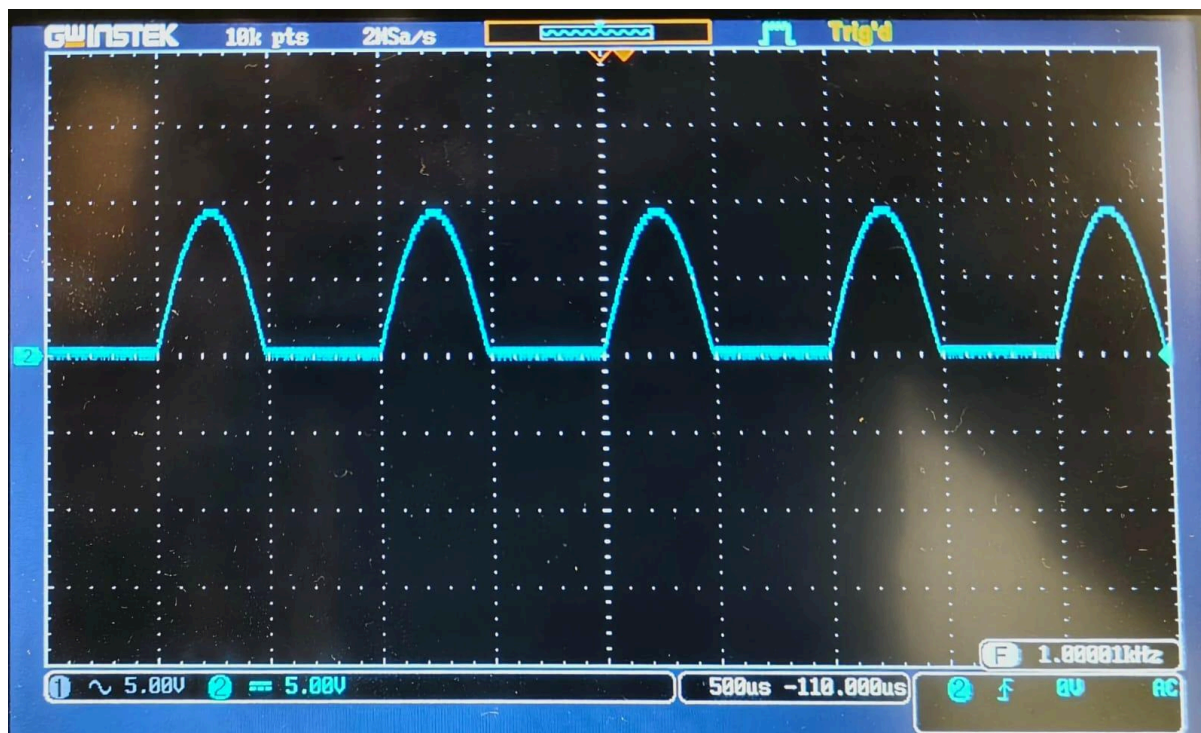


Fig: Full-Wave Rectified Output Voltage (V_o)





Appendix:

Group: 01




Experiment 2

Rectification

Half wave rectification.

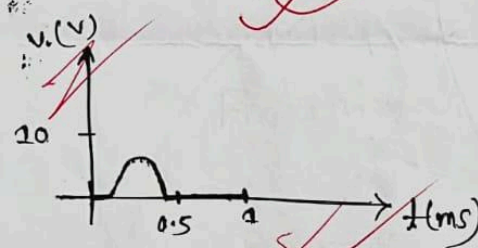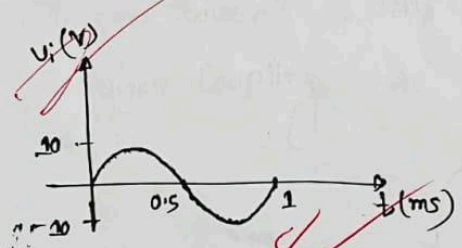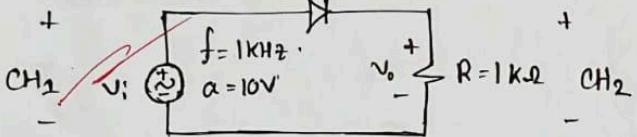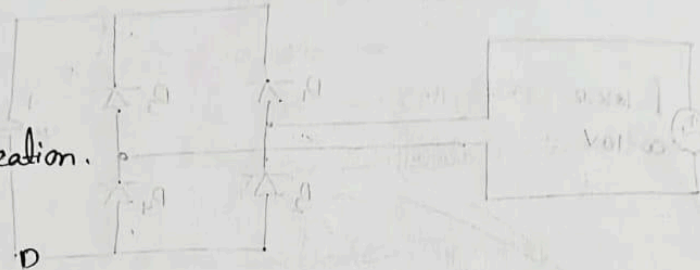

Full-wave Rectifier:

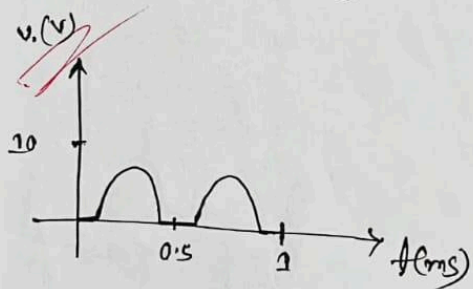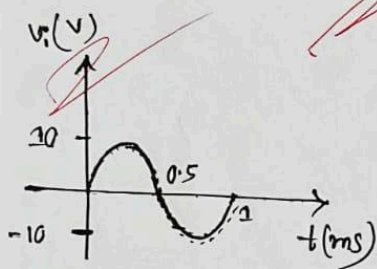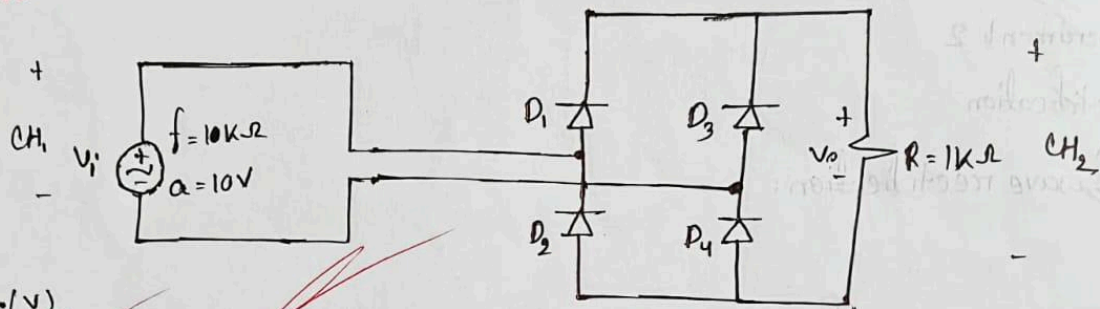

Work

Oscilloscope settings:

| | CH ₁ | CH ₂ |
|--------------|-----------------|---|
| Probe Switch | 1X | 1X → connector |
| Zero Line | x axis | x axis → |
| AC/DC | AC | DC → (CH ₁ & CH ₂) |
| Volts / DIV. | 5V | 5V → (scale → downside of CH ₁ & CH ₂) |

Time / DIV

0.5ms → (scale → Top right).

| | |
|------------------|-----------------------------------|
| Trigger mode | ATO |
| Trigger Level | 0V |
| Trigger Source | CH ₁ / CH ₂ |
| Trigger Coupling | AC |

(menu)

$\frac{10}{10}$

Experiment 1

↓

Zener

↓

Some Faults

[Signature]

2015-October-30