

Brac University

Department of Electrical & Electronic Engineering

Semester - Fall25



Course Number

Course Title: ELECTRONIC CIRCUITS I LABORATORY

Section:01

Lab Report

Experiment no.

Name of the experiment: Clipping and Clamping

Prepared by:

Name: Tashin Ahmed Sakib ID: 24121076

Group Number: 01

Other Group members:

<i>Sl.</i>	<i>ID</i>	<i>Name</i>
<i>01</i>	<i>24121308</i>	<i>Alif Tamjid</i>
<i>02</i>	<i>24121205</i>	<i>Souvik Barman Ratul</i>
<i>03</i>	<i>24121058</i>	<i>Muhammad Mushfiqur Rahman</i>
<i>04</i>	<i>24121204</i>	<i>Abir Chowdhury Ratul</i>

Experiment 03

Clipping and Clamping

Objective: To find the operation and characteristics of diode-based clipping and clamping circuits by analyzing their modification of the peak amplitude and DC reference level of input waveforms.

Equipments:

1. Breadboard
2. Jumper Wires
3. AC and DC voltage Source
4. $10\text{K}\Omega$ and $220\text{K}\Omega$ Resistors
5. Diode (1N4007)
6. $1\mu\text{F}$ Capacitor
7. Oscilloscope

Clipping Circuit:

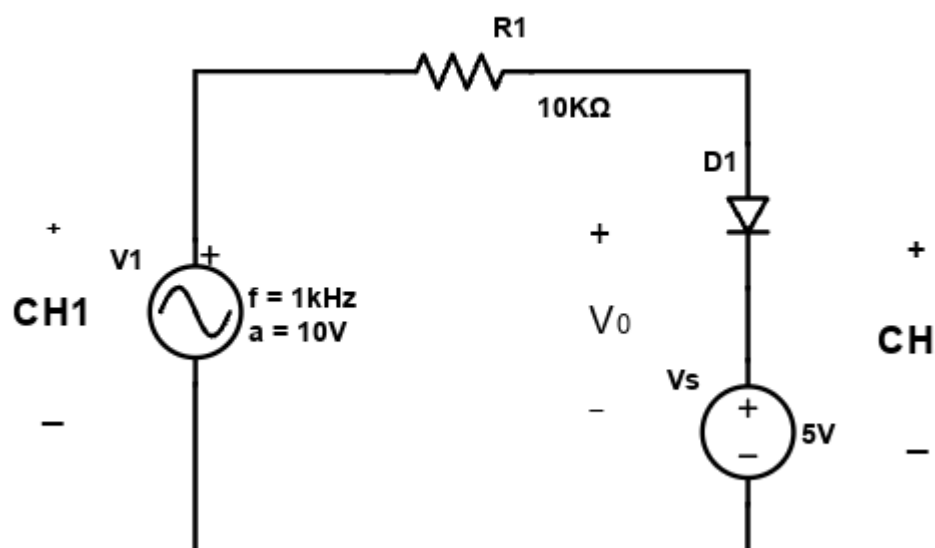


Fig: Clipping Positive Circuit

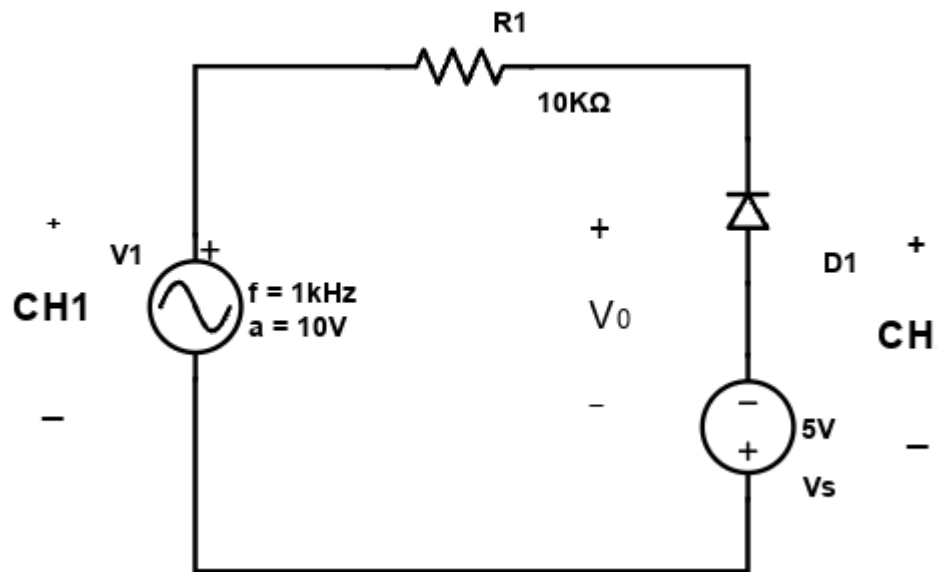


Fig: Clipping Negative Circuit

Data:

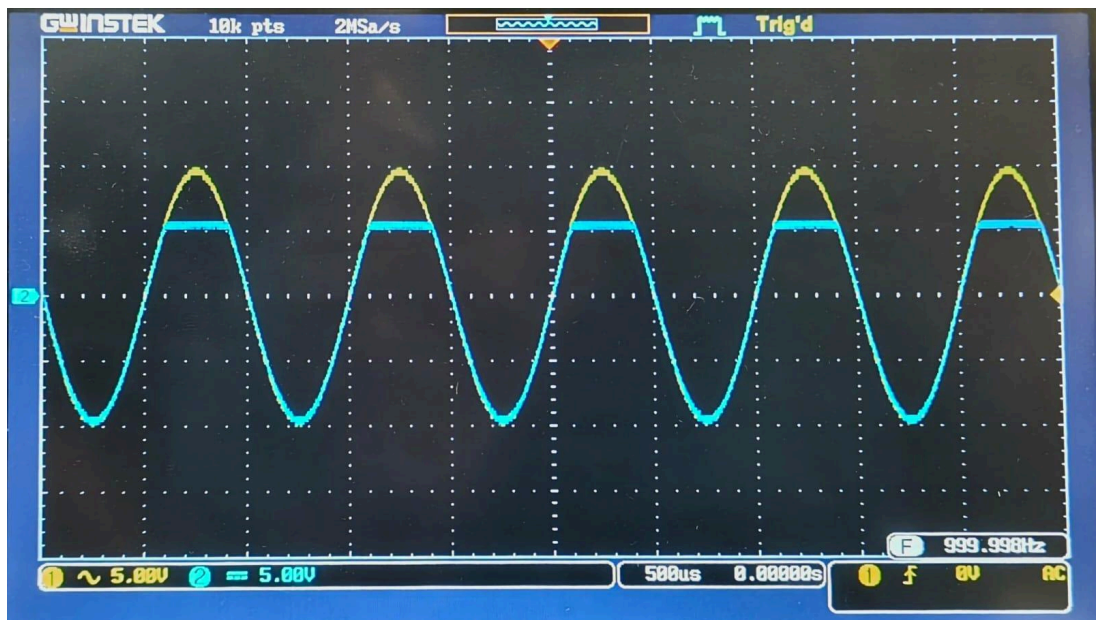


Fig: Input and Output Waveforms of a Positive Clipping Circuit

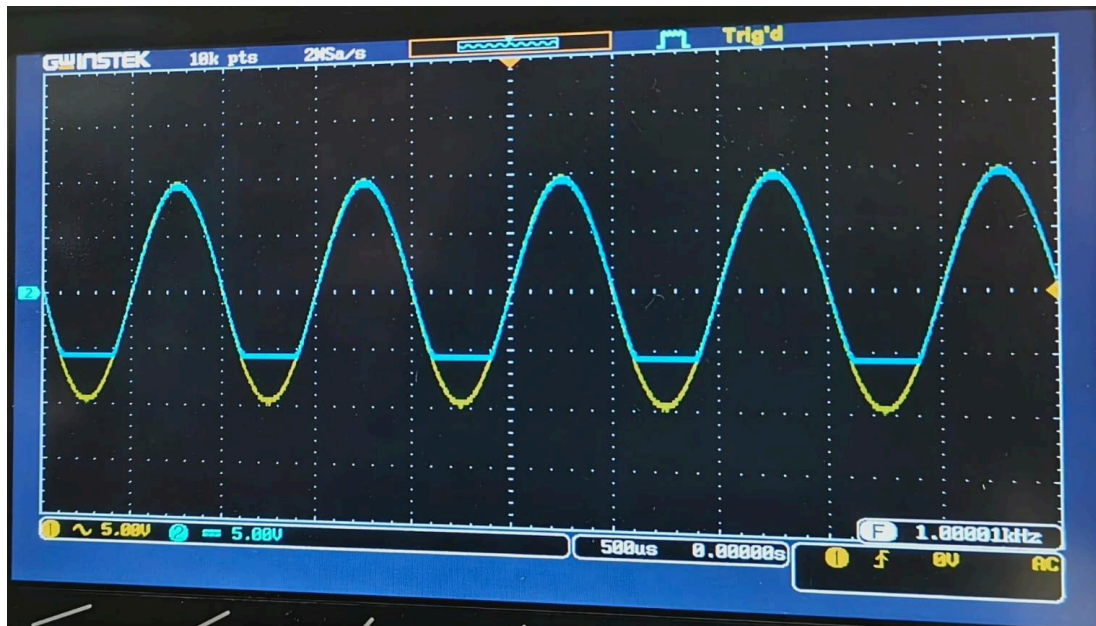


Fig: Input and Output Waveforms of a Negative Clipping Circuit

Clamping circuit:

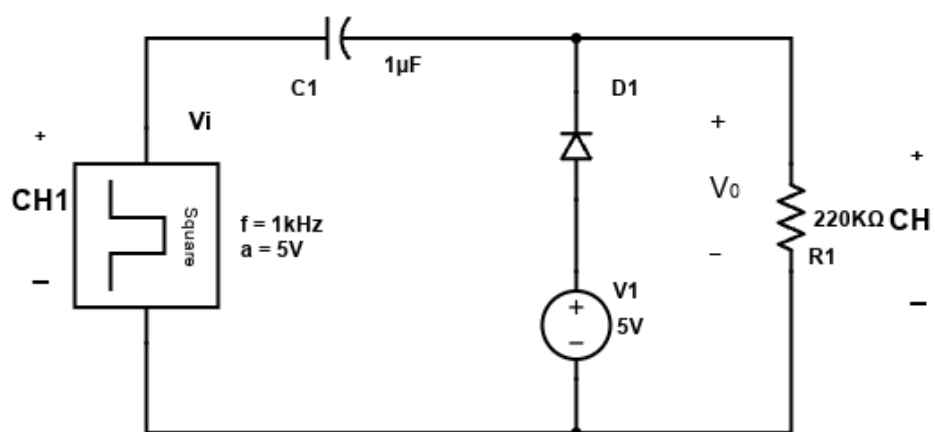


Fig: Clamping Positive Circuit

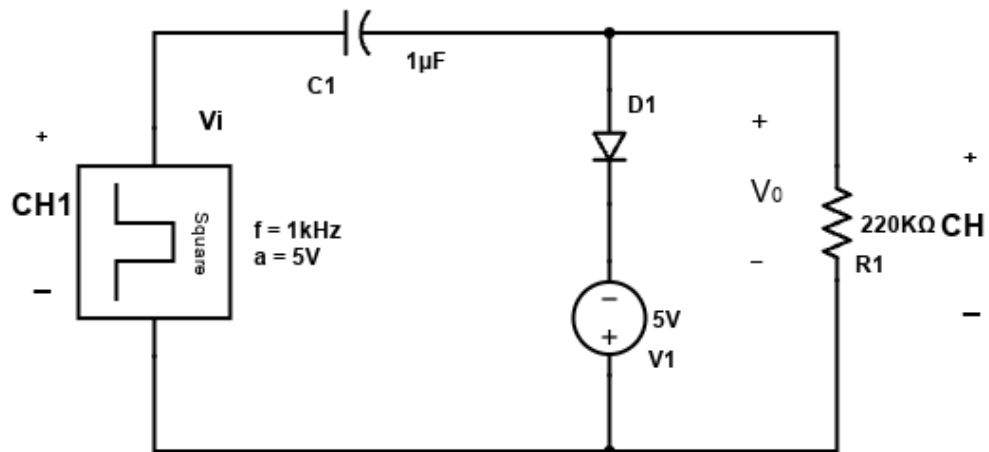


Fig: Clamping Negative Circuit

Data:

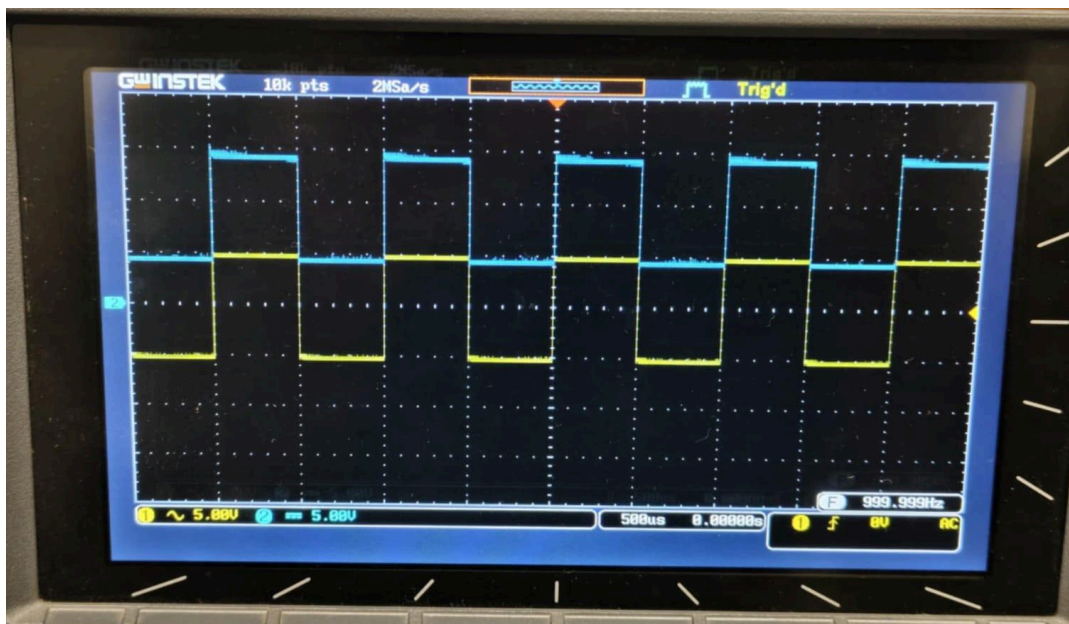


Fig: Input and Output Waveforms of a Positive Clamping Circuit



Fig: Input and Output Waveforms of a Negative Clamping Circuit



Appendix:

Experiment 3



Group: 02

Clipping and clamping.



Clipping: (1) Positive

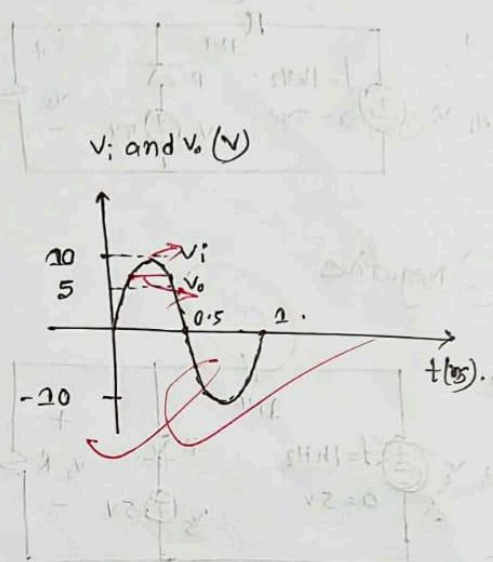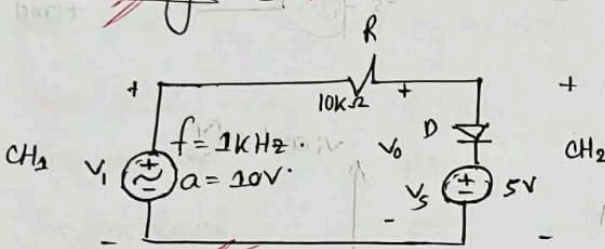



(2) Negative

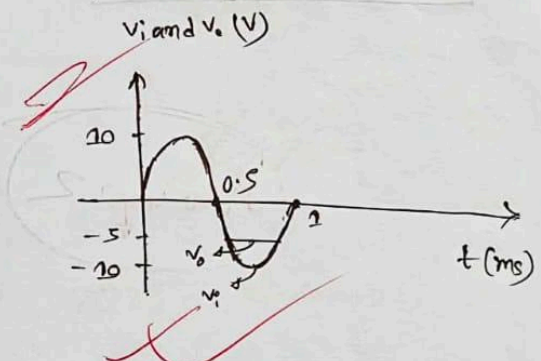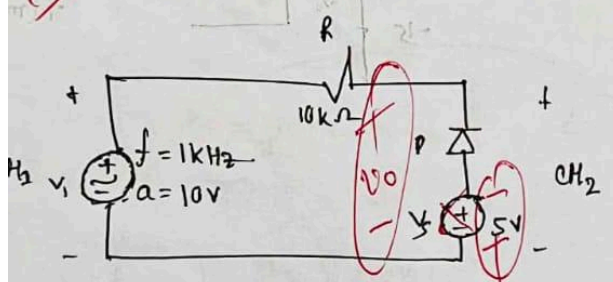

Clamping: (1) Positive

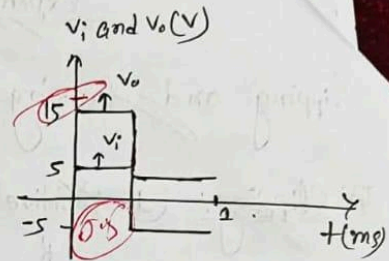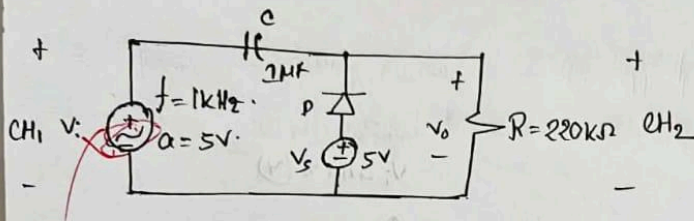

(2) Negative

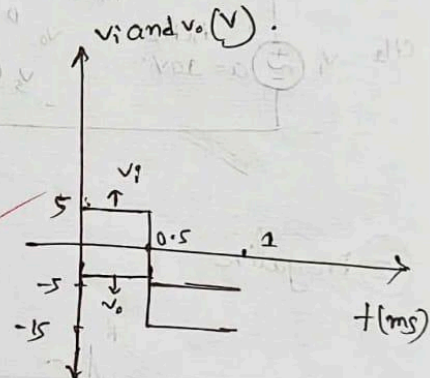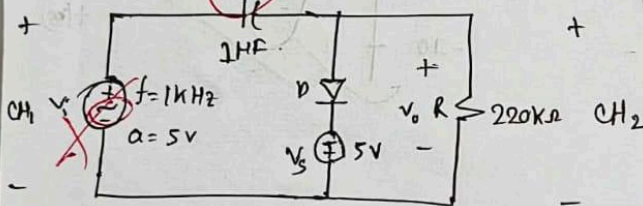

Group 2

Experiment 2 Oscilloscope Settings

Probe Switch

CH₁

CH₂

1X

1X

Zero Line

X-axis

X-axis

AC/DC

AC

DC

VOLTS/DIV

5V

5V

Time/DIV

0.5ms

Trigger mode

ATO

Trigger Level

0V

Trigger Source

CH₁

Trigger Coupling

AC

40
10

Experiment 2

↓

Full-Wave

↓

Alright

2025- November - 6