

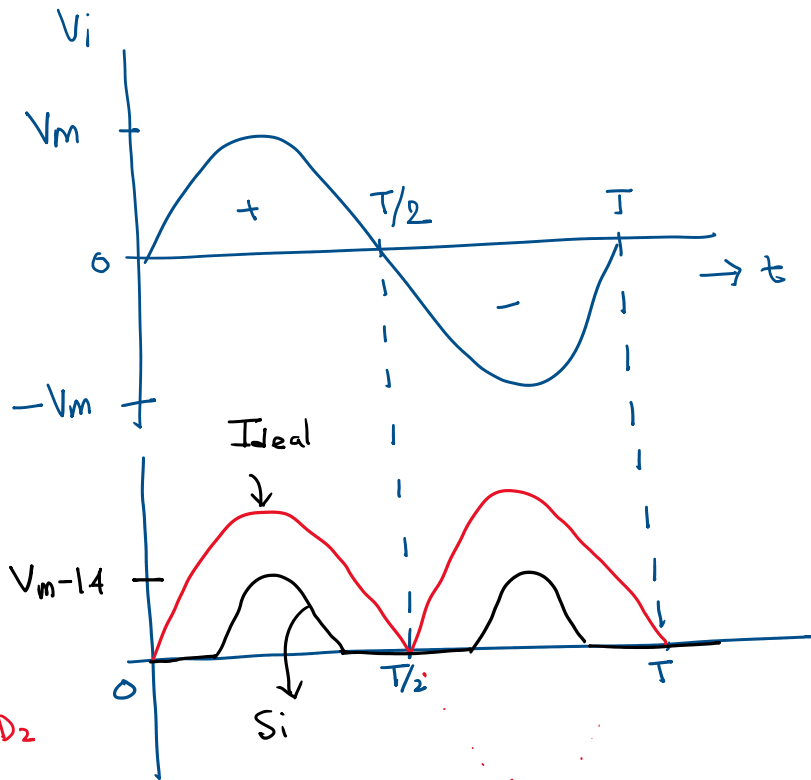


# □ F.W. Bridge Rectifier


Idea chide,  $V_D = 0V$  [F.B]

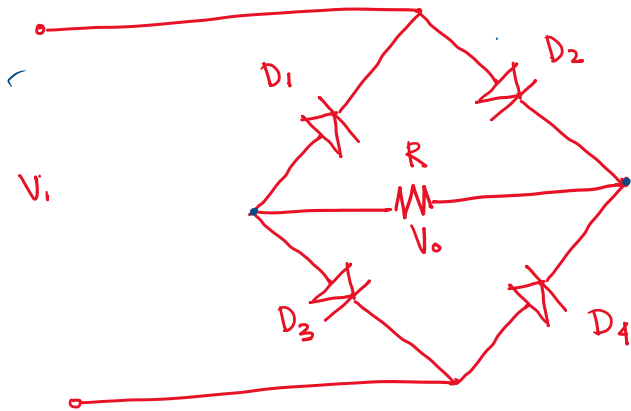

$0 < t < T/2, V_o > 0$

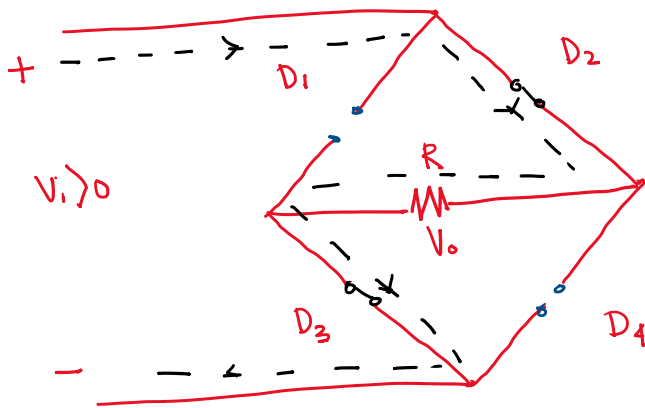



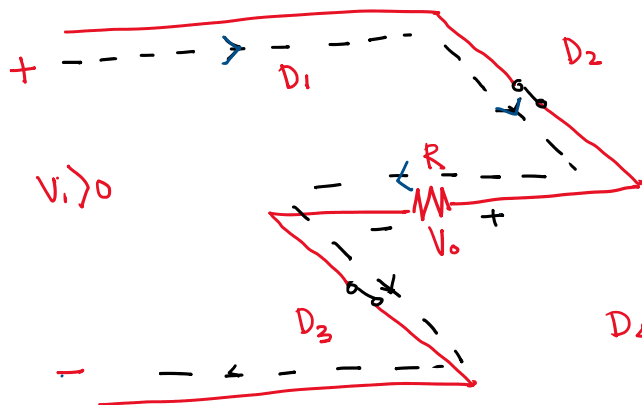
$D_1 \text{ \& } D_4 \rightarrow R.B$   
 $D_2 \text{ \& } D_3 \rightarrow F.B$



$$+ V_i - V_o = 0$$

$$\Rightarrow \boxed{V_o = V_i}$$

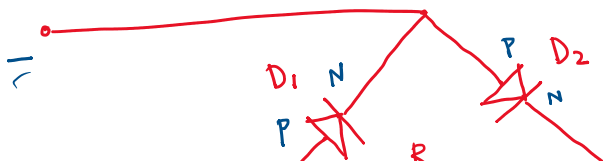

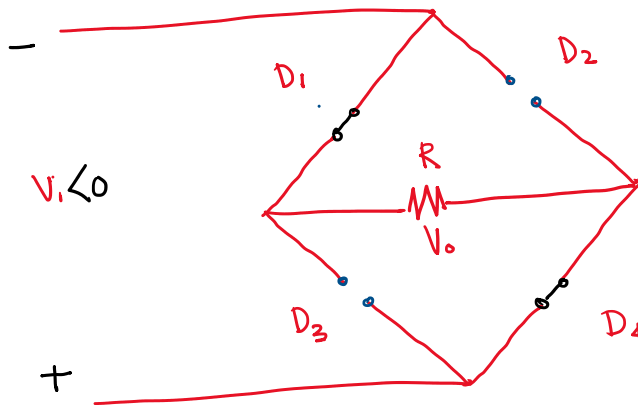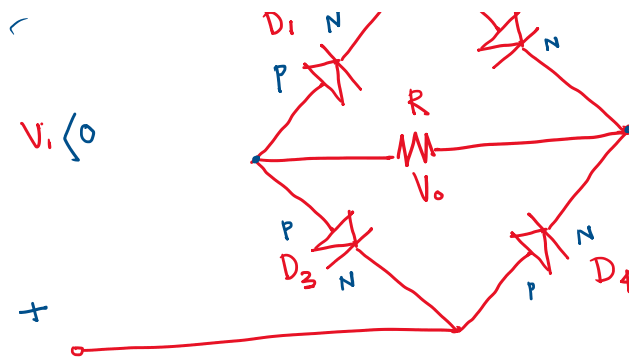


$$T/2 < t < T, V_i < 0$$

$$D_2 \text{ \& } D_3 \rightarrow R.B$$

$$D_1 \text{ \& } D_4 \rightarrow F.B$$

1. Magnitude
2. Sign (+/-)

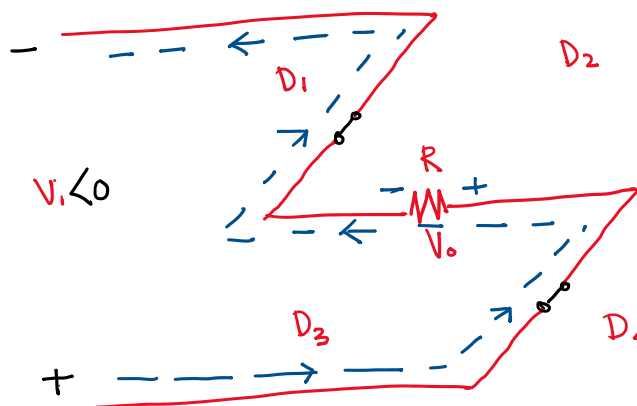

$$-V_i + V_o = 0$$


$$\Rightarrow V_o = V_i$$

$$| \frac{V_i < 0}{=} |$$

$$-V_i + V_o = 0$$

$$\Rightarrow \boxed{V_o = V_i} \rightarrow \text{Magnitude}$$

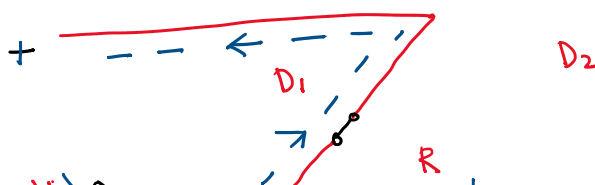If we assume that  $V_i$  is unknown, therefore we consider that  $V_i$  is +ve ( $V_i > 0$ ),



$$+V_i + V_o = 0$$


$$\Rightarrow \boxed{V_o = -V_i}$$

$$V_o(\max) = -(-V_m) = V_m$$



⑤


$$V_i > 0$$

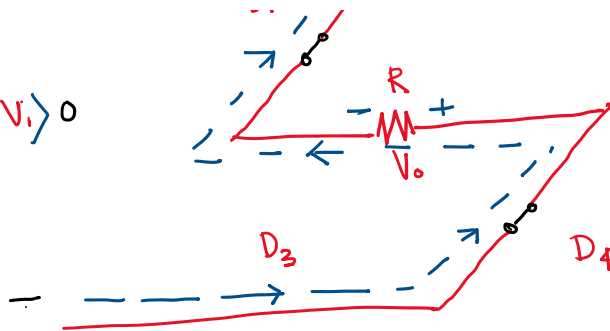

$$\Rightarrow \underline{V_o = -V_i}$$

$$V_o(\max) = -(-V_m) = V_m$$

$$V_i(\max) = -V_m$$

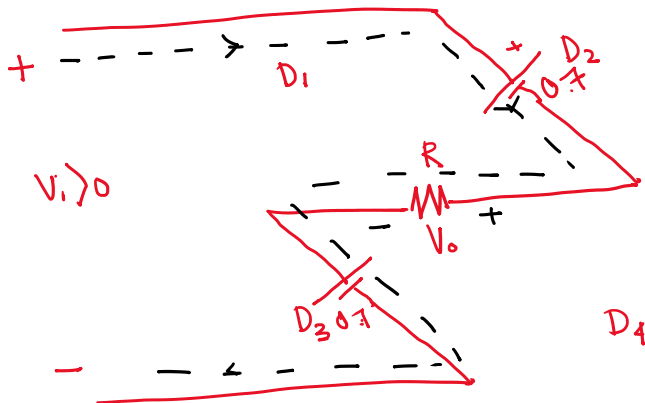

$$V_i - 0.7 - V_o - 0.7 = 0$$

$$\Rightarrow V_o = V_i - 1.4$$