
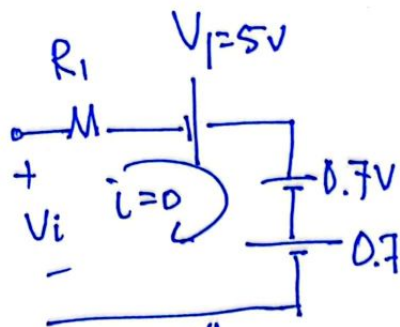
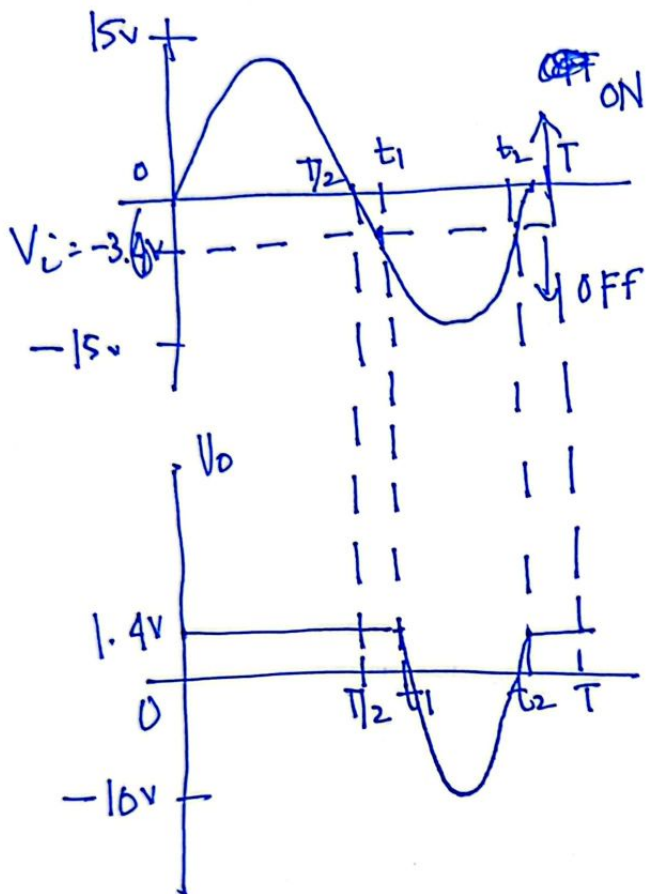


□

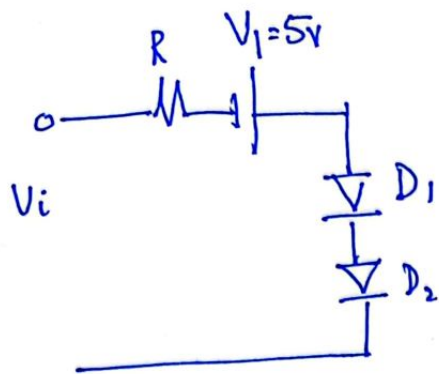



$$V_i - iR_1 + 0.5 - 0.7 - 0.7 = 0$$

$$V_i = -3.6V$$

$0 < t < t_1, V_i > -3.6V, \text{ ON}$

$t_1 < t < t_2, V_i < -3.6V, \text{ OFF}$


$t_2 < t < T, V_i > -3.6V, \text{ ON}$

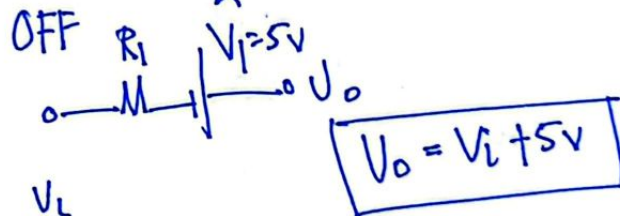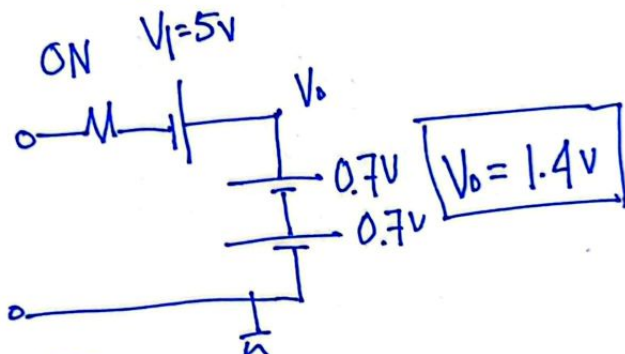


$$V_i(\max) = -15V$$

$$V_o(\max) = -15 + 5 = -10$$

□

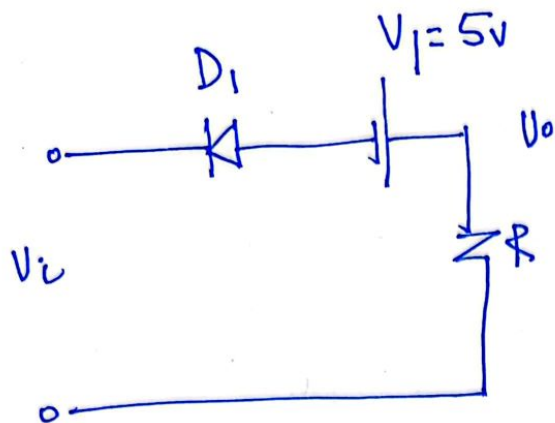


Transition State

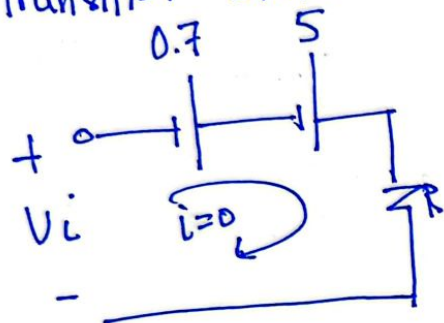

$$V_i + 0.7 + 5 = iR = 0$$

$$V_i = -5.7V$$

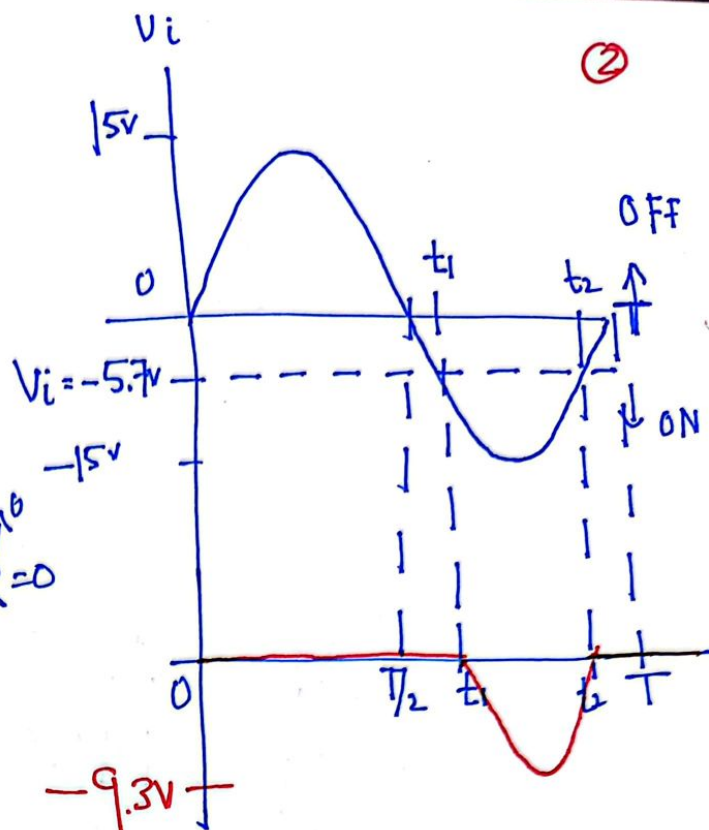


$$V_i(\max) = -15, V_o(\max) = -15 + 5.7 = -9.3V$$

$0 < t < t_1, V_i > -5.7V, \text{ OFF.}$

$t_1 < t < t_2, V_i < -5.7V, \text{ ON}$

$t_2 < t < T, V_i > -5.7V \text{ OFF}$


Vo: ON 0.7 5v

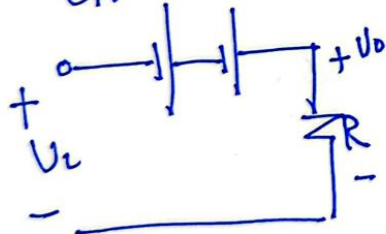

$$V_i + 0.7 + 5 = V_o$$




$$\Rightarrow V_o = V_i + 5.7$$

OFF

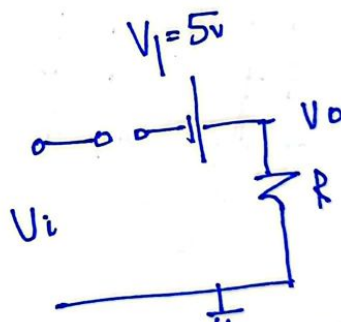

$$V_o = iR = 0 \quad [i=0]$$


③

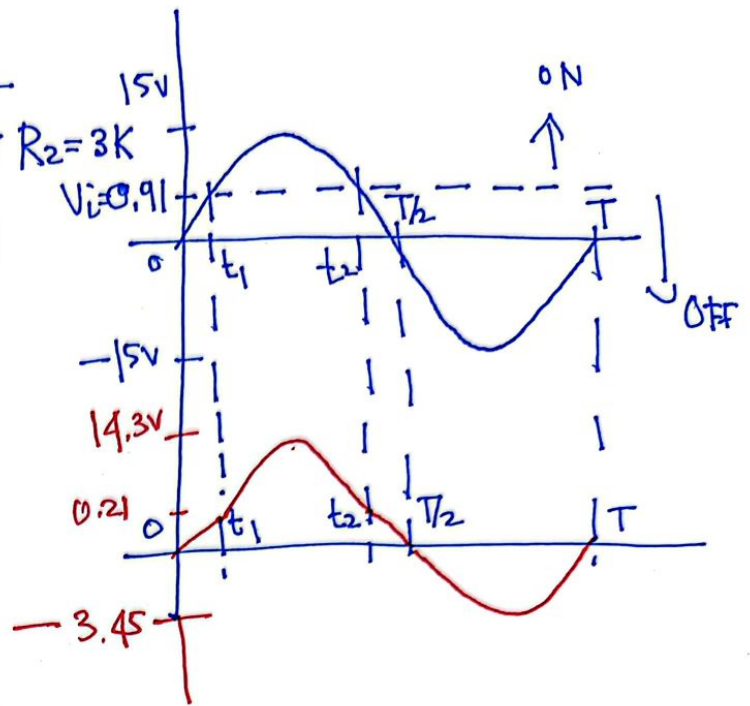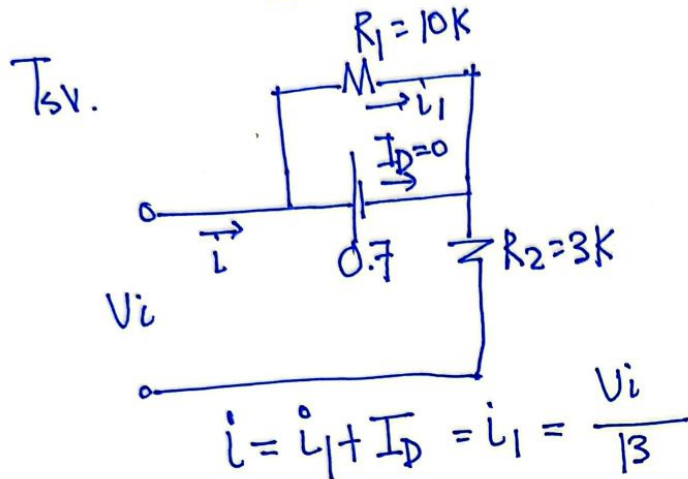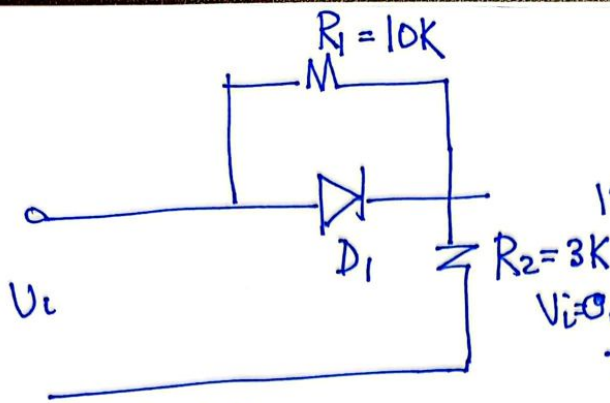

at Transition  $V_{R1} = 0.7V$  [  $R_1$  & Diode are parallel ]

$$\Rightarrow i R_1 = 0.7V \Rightarrow \frac{V_i}{13} \times 10 = 0.7V \Rightarrow \boxed{V_i = 0.91V} \text{ TSV}$$

Vo: Relation:  $R_1 = 10K$

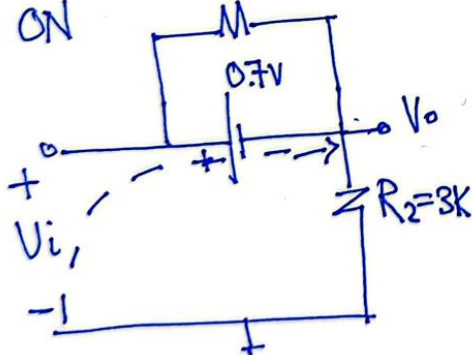


$$V_i - 0.7 = V_o$$

$$\boxed{V_o = V_i - 0.7}$$

~~$t=0, V_o = -0.7V$~~

~~$t=t_1, V_i = 0.91, V_o = 0.91 - 0.7 = 0.21$~~

$V_i(\max) = 15V, V_o = 15 - 0.7 = 14.3$

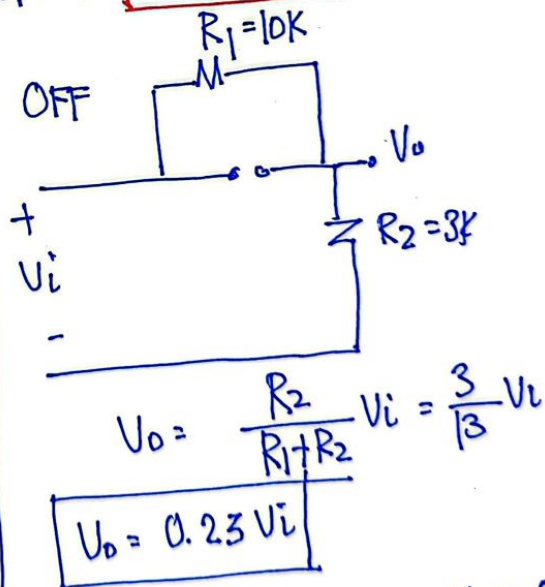



$t=0, V_i = 0, V_o = 0$

$t=t_1, V_i = 0.91, V_o = 0.21$


$V_i(\max) = -15V, V_o(\max) = 0.23 \times (-15) = -3.45V$



④

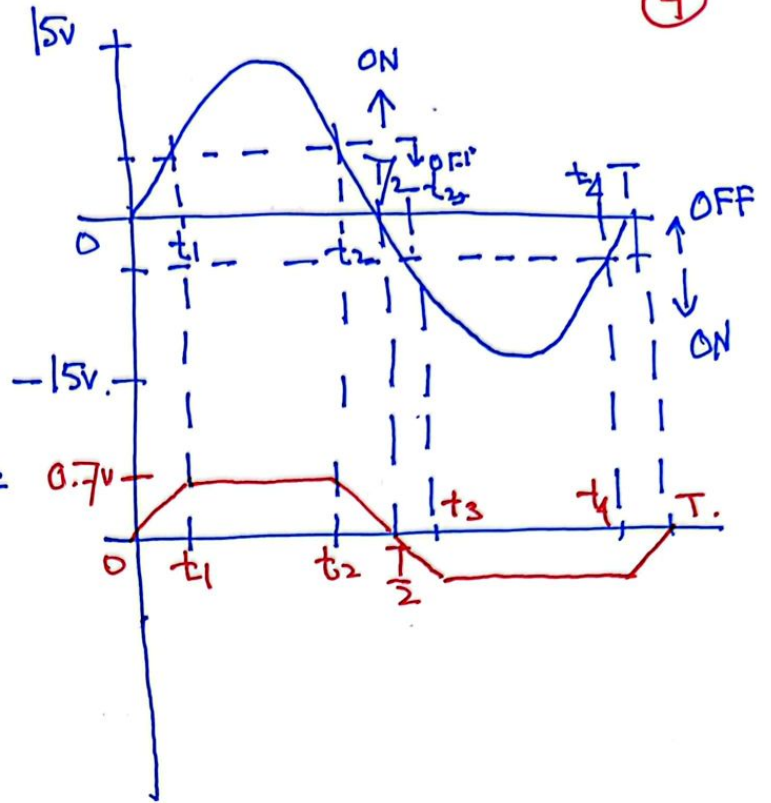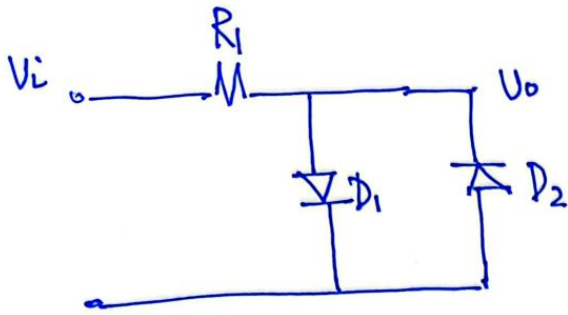

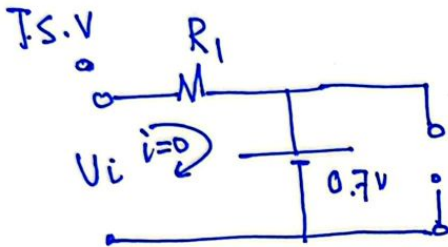$0 < t < T/2, V_i > 0, D_2 \rightarrow R.B. \rightarrow OFF$




$$V_i = 0.7V$$

$0 < t < t_1: V_i < 0.7V, OFF.$


$t_1 < t < t_2: V_i > 0.7V, ON$

$t_2 < t < T/2, V_i < 0.7V, OFF$

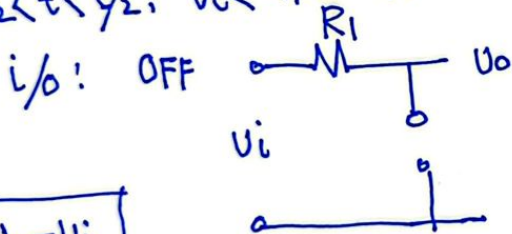


$$V_o = V_i$$

ON

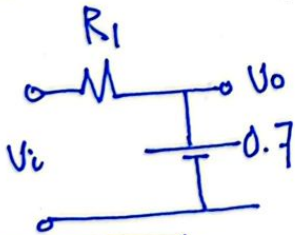

$$V_o = 0.7V$$

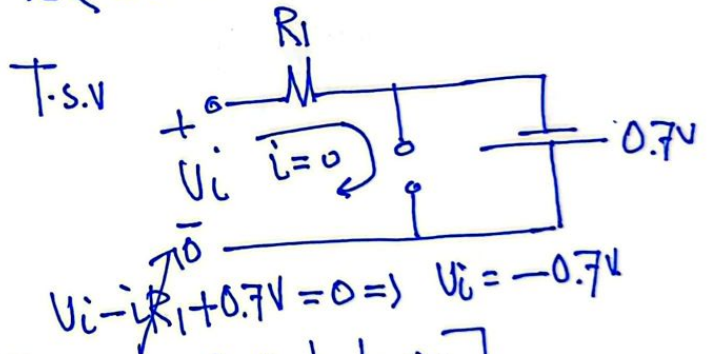$T/2 < t < T, D_1 \rightarrow R.B. \rightarrow OFF$



$$V_i - iR_1 + 0.7V = 0 \Rightarrow V_i = -0.7V$$


[Diode Anticlockwise]

$T/2 < t < t_3, V_i > -0.7V, OFF$

$t_3 < t < t_4, V_i < -0.7V, ON$


$t_4 < t < T, V_i > -0.7V, OFF$

$i_o: OFF, V_o = V_i$


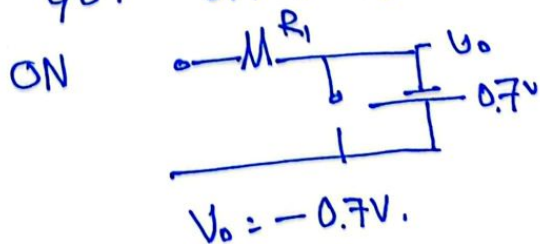


$$V_o = -0.7V$$

5

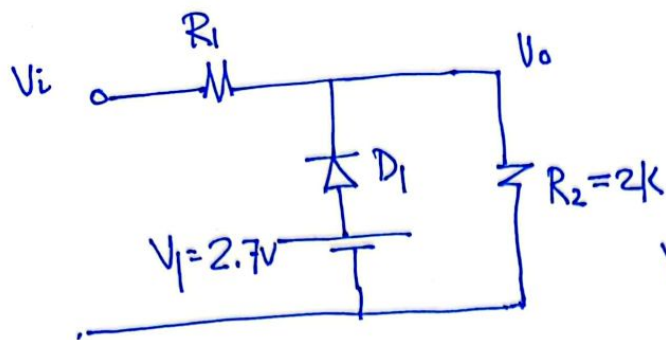

Diode  
Anticlockwise

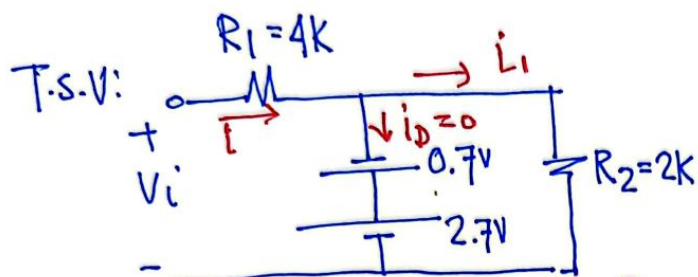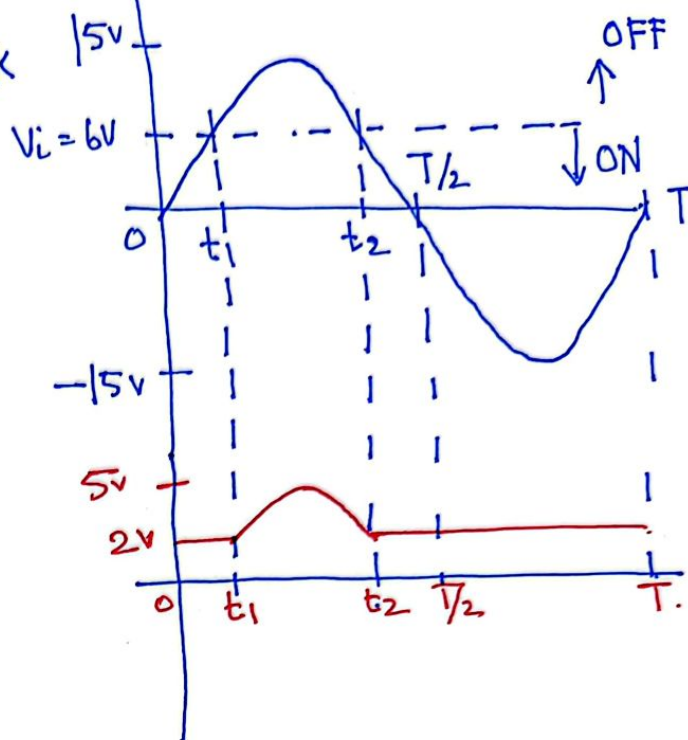

$$i = i_D + i_1 \quad [\text{at transition}]$$

$$i = i_1 = \frac{V_i}{R_1 + R_2} = \frac{V_i}{6}$$

$$V_{R_2} = 2.7 - 0.7 = 2V$$

$$\Rightarrow i_{R_2} = 2 \Rightarrow \frac{V_i}{6} \times 2 = 2$$

$$\Rightarrow V_i = 6V$$



$0 < t < t_1$ ,  $V_i < 6V$ , ON

$t_1 < t < t_2$ ,  $V_i > 6V$ , OFF

$t_2 < t < T$ ,  $V_i < 6V$ , ON

i/o. Relationship.

ON

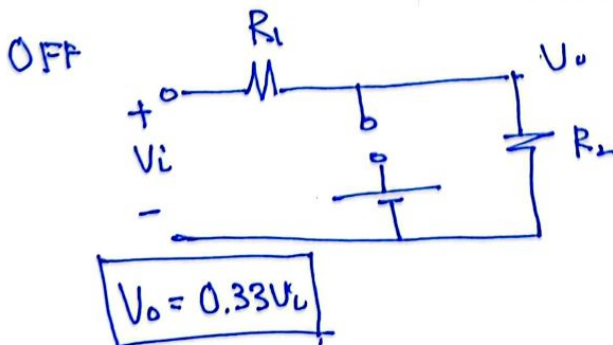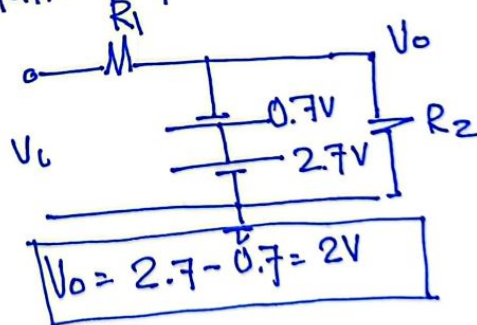

$$V_o = \frac{R_2}{R_1 + R_2} V_i$$

$$= \frac{2}{6} V_i = 0.33 V_i$$

③  $V_i(\max) = 15V$ ,  $V_o(\max) = 0.33 \times 15 = 5V$ .