

## Lecture

24.12.25

### BJT / MOSFET Switching:


For switching - 2 area of operation is required.

BJT : ON(sat)  $\leftrightarrow$  OFF (cut-off)

BJT

MOSFET : ON (Triode)  $\leftrightarrow$  OFF (cut-off)

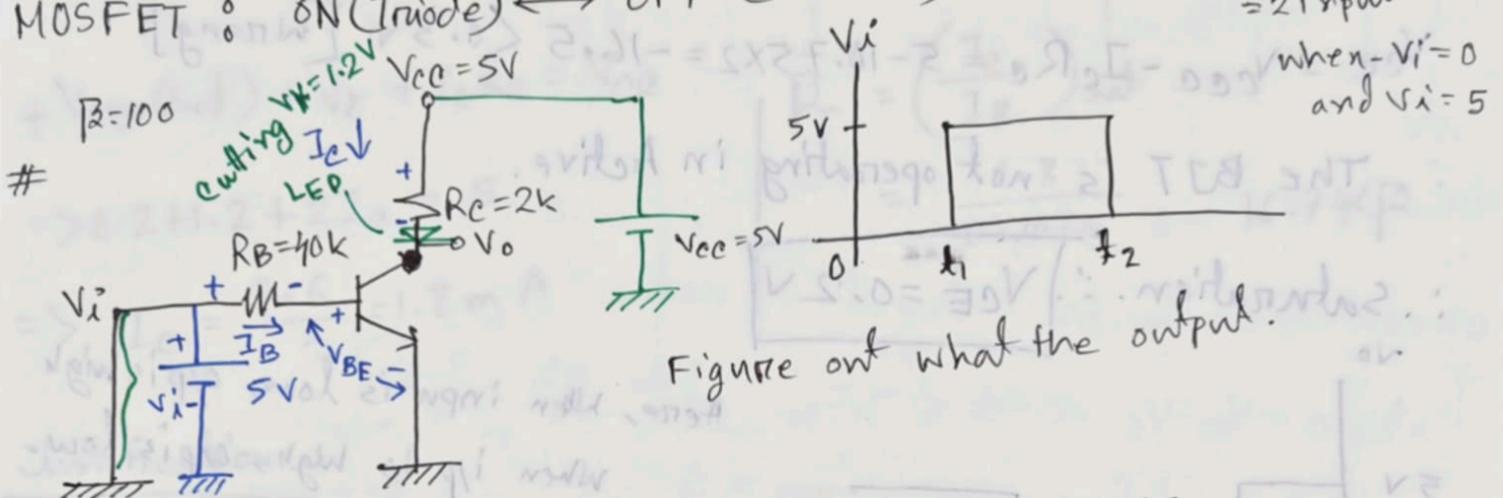= 2 input  
when  $V_i = 0$   
and  $V_i = 5$




for  $0 < t < t_1$ ,  $V_i = 0V \Rightarrow$  Now Analyze the BJT.

Check EBJ :  $V_p - V_n = 0 < 0.7V$  [R.B]

BJT is operating in cut-off.  $\therefore I_B = I_C = I_E = 0$ .

For  $V_o$  (check  $V_{CE}$ ) :  $\therefore V_o = V_{CE} = V_{CC} - I_C R_C$
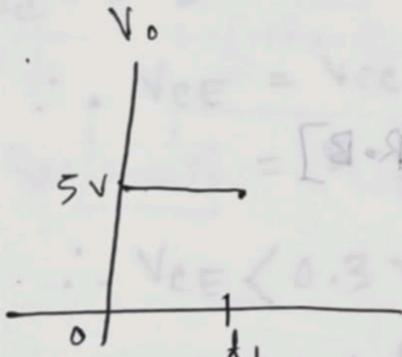
$$\therefore V_o = V_{CE} = V_{CC} = 5V$$



For  $t_1 < t < t_2$ ,  $V_i = 5V$

Check EB] :  $V_p - V_n = 5 - 0 = 5 > 0.7V$

[F.B]

Either operating In Active  
or Saturation:

Assume Active: ( $\alpha, \beta$ ) allowed. Verification:  $V_{CE} > 0.3V$


$$I_B = \frac{V_i - V_{BE}}{R_B} = \frac{5 - 0.7}{40} = \frac{4.3}{40} = 0.1075 \text{ mA}$$

$$\therefore I_C = \beta I_B = 100 \times 0.1075 = 10.75 \text{ mA}$$

$$V_{CE} = V_{CCC} - I_C R_C = 5 - 10.75 \times 2 = -16.5 < 0.3V \quad [\text{Wrong}]$$

The BJT is not operating in Active.

Saturation:  $\therefore V_{CE} = 0.2V$

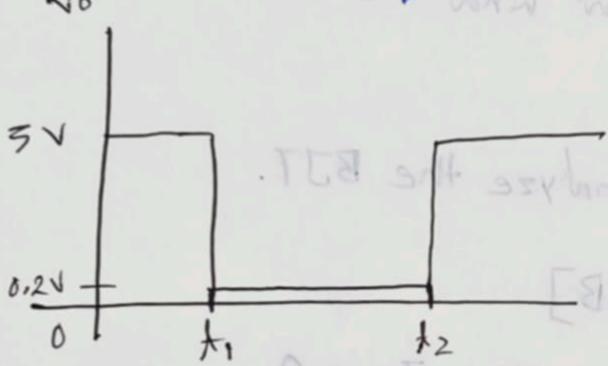


Hence, When input is low, o/p is high.  
When i/p is high, o/p is low.

The BJT inverts the signal.

Act's like an inverter.

or: NOR gate  $0 \rightarrow 1 \quad 1 \rightarrow 0$

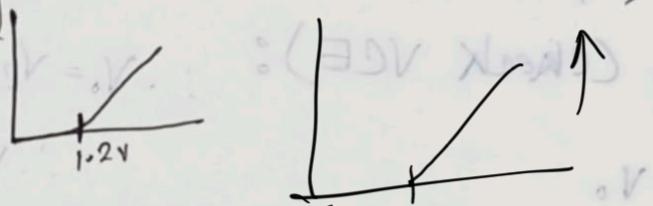Let's Assume the LED attached has a cutting Voltage  $V_D = 1.2V$



For BJT,

$$\text{For } 0 < t < t_1, V_i = 0V$$

$$V_i = 0V$$

$$1.2$$

$$\text{check } V_{BE} = 0 - 0 = 0 < 0.7V \quad [\text{R.B.}]$$

cut-off,  $I_B = I_C = I_E = 0$

The LED is off.  $\times$

For  $f_1 < f < f_2$ ,  $V_i = 5V$

check EBJ;  $V_p - V_n = 5 - 0.7 > 0.7V$  [F.B] [Not in cut-off]

Assume Saturation:

$$I_B = \frac{V_i - V_{BE}}{R_B} = \frac{5 - 0.7}{40} = \frac{4.3}{40} = 0.1075 \text{ mA}$$

LED ✓

$$+V_{CE(\text{sat})} + V_R + I_C R_C = V_{CC}$$

$$\Rightarrow 0.2 + 1.2 + 2I_C = 5$$

$$\Rightarrow I_C = \frac{3.6}{2} = 1.8 \text{ mA}$$

$$\beta_f = \left( \frac{I_C}{I_B} \right)_{\text{sat}}$$

$$= \frac{1.8}{0.1075}$$

$$16.74 \text{ k}\Omega$$

Justification:

Assume Active:  $\times/\beta$  allowed

$$I_B = 0.1075 \text{ mA}$$

$$\therefore I_C = \beta I_B = 10.75 \text{ mA}$$


$$\therefore V_{CE} = V_{CC} - I_C R_C - V_R$$

$$= 5 - 10.75 \times 2 - 1.2 = -17.7V < 0.3V$$

$$\therefore V_{CE} < 0.3V \quad [\text{Assumption Wrong}]$$

∴ Not in Active.

## MOSFET

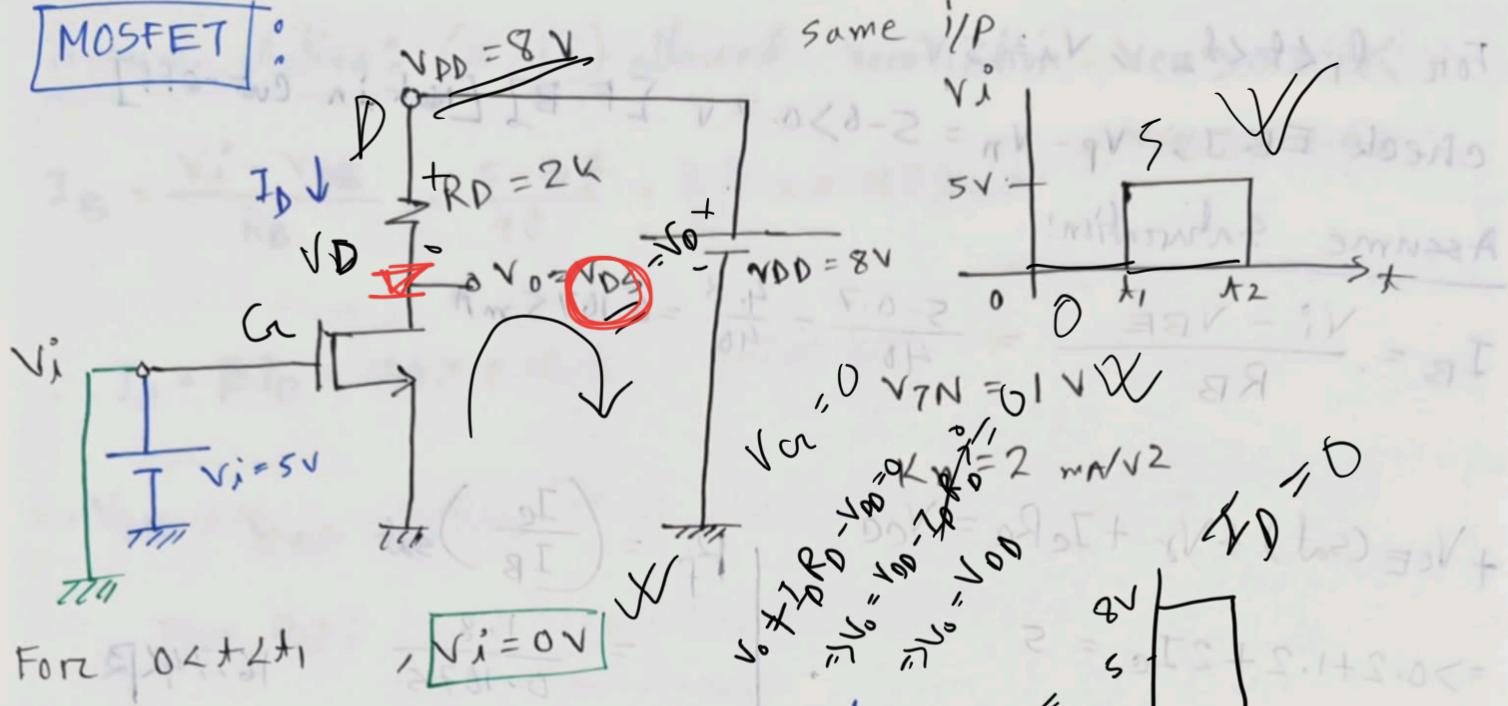

For  $0 < t < t_1$ ,  $V_i = 0V$

$$V_{GDS} = V_G - V_S = 0 - 0 < V_{TN}$$

[No. ch. Trd]


Cut off region,  $I_D = 0$

$$V_o = V_{DS} = V_{DD} - I_D R_D = 8V$$

For,  $t_1 < t < t_2$ ,  $V_i = 5V$   $V_g = 5V$ ,  $V_s = 0V$

$$V_{GDS} = V_G - V_S = 5 - 0 > V_{TN}$$

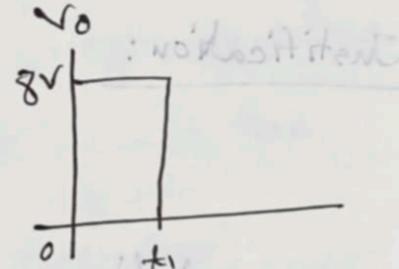[Ch is induced]  $\times$   
[Not cut-off]




check the ch. is induced or not.  $I_D \times$

$$V_{GDS} = V_G - V_S = 5 - 0 > V_{TN}$$

[Ch is induced]  $\times$   
[Not cut-off]

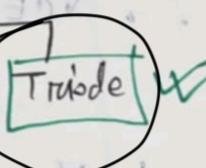For switching, consider MOSFET saturation in Triode by default.



$$I_D = K_n \left[ 2(V_{DS} - V_{TN}) V_{DS} - V_{DS}^2 \right]$$

$$= 2 \left[ 2(0 - 0)(V_D - V_S) - (V_D - V_S)^2 \right]$$

$$I_D = 16V_D - 2V_D^2 = \frac{V_{DD} - V_{DS}}{R_D}$$

$$\Rightarrow \frac{8 - V_D}{2} = 16V_D - 2V_D^2$$

$$\Rightarrow 4V_D^2 - 33V_D + 8 = 0$$

$$\therefore V_{D_1} = 8V$$

$$V_{D_2} = -\frac{1}{4}V$$

$$= 8 - V_D = \frac{32V_D}{2} + \frac{V_D^2}{2} - \frac{4V_D^2}{2}$$

To justify:



$$V_{DD} = V_{G2} - V_D = 5 - 8 = -3V \times$$

$$\sqrt{V_{DD}} = \sqrt{5 - 8} = \sqrt{-3}V \times$$

$$\sqrt{V_{G2} - V_D} = \sqrt{5 - 0.25} = \frac{4.75}{2} \downarrow$$



Triode
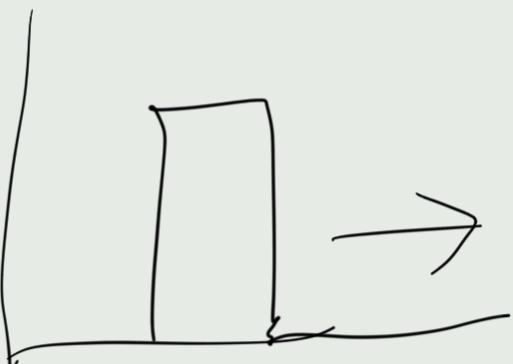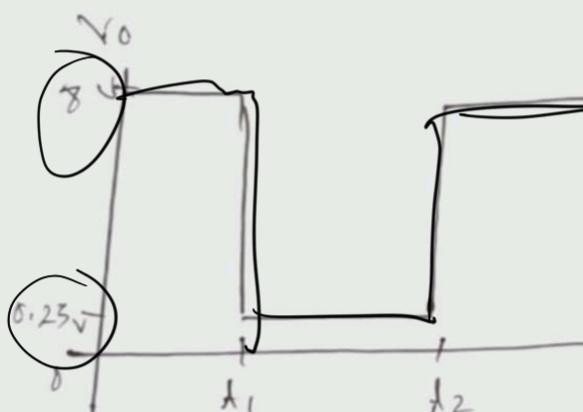
$$\therefore V_D = 0.25V \quad V_0 = 0.25V$$






## Logic Circuits

OR Circuits

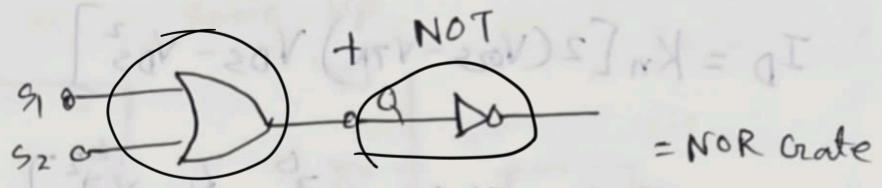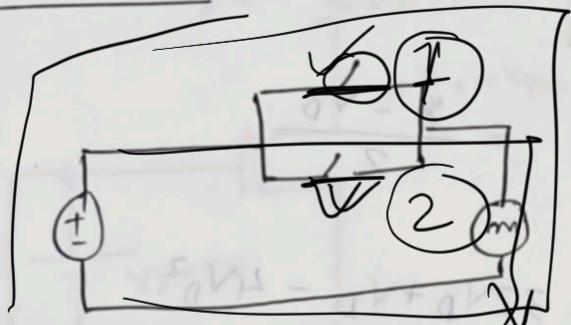


S <sub>1</sub>	S <sub>2</sub>	Q	Q̄
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

∴ NOR Gate:

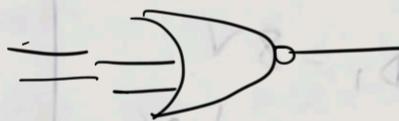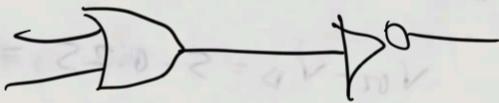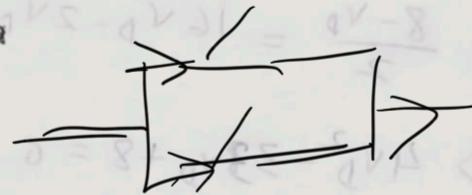

↓  
about

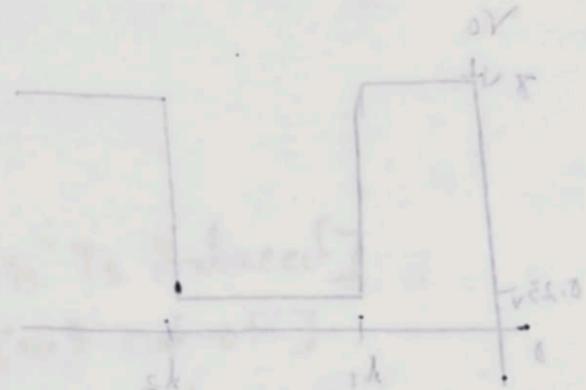

**TYU 3.12** The circuit shown in Figure 3.45 is biased at  $V_{DD} = 10 \text{ V}$ , and the transistor parameters are  $V_{TN} = 0.7 \text{ V}$  and  $K_n = 4 \text{ mA/V}^2$ . Design the value of  $R_D$  such that the output voltage will be  $v_O = 0.20 \text{ V}$  when  $v_I = 10 \text{ V}$ . (Ans.  $0.666 \text{ k}\Omega$ )

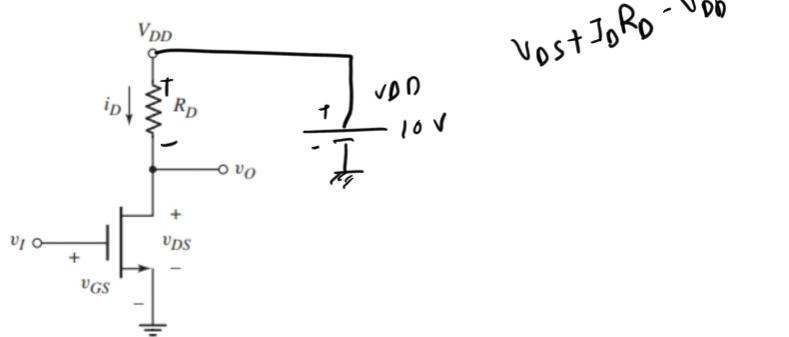


Figure 3.45 NMOS inverter circuit

Nmos,

$$V_{TN} = 0.7 \text{ V}$$

$$K_n = 4 \text{ mA/V}^2$$

$$\text{For } V_i = 10 \text{ V}, \text{ Check } V_{GS}, \\ V_{GS} = 10 \text{ V}, \quad V_S = 0 \text{ V} \\ \therefore V_{GS} = 10 - 0 = 10 \text{ V} > V_{TN} \quad [\text{ch induced}]$$

Triode [Assuming]

$$I_D = K_n [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2] \\ = K_n [2(V_{GS} - 0.7) V_D - V_D^2] = [74.4 V_D - 4 V_D^2]$$

$$I_D = \frac{V_{DD} - V_{DS}}{R_D}$$

$$\Rightarrow 74.4(0.2) - 4(0.2)^2 = \frac{V_{DD} - V_{DS}}{R_D}^{0.2}$$


$$\Rightarrow 14.88 - 0.16 = \frac{10 - 0.2}{R_D}$$

$$\Rightarrow 14.72 = \frac{9.8}{R_D}$$

$$\therefore R_D = 0.666 \text{ k}\Omega$$

$$V_D = V_{OS} = 0.2 \text{ V}$$

- The transistor in the circuit shown in Figure has parameters  $K_n = 4 \text{ mA/V}^2$  and  $V_{TN} = 0.6V$ , and is used to switch the LED on and off. The LED cut-in voltage is  $V_y = 1.2V$ . The LED is turned on by applying an input voltage of  $V_I = 5V$ .  $R = 1.2k$ . Determine  $I_D$  and  $V_{DS}$ .
- The transistor in the circuit shown in Figure has parameters  $K_n = 3 \text{ mA/V}^2$  and  $V_{TN} = 0.6V$ , and is used to switch the LED on and off. The LED cut-in voltage is  $V_y = 1.6V$ . The LED is turned on by applying an input voltage of  $V_I = 5V$ . Design  $R$  such that  $V_{DS} = 0.15V$  for  $V_I = 5V$ . Determine  $I_D$ .

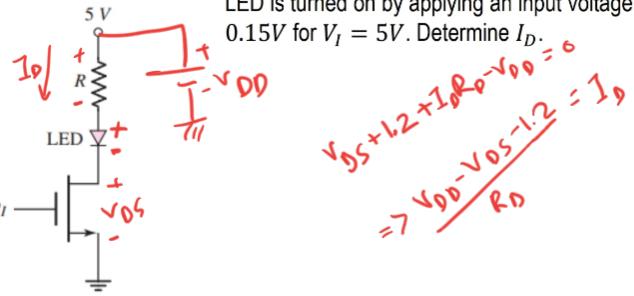

Given,  $K_n = 4$ ,  $V_{TN} = 0.6V$ ,  $V_y = 1.2V$

$$[V_a = 5V, V_s = 0]$$

$$V_I = 5V, R = 1.2k \quad I_D = ?, V_{DS} = ?$$

First, check  $V_{DS} = V_a - V_s = 5 > V_{TN}$  [ch induced]

Assume Triode,

$$I_D = K_n [2(V_{DS} - V_{TN})V_{DS} - V_{DS}^2]$$

$$= 4 [2(5 - 0.6)V_D - V_D^2] = \frac{V_{DD} - V_{DS} - 1.2}{R_D}$$

$$\Rightarrow 35.2V_D - 4V_D^2 = \frac{5 - 1.2 - V_D}{1.2} \Rightarrow 42.24V_D + V_D - 4.8V_D^2 - 3.8 = 0$$

$$\Rightarrow 4.8V_D^2 - 43.24V_D + 3.8 = 0$$


Check  $V_{DS}$ :

$$V_D = 8.919, 0.088$$

$$V_a - V_{D1} \Rightarrow 5 - 8.919 < V_{TN} \times$$


$$V_a - V_{D2} \Rightarrow 5 - 0.088 > V_{TN} \times \therefore V_D = 0.088$$
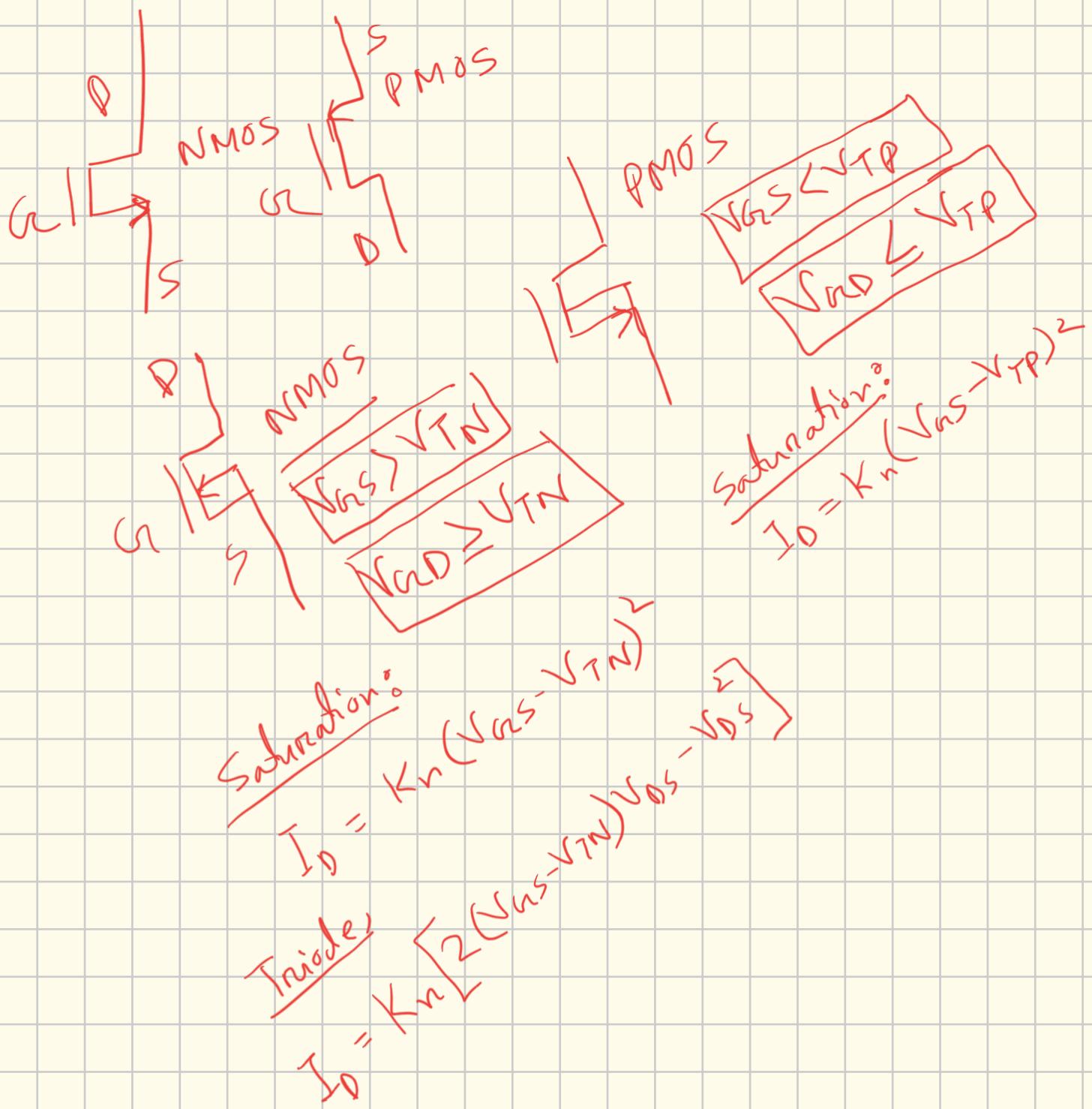
$$\therefore I_D = \frac{V_{DD} - V_D}{1.2} = \frac{5 - 1.2 - 0.088}{1.2} = 3.873 \text{ mA}$$



BJT

NPN

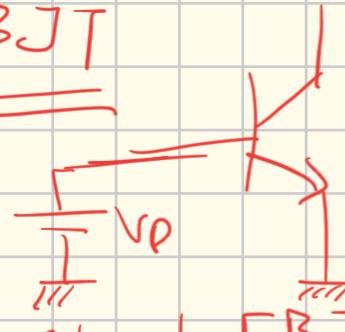

$$\text{Check } [V_{BE}] = V_p - V_N > 0.7$$

$[F \cdot B] \rightarrow$  Active or Saturation

$[R \cdot B] \rightarrow$  Cutoff

Active,  $V_{BE} = 0.7 \text{ V}$


$$V_{CE} > 0.3 \text{ V}$$

$$V_{BC} > -0.4 \text{ V}$$


Saturation,  $V_{CE} = 0.2 \text{ V}$

$$V_{BE} = 0.7 \text{ V}$$

$$V_{CB} = -0.5$$

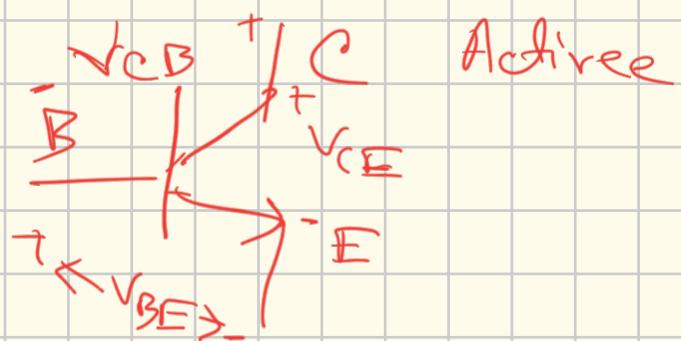

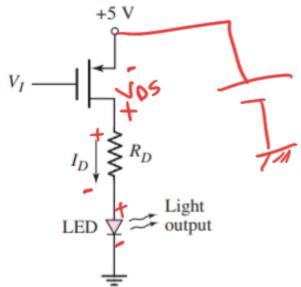1. The transistor in the circuit shown in Figure has parameters  $K_P = 3 \text{ mA/V}^2$  and  $V_{TP} = -0.6V$ , and is used to switch the LED on and off. The LED cutin voltage is  $V_y = 1.2V$ . The LED is turned on by applying an input voltage of  $V_I = 0V$ . Design  $R_D$  such that  $V_{DS} = -0.12V$  for  $V_I = 0V$ . Determine  $I_D$ .



Given,  $K_P = 3$

$$V_{TP} = -0.6V$$

$$V_y = 1.2V$$

$$V_I = 0V$$

$$V_o = V_{DS} = -0.12V$$

$$V_S = 5V$$

Check  $V_{DS}$ ,  $V_{DS} - V_y = 0 - 5 = -5 < V_{TP}$  [Ch induced]

Assume Triode,

$$I_D = K_P \left[ 2(V_{DS} - V_{TP}) \frac{V_{DS} - V_{SS}}{2} \right]$$

$$= 3 \left[ 2(-5 + 0.6)(-0.12) - (0.12) \right] = 3.1248 \text{ mA}$$

$$\therefore +1.2 + I_D R_D - V_{DS} - V_{SS} = 0$$

$$\Rightarrow R_D = \frac{V_{DS} + V_{SS} - 1.2}{I_D} = \frac{-0.12 + 5 - 1.2}{3.1248} = 1.178 \text{ k}\Omega$$

$$\therefore R_D = 1.178 \text{ k}\Omega \text{ (Ans.)}$$