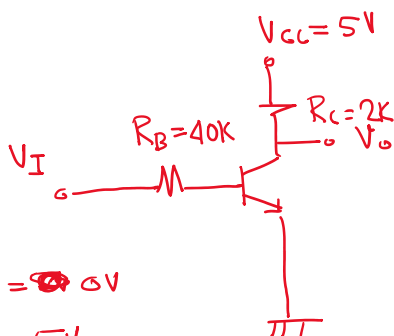



BJT Switching

Cut-off & Saturation

Cut-off & Triode Region } MOSFET Switching
 OFF ON



or $0 < t < t_1$: $V_I = 0V$
 $t_1 < t < t_2$: $V_I = 5V$

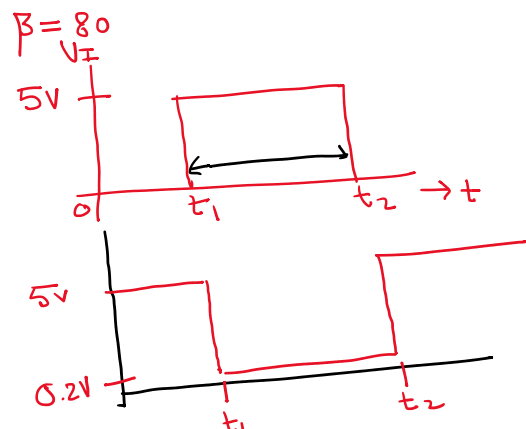 $0 < t < t_1$, $V_I = 0V$ 


Check EBJ, $V_P - V_N = 0 - 0 < 0.7V$
 R.B

Cut-off Region.

$$I_B = I_C = I_E = 0$$

$$V_O = V_{CE} = V_{CC} - I_C R_C$$

$$V_O = V_{CE} = V_{CC} = 5V$$

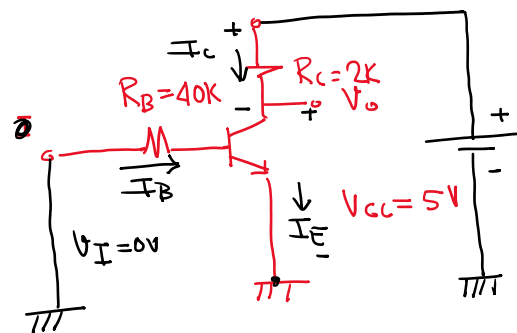


$V_I = 0 \rightarrow V_O = 5V$
 Low \rightarrow High.

 $t_1 < t < t_2$: $V_I = 5V$

Check EBJ: F.B

$$V_P - V_N = 5 - 0 > 0.7V$$

- Saturation

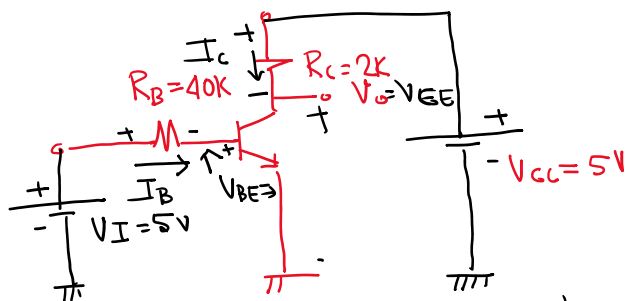- ~~Cut-off~~ Active

Assume Saturation: \square No α/β to determine currents

$$\square V_{CE}(\text{Sat}) = 0.2V$$

$$\square \beta_s = \left(\frac{I_C}{I_B} \right)_{\text{sat}} < \beta \text{ [for Justification]}$$

$$V_I - I_B R_B - V_{BE} = 0$$

$$\Rightarrow I_B = \frac{V_I - V_{BE}}{R_B}$$

$$= \frac{5 - 0.7}{40k} = 0.1075 \text{ mA}$$

$$V_O = V_{CE}(\text{Sat}) = 0.2V$$

$V_I = 5V \rightarrow V_O = 0.2V$
 High \rightarrow Low

KVL. In output loop


$$= \frac{5-0.7}{40K} = 0.1075 \text{ mA}$$

KVL In output loop

$$+V_{CE}(\text{sat}) + I_C R_C = V_{CC} \Rightarrow V_{CE}(\text{sat}) = V_o = \frac{V_{CC} - V_{CE}}{R_C}$$

$$= \frac{5-0.2}{2} = 2.4 \text{ mA}$$
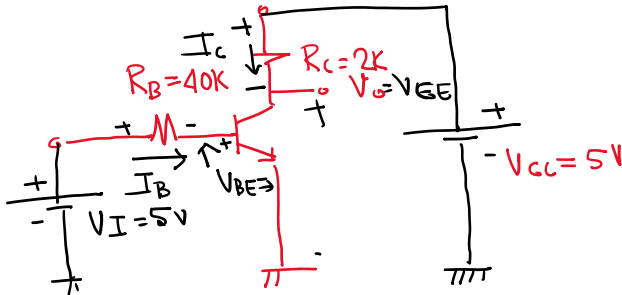
$$\beta_f = \frac{2.4}{0.1075} \approx 22 < \beta(80)$$



Assume, Active Region
 □ α/β Allowed to determine currents
 □ Justification. $V_{CE} \rightarrow$ R.B or not
 $V_{CE} > 0.3V \rightarrow$ Active
 $< 0.3V \rightarrow$ Saturation.

$$I_B = 0.1075 \text{ mA},$$

$$I_C = \beta I_B = 80 \times 0.1075 \text{ mA} = 8.6 \text{ mA}$$

$$+V_{CE} + I_C R_C = V_{CC} \Rightarrow V_{CE} = V_{CC} - I_C R_C$$

$$= 5 - 8.6 \times 2$$

$$= -12.2V < 0.3V$$

V_{CE}


Saturation

$$V_{CE} = V_o = 0.2V$$

$$V_I - I_B R_B - V_{BE} = 0$$


$$\Rightarrow I_B = \frac{V_I - V_{BE}}{R_B}$$
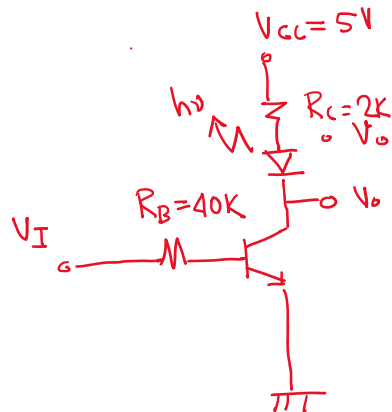
$$= \frac{5-0.7}{40K} = 0.1075 \text{ mA}$$



$V_I = 0, I_B = I_C = I_E = 0$
 LED is OFF \rightarrow R.B.

$$V_I = 5V$$

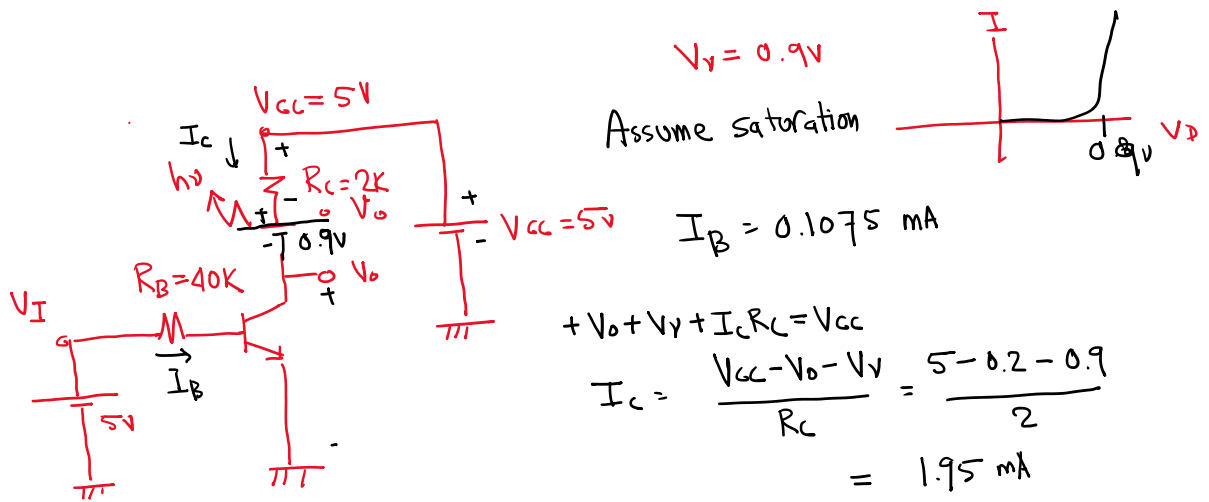

Assume saturation

$$I_B = 0.1075 \text{ mA}$$

$$+V_o + V_{BE} + I_C R_C = V_{CC}$$

$$I_C = \frac{V_{CC} - V_o - V_{BE}}{R_C} = \frac{5 - 0.2 - 0.9}{2} = 1.95 \text{ mA}$$

$$\beta_{\beta} = \frac{1.95}{0.1075} = 18.13 < \beta (80)$$

Assume Active, $I_B = 0.1075 \text{ mA}$, $I_C = \beta I_B = 8.6 \text{ mA}$

$$+V_{CE} + V_{BE} + I_C R_C = V_{CC} \Rightarrow V_{CE} = V_{CC} - V_{BE} - I_C R_C$$

$$= 5 - 0.9 - 8.6 \times 2$$

$$= -13.1V < 0.3V$$

\hookrightarrow Saturation region. $V_o = V_{CE} = 0.2V$