

### Section 10.5: Piecewise-Linear Diode Models

**P10.42.** If a nonlinear two-terminal device is modeled by the piecewise-linear approach, what is the equivalent circuit of the device for each linear segment?

**P10.43.** A resistor  $R_a$  is in series with a voltage source  $V_a$ . Draw the circuit. Label the voltage across the combination as  $v$  and the current as  $i$ . Draw and label the volt-ampere characteristic ( $i$  versus  $v$ ).

**P10.44.** The volt-ampere characteristic of a certain two-terminal device is a straight line that passes through the points (2 V, 5 mA) and (3 V, 15 mA). The current reference points into the positive reference for the voltage. Determine the equivalent circuit for this device.

**P10.45.** Consider the volt-ampere characteristic of an ideal 10-V Zener diode shown in Figure 10.14 on page 486. Determine the piecewise-linear equivalent circuit for each segment of the characteristic.

**\*P10.46.** Assume that we have approximated a nonlinear volt-ampere characteristic by the straight-line segments shown in Figure P10.46(c). Find the equivalent circuit for each segment. Use these equivalent circuits to find  $v$  in the circuits shown in Figure P10.46(a) and (b).

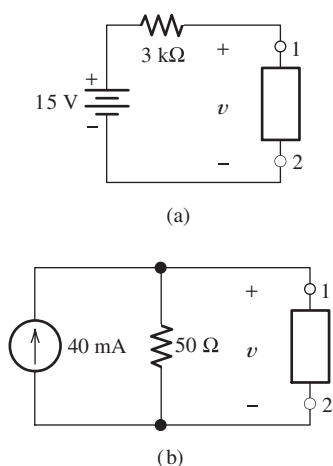


Figure P10.46

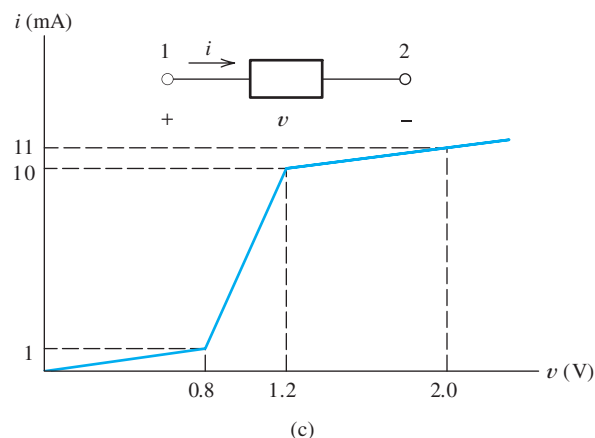


Figure P10.46 (Cont.)

**\*P10.47.** The Zener diode shown in Figure P10.47 has a piecewise-linear model shown in Figure 10.19 on page 489. Plot load voltage  $v_L$  versus load current  $i_L$  for  $i_L$  ranging from 0 to 100 mA.

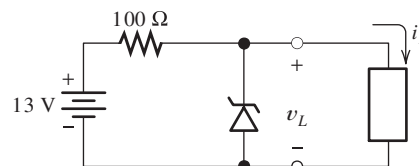


Figure P10.47

**P10.48.** The diode shown in Figure P10.48 can be represented by the model of Figure 10.23 on page 491, with  $V_f = 0.7$  V. **a.** Assume that the diode operates as an open circuit and solve for the node voltages  $v_1$  and  $v_2$ . Are

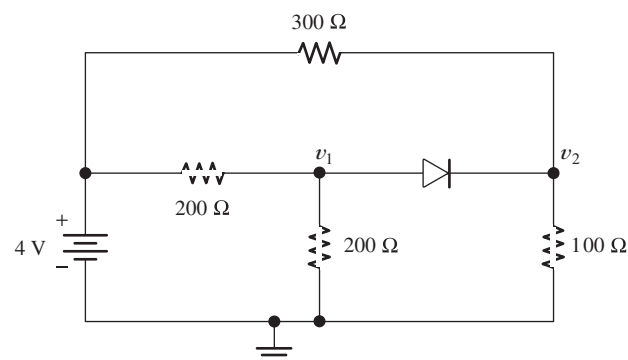


Figure P10.48