

Department of Electrical & Electrical Engineering
BRAC University
Semester- Fall 2025



EEE205L

ELECTRONIC CIRCUITS I LABORATORY

Section: 01

Experiment: 04

Group Number: 01

Group Members:

SL	Student ID	Name
01.	24121308	Alif Tamjid
02.	24121205	Souvik Bamran Ratul
03.	24121058	Muhammad Mushfiquir Rahman
04.	24121204	Abir Chowdhury Ratul
05.	24121076	Tashin Ahmed Sakib

Submitted by :

Submitted To :

Name : Alif Tamjid

Aldrin Nippon Bobby

ID : 24121308


Objective:

Analyzing the characteristics of N-channel MOSFET at its input and output.

Equipments:

1. Breadboard
2. Jumper Wires
3. DC voltage Source
4. $100\text{k}\Omega$ & $1\text{k}\Omega$ Resistors
5. MOSFET (IRF540N)

Circuit:

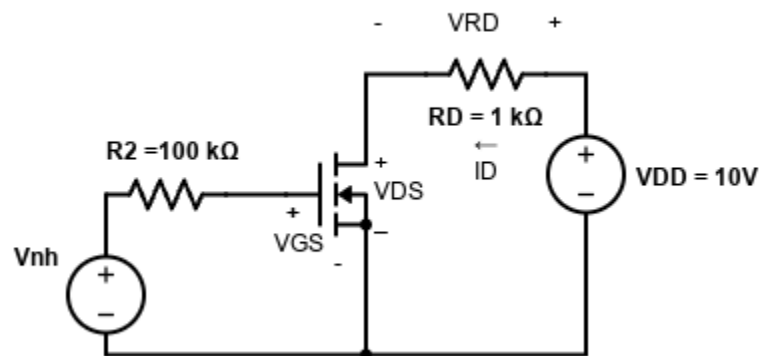


Data:

V_{RD} (mV)	V_{GS} (V)
100.1	3.14

R_D (KΩ)	V_{DS} (mV)	V_{RD} (mV)	$I_D = V_{RD} / R_D$ (μA)
0.985	10	27.6	28.02
0.985	30	60.3	61.22
0.985	50.8	76.6	77.77
0.985	70.8	84	85.28
0.985	90	88	89.34
0.985	100.3	89.2	90.56
0.985	201	94	95.43
0.985	302	95.4	96.85
0.985	405	96	97.46
0.985	504	96.4	97.87
0.985	502	96.2	97.66
0.985	705	96.1	97.56
0.985	804	96.1	97.56
0.985	903	96.1	97.56
0.985	1006	96.1	97.56
0.985	2000	96.8	98.27
0.985	4010	97.1	98.58
0.985	6000	97.5	98.98
0.985	8010	97.8	99.29
0.985	10010	97.9	99.39

Graph:

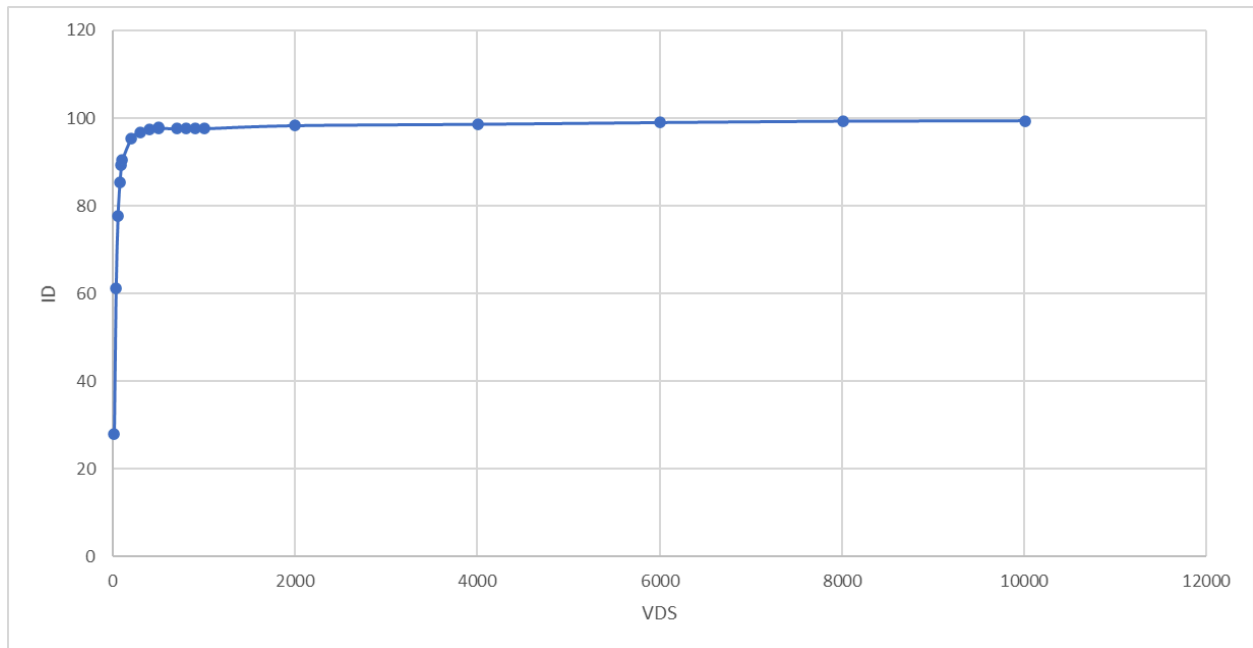


Appendix:

Experiment: 04 → MOSFET Characteristics

Group: 01


Circuit:

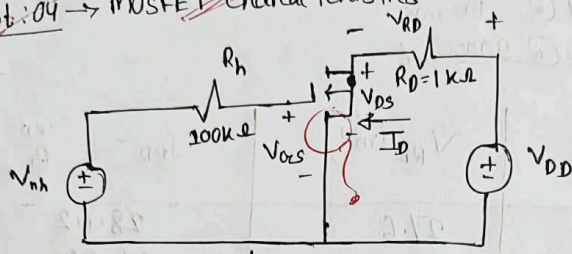

Data:

$$V_{DD} = 10V$$

$$V_{RD} = 100mV$$

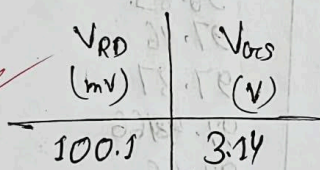


✓


$V_{DS} \rightarrow 10 \text{ mV} - 90 \text{ mV} @ 20 \text{ mV}$
 $100 \text{ mV} - 1000 \text{ mV} @ 100 \text{ mV}$
 $2000 \text{ mV} - 10000 \text{ mV} @ 2000 \text{ mV}$

$R_D (\text{k}\Omega)$	$V_{DS} (\text{mV})$	$V_{RD} (\text{mV})$	$I_{RD} = \frac{V_{RD}}{R_D} (\text{mA})$
0.985	10	27.6	28.02
	30	60.3	61.22
	50.8	60.3 76.6	77.77
	70.8	84	85.28
	90	88	89.34
	100.3	89.2	90.56
	201	94	95.43
	302	95.4	96.85
	405	96	97.46
	504	96.4	97.87
	602	96.2	97.466
	705	96.1	97.56
	804	96.1	97.56
	903	96.11	97.56
	1006	96.1	97.56
	2000	96.8	98.27
	4010	97.1	98.58
	6000	97.5	98.98
	8010	97.8	99.29
	10010	97.9	99.39

Exp graph:

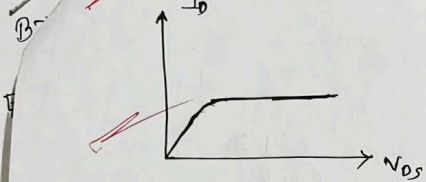

Terminal Configuration:

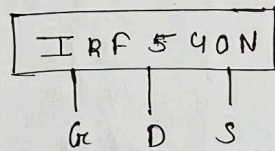

$$\frac{10}{10}$$

Alto

2015- November - 20

Experiment 3

↓

Clamping

↓

Alright