

Brac University
Department of Electrical & Electronic Engineering
Fall2025

Course Number : EEE205L

Section :01

Group No :01



Lab Report

Experiment no: 07

Name of the experiment:

Implementation of Common Emitter BJT Amplifier Circuits

Prepared by:

Name: ID:

All Group members:

<i>Sl.</i>	<i>ID</i>	<i>Name</i>
1.	24121205	Souvik Barman Ratul
2.	24121308	Alif Tamjid
3.	24121076	Tashin Ahmed Sakib
4.	24121058	Muhammad Mushfiqur Rahman
5.	24121204	Abir Chowdhury Ratul

Objective:

The main objective of this experiment is to study the operation of a Common Emitter (CE) BJT amplifier. The voltage gain, input impedance, output impedance, and phase relationship between input and output signals are measured and analyzed.

Equipments:

1. NPN Transistor (Q2N760)
2. Resistors: 1 k Ω , 2.2 k Ω , 10 k Ω , 33 k Ω , 100 k Ω
3. Potentiometer: 100 k Ω
4. Capacitors: 1 μ F, 10 μ F, 47 μ F
5. Use Pspice app for simulation

Circuit Diagram

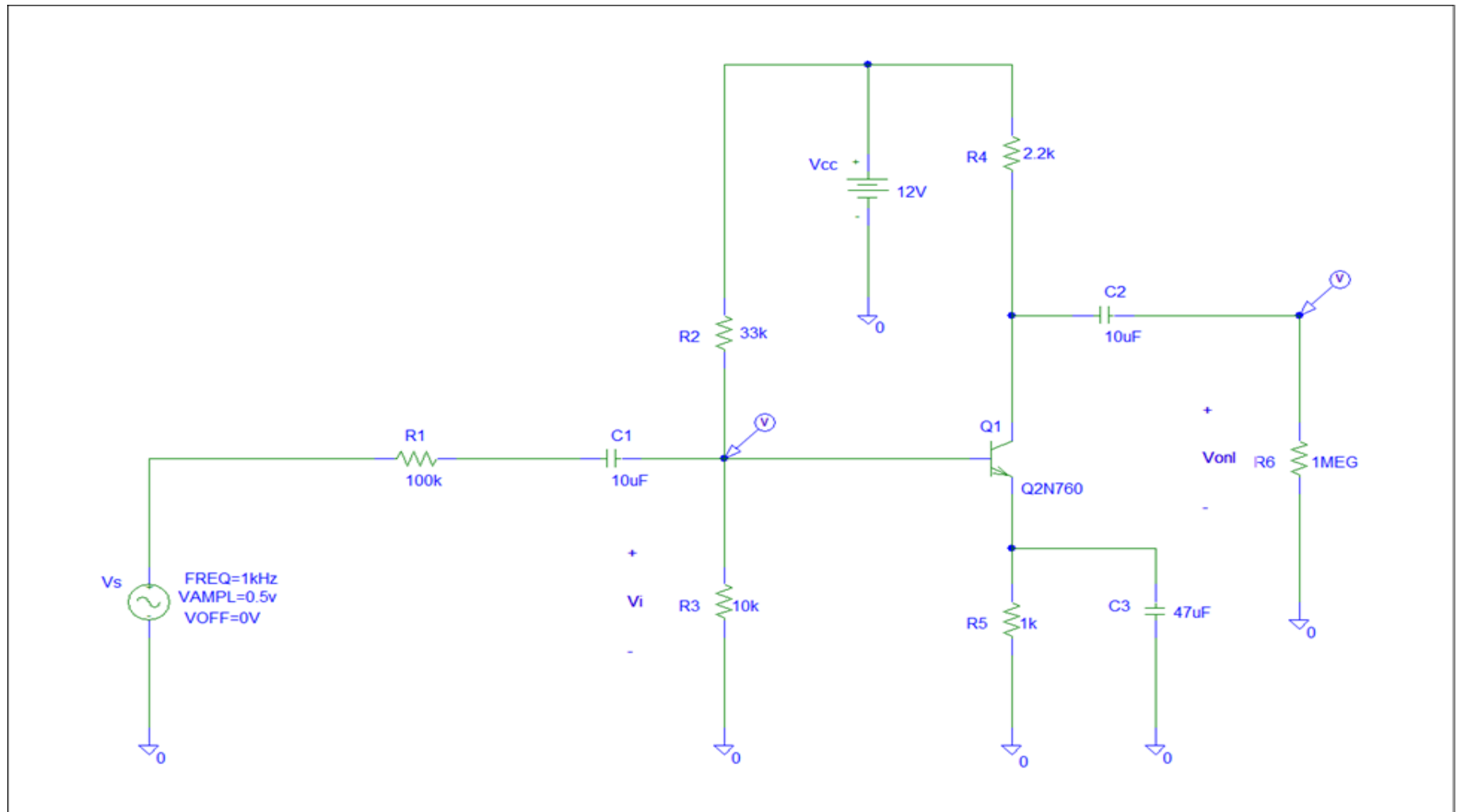


Figure:- Common Emitter BJT amplifier implemented.

Transient Parameter

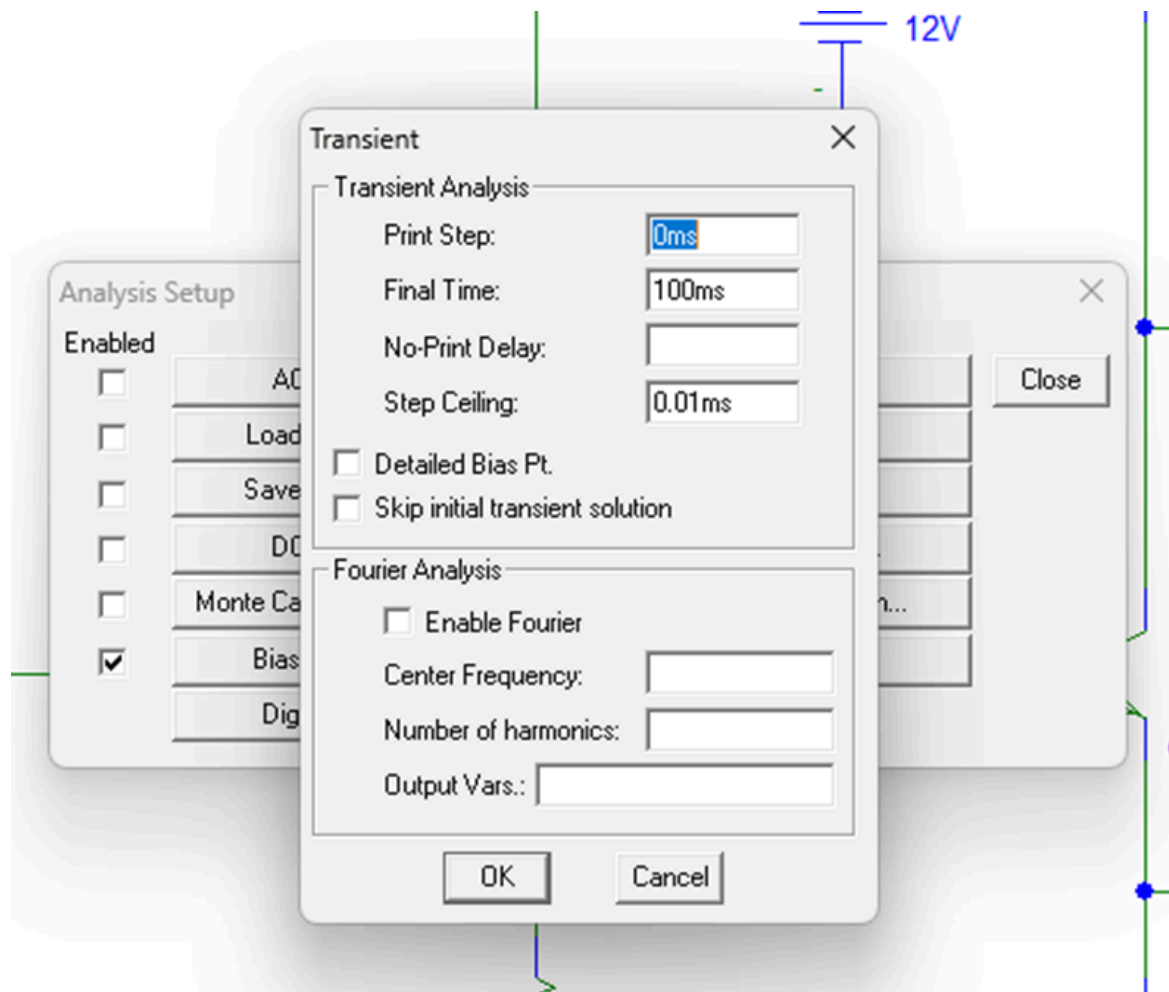


Figure:- Transient analysis parameter settings used to define simulation time and step size for observing the CE amplifier response.

V_i & V_o Graph

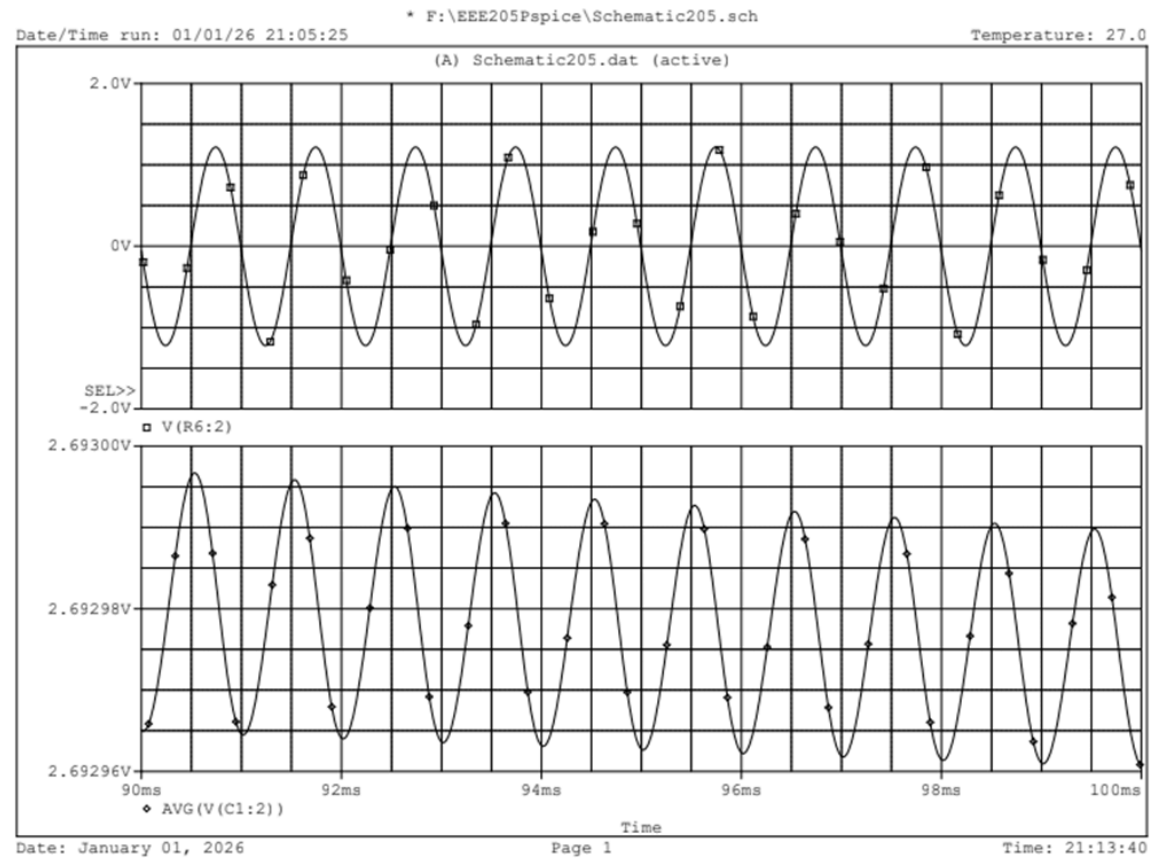


Figure: -Input and output voltage waveforms

Circuit Diagram

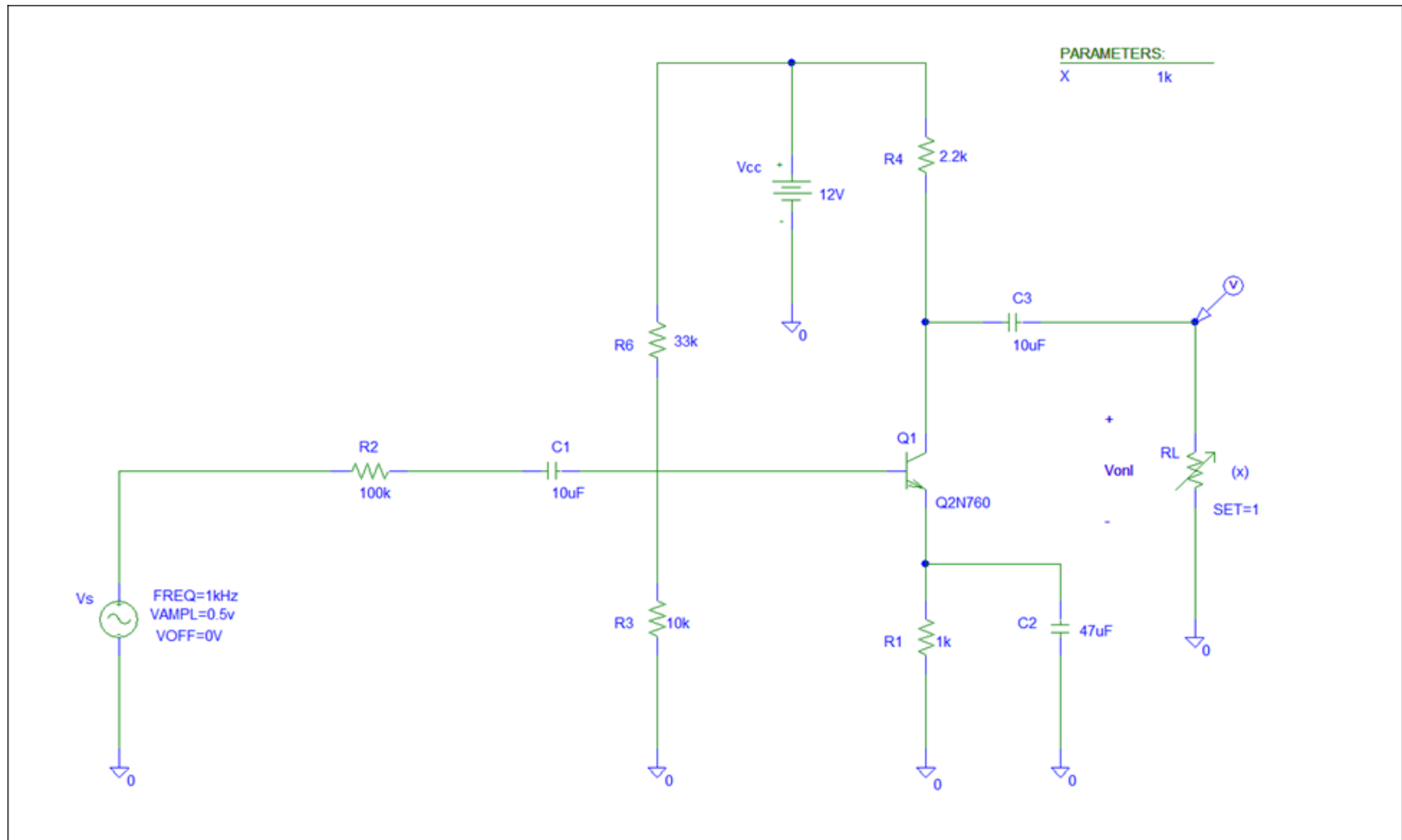


Figure: - CE amplifier circuit with output potentiometer for output impedance measurement

Transient Parameter

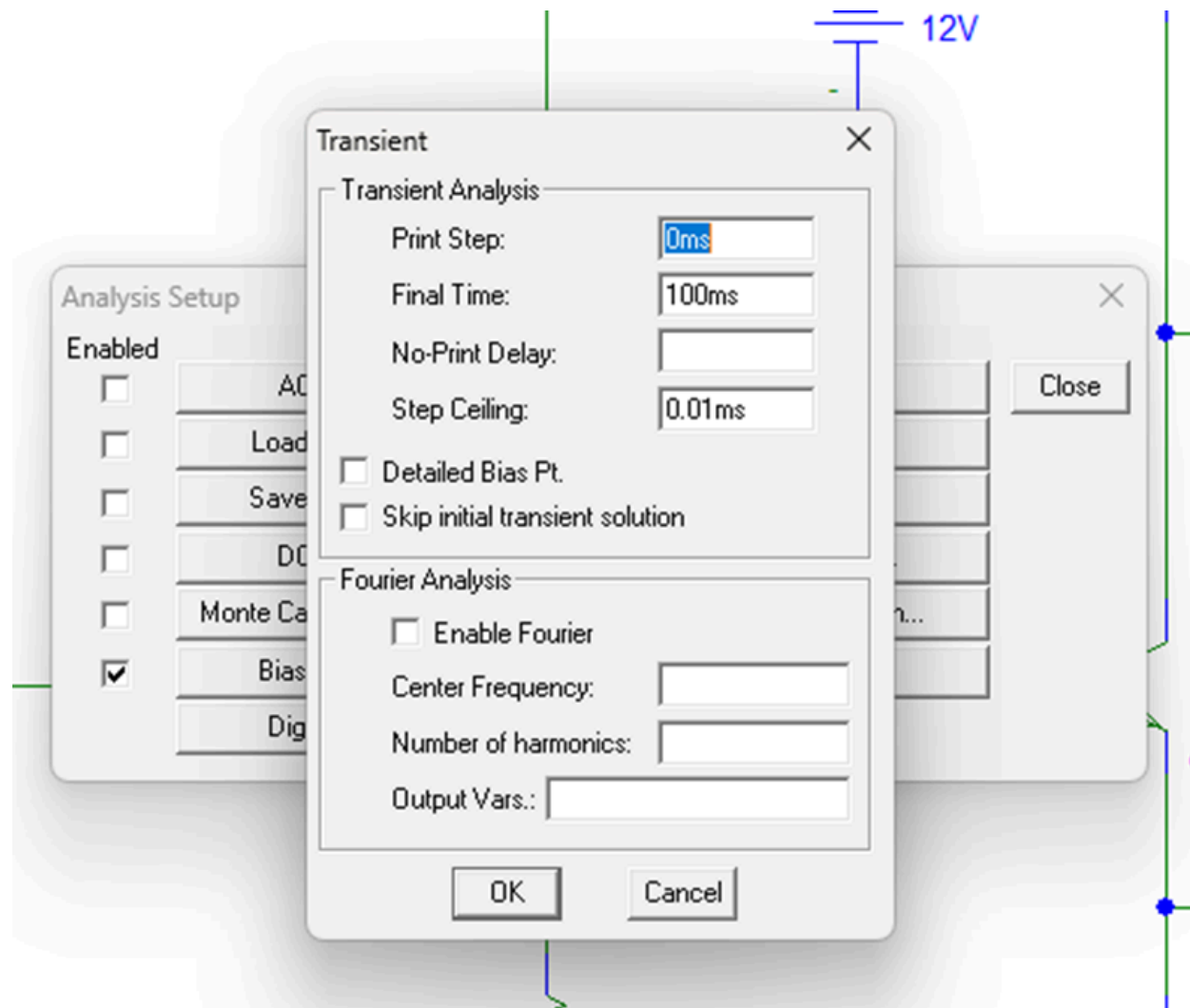


Figure: - Transient analysis parameter settings used to define simulation time and step size for observing the CE amplifier response.

Parametric parameter

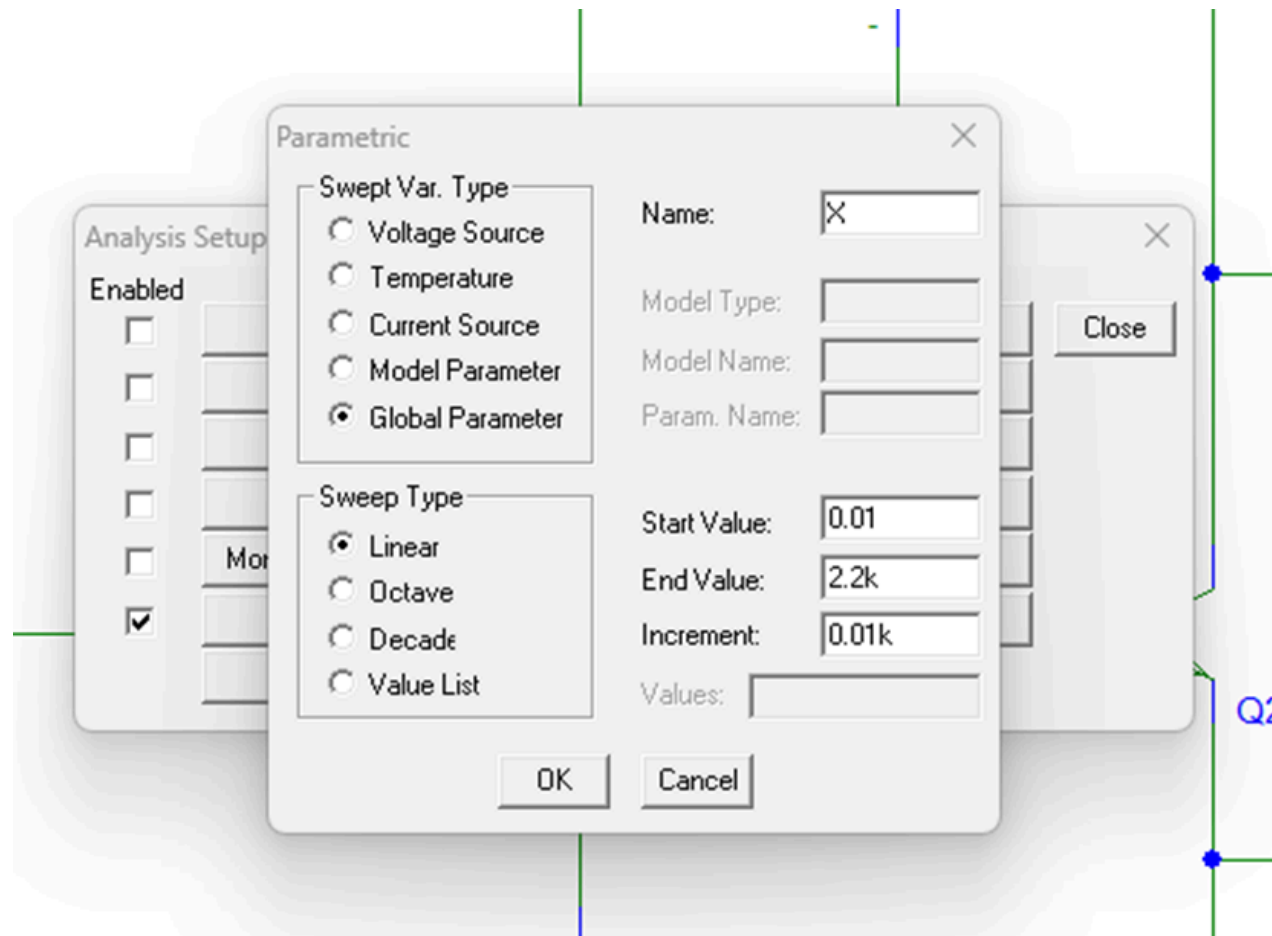


Figure: -Parametric analysis settings used to observe the effect of parameter variation on CE amplifier performance.

Axis Setting

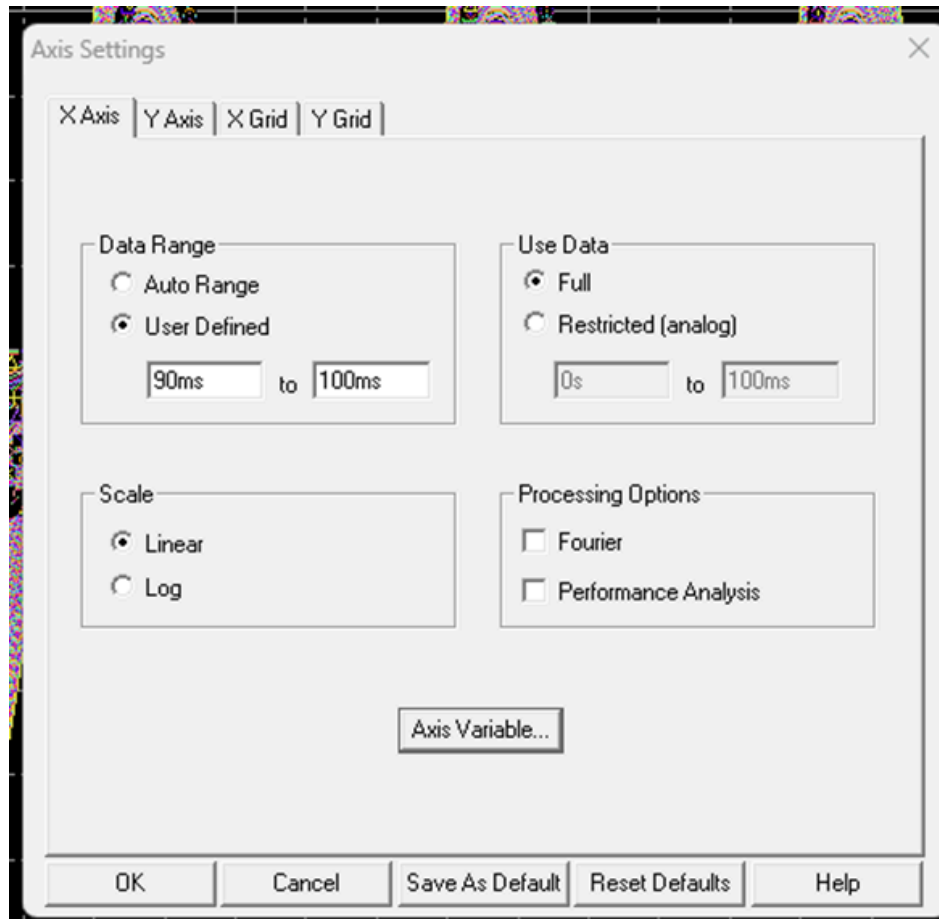


Figure: - To define the time range and scale for proper visualization of simulation waveforms.

Graph

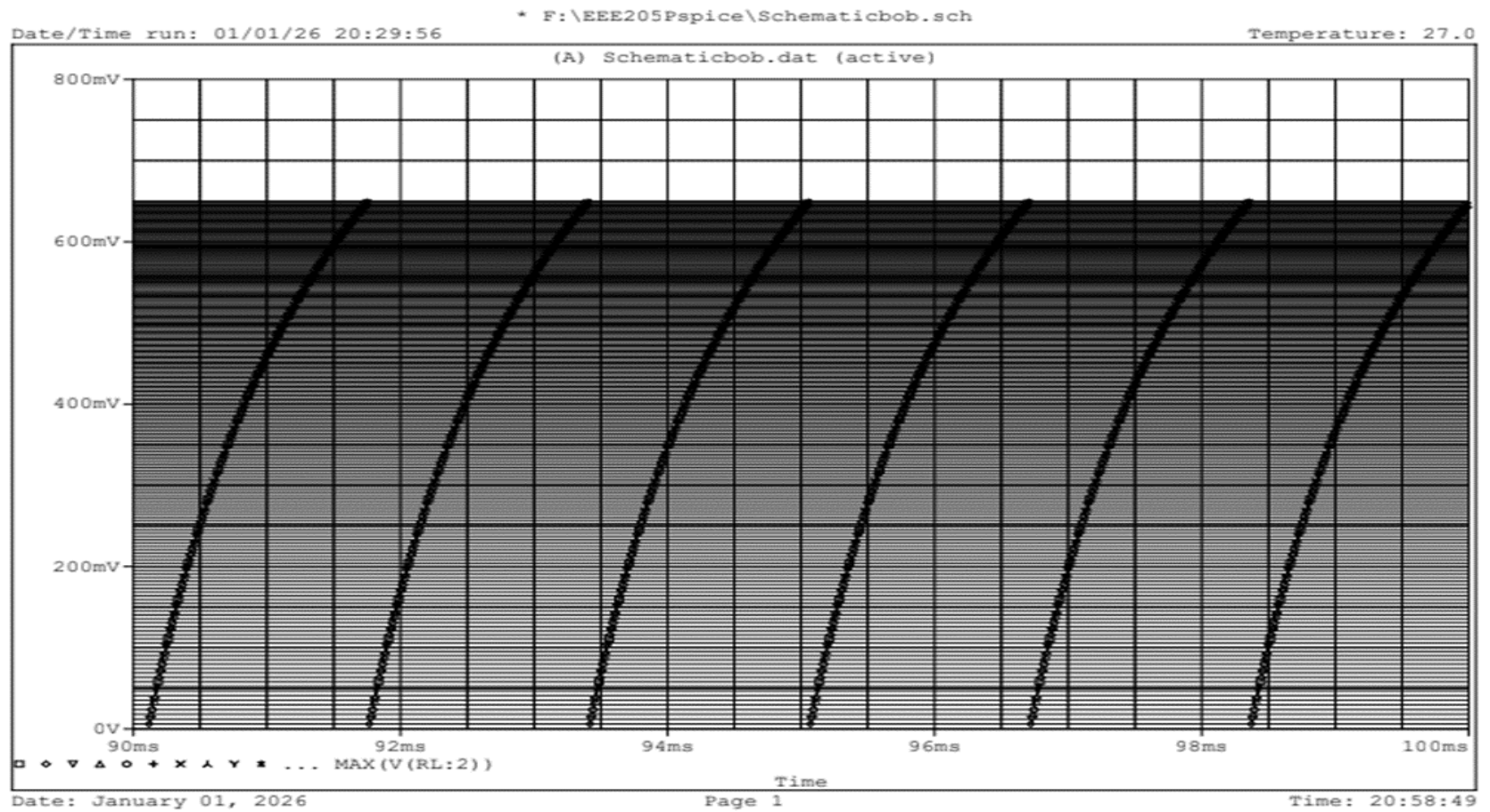


Figure: - Voltage gain characteristics of the CE amplifier.

R_o Graph

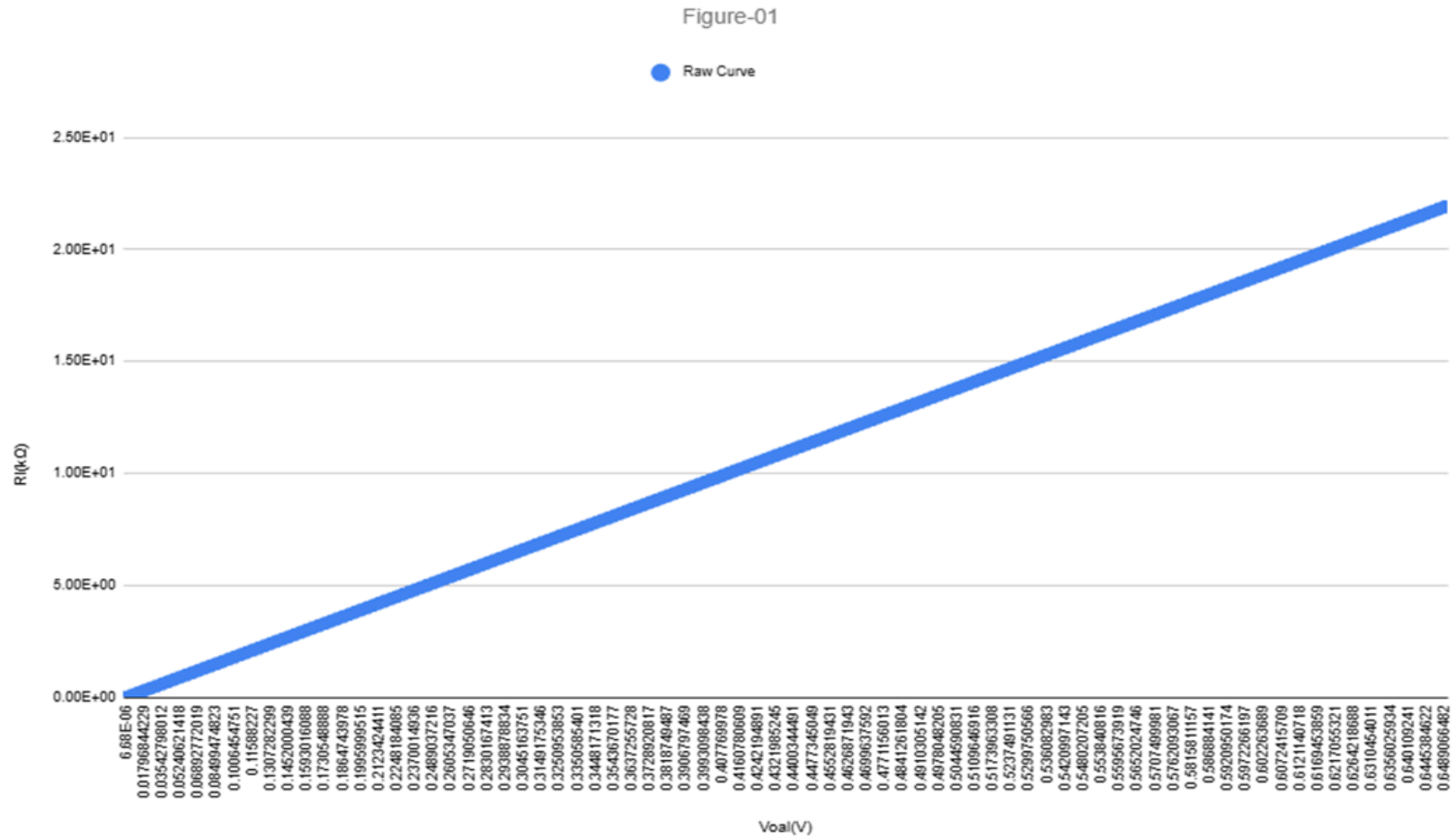


Figure: - Phase relationship graph between input and output signals

