

**Brac University**  
**Department of Electrical & Electronic Engineering**  
**Fall2025**



Course Number : EEE205L

Section :01

Group No :01

## Lab Report

**Experiment no:** 01

**Name of the experiment:**

Semiconductor and Zener diode characteristics

*Prepared by:*

Name: Souvik Barman Ratul ID: 24121205

***All Group members:***

<b><i>Sl.</i></b>	<b><i>ID</i></b>	<b><i>Name</i></b>
1.	24121205	Souvik Barman Ratul
2.	24121308	Alif Tamjid
3.	24121076	Tashin Ahmed Sakib
4.	24121058	Muhammad Mushfiqur Rahman
5.	24121204	Abir Chowdhury Ratul

**Objective:**


The objective of this experiment is to study the voltagecurrent (VI) characteristics of a semiconductor diode and a Zener diode. This experiment helps us understand how a normal diode behaves in forward bias and how a Zener diode works in reverse bias. We also aim to find the knee voltage of the semiconductor diode and the Zener breakdown voltage from the graph. This experiment helps us learn the basic working principle and practical use of diodes in electronic circuits.

**Equipments:**


1. Breadboard
2. Jumper Wires
3.  $1\text{K}\Omega$  Resistors
4.  $470\Omega$  Resistors
5. Semiconductor diode
6. Zener diode

## Circuit Diagram

### Semiconductor diode circuit:

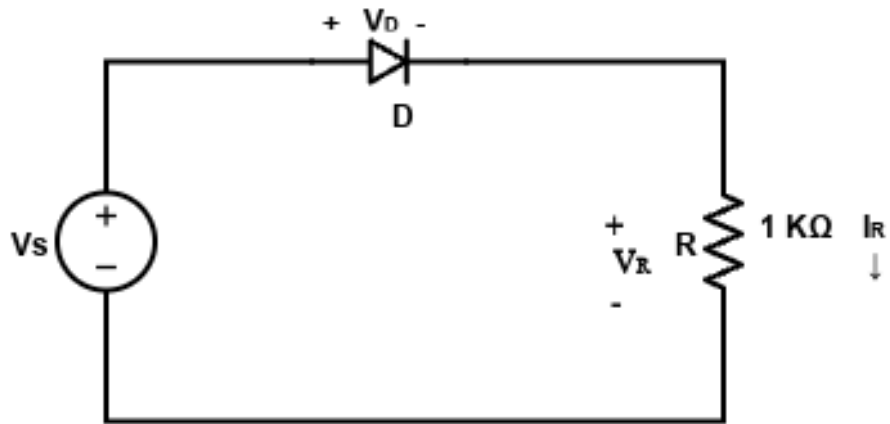

### Zener diode circuit:

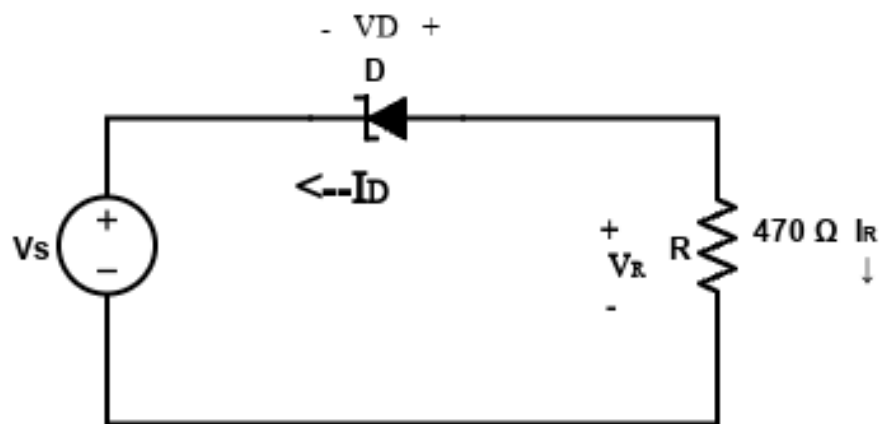

**Data Table**

<b>Semiconductor diode data</b>					
R( k $\Omega$ )	V <sub>s</sub> (V)	V <sub>D</sub> (V)	V <sub>R</sub> (V)	I <sub>R</sub> =V <sub>R</sub> /R (mA)	I <sub>D</sub> =I <sub>R</sub> (mA)
0.983	0	0	0	0	0
	0.103	0.103	0	0	0
	0.228	0.226	0	0	0
	0.33	0.323	0.006	0.0061	0.0061
	0.427	0.386	0.04	0.0407	0.0407
	0.549	0.423	0.1245	0.127	0.127
	0.667	0.442	0.225	0.23	0.23
	0.726	0.449	0.275	0.28	0.28
	0.850	0.462	0.388	0.395	0.395
	0.919	0.467	0.450	0.458	0.458
	1.034	0.476	0.556	0.560	0.566
	2.01	0.517	1.49	1.52	1.52
	3.00	0.542	2.46	2.502	2.502
	4.06	0.560	3.5	3.56	3.561
	4.99	0.573	4.42	4.50	4.50
	6.01	0.585	5.42	5.513	5.513
	7.07	0.595	6.44	6.551	6.551
	8.04	0.603	7.44	7.57	7.57
	9.04	0.611	8.43	8.576	8.576
	10.0	0.618	9.40	9.563	9.563

Zener diode data					
R( k $\Omega$ )	V <sub>S</sub> (V)	V <sub>D</sub> (V)	V <sub>R</sub> (V)	I <sub>R</sub> =V <sub>R</sub> /R (mA)	I <sub>D</sub> =-I <sub>R</sub> (mA)
0.468	0	0	0	0	0
	1.00	-1.00	0	0	0
	2.01	-2.01	0	0	0
	3.03	-3.02	0	0	0
	4.04	-4.03	0	0	0
	4.23	-4.22	0	0	0
	4.43	-4.42	0	0	0
	4.64	-4.62	0	0	0
	4.83	-4.80	0.015	0.032	-0.032
	5.04	-4.99	0.041	0.088	-0.088
	5.26	-5.13	0.121	0.259	-0.259
	5.47	-5.18	0.280	0.598	-0.598
	5.63	-5.20	0.423	0.903	-0.903
	5.85	-5.20	0.636	1.36	-1.36
	6.06	-5.21	0.844	1.803	-1.803
	7.00	-5.22	1.769	3.78	-3.78
	8.05	-5.23	2.81	6.004	-6.004
	9.05	-5.24	3.80	8.12	-8.12
	10.01	-5.23	4.75	10.149	-10.149

## Graph:-

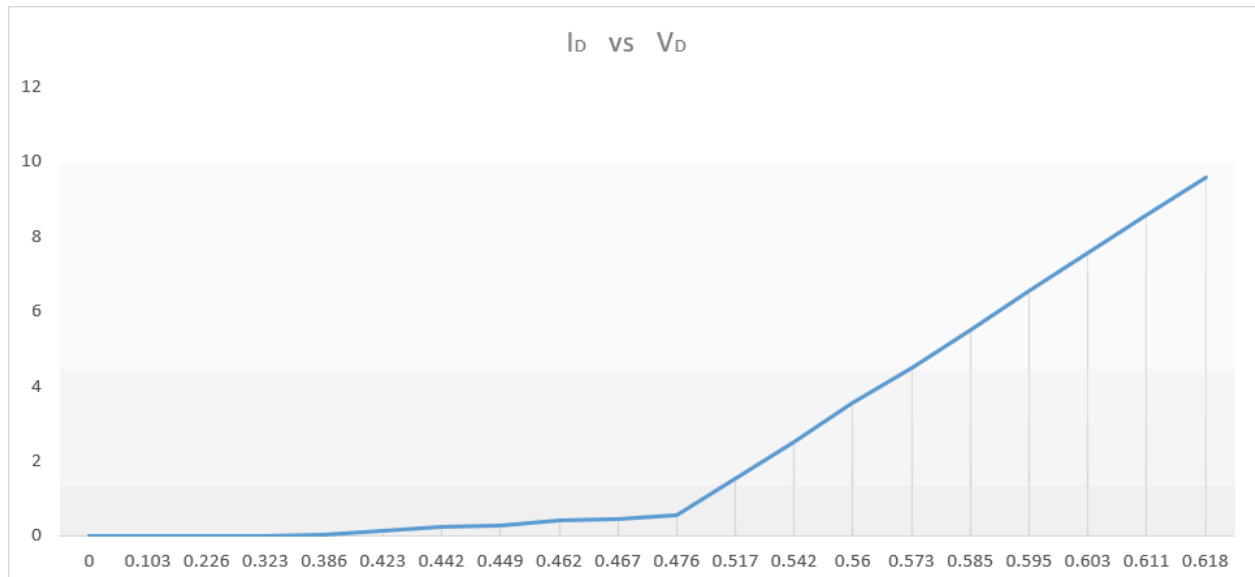


Figure 1:- Semiconductor diode graph (I<sub>D</sub> vs V<sub>D</sub>)

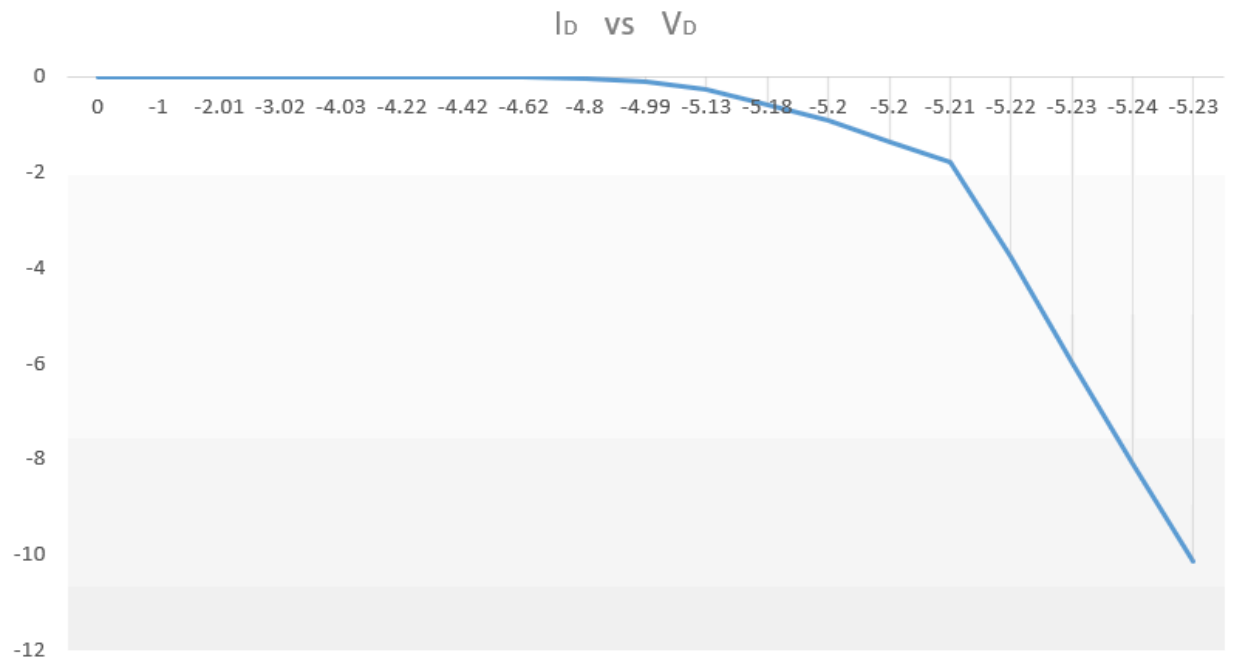


Figure 2:- Zener diode graph (I<sub>D</sub> vs V<sub>D</sub>)

## Appendix:


Q

Experiment 01

Group-1

Semiconductor and Zener Diode characteristics.



Q Semiconductor Diode characteristics:

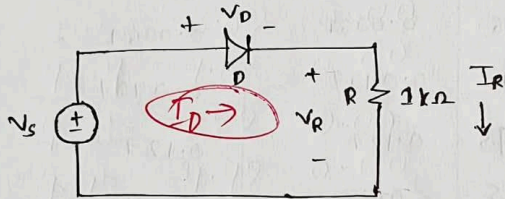


$V_s \rightarrow$  0V - 1V @ 0.1V  
1V - 10V @ 1V

$R$ (k $\Omega$ )	$V_S$ (V)	$V_D$ (V)	$V_R$ (V)	$I_R = \frac{V_R}{R}$ (mA)	$I_D = I_R$ (mA)
0.983	0.103	0.103	0	0	0
	0.228	0.226	0	0	0
	0.33	0.323	0.006	0.0061	0.0061
	0.427	0.386	0.04	0.0407	0.0407
	0.549	0.423	0.1245	0.127	0.127
	0.667	0.442	0.225	0.23	0.23
	0.726	0.449	0.275	0.28	0.28
	0.850	0.462	0.388	0.395	0.395
	0.919	0.467	0.450	0.458	0.458
	1.034	0.476	0.556	0.566	0.566
	2.01	0.517	1.49	1.52	1.52
	3.00	0.542	2.46	2.502	2.502
	4.06	0.560	3.5	3.560	3.561
	4.99	0.573	4.42	4.50	4.50
	6.01	0.585	5.42	5.513	5.513
	7.07	0.596	6.44	6.551	6.551
	8.04	0.603	7.44	7.57	7.57
	9.04	0.611	8.43	8.576	8.576
	10.0	0.618	9.40	9.563	9.563



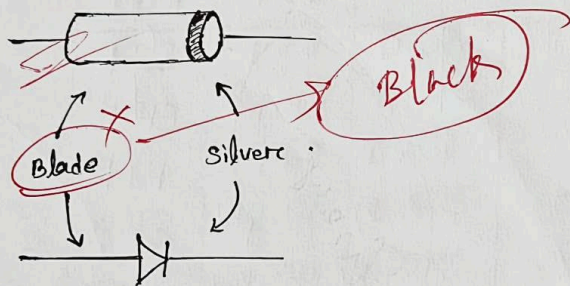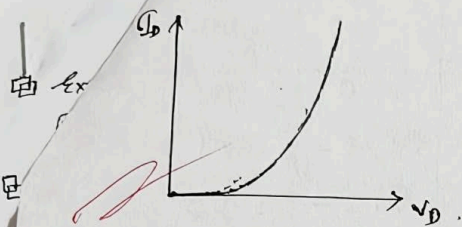


□ Zener Diode characteristics:

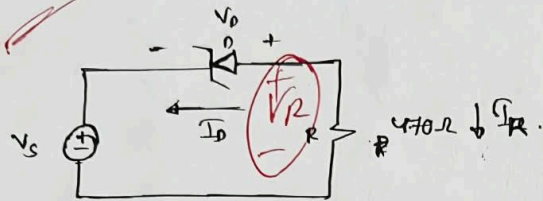

$V_s \rightarrow$  0V-4V @ 1V  
4V-6V @ 0.2V  
6V-10V @ 1V

Group 2

Experiment Rectifier	$V_s$ (V)	$V_D$ (V)	$V_R$ (V)	$I_R = \frac{V_R}{R}$ (mA)	$I_D = -I_R$ (mA)
Half 0.468	0	0	0	0	0
	1.00	-1.00	0.00	0	0
	2.01	-2.01	0.00	0	0
	3.03	-3.02	0.00	0	0
	4.04	-4.03	0.00	0	0
	4.23	-4.22	0.00	0	0
	4.43	-4.42	0.00	0	0
	4.64	-4.62	0.00	0	0
	4.83	-4.80	0.015	0.032	-0.032
	5.04	-4.99	0.041	0.088	-0.088
	5.26	-5.13	0.121	0.259	-0.259
	5.47	-5.18	0.280	0.598	-0.598
	5.63	-5.20	0.4263	0.903	-0.903
	5.85	-5.20	0.636	1.35	-1.36
	6.06	-5.21	0.844	1.803	-1.803
	7.00	-5.22	1.769	3.78	-3.78
	8.05	-5.22	2.81	6.004	-6.004
	9.05	-5.24	3.80	8.12	-8.12
	10.01	-5.23	4.75	10.149	-10.149

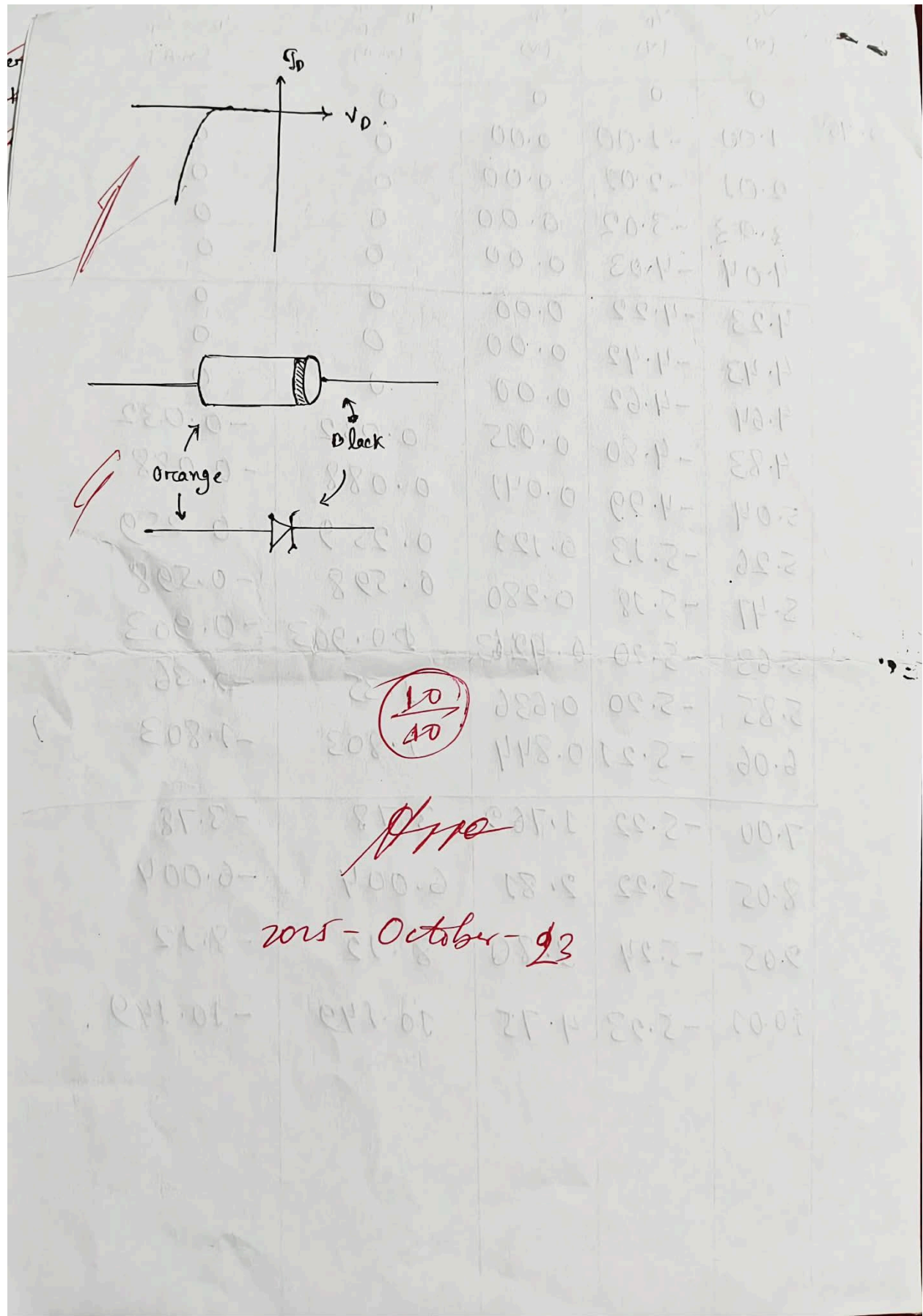

10/40

2015 - October - 23

